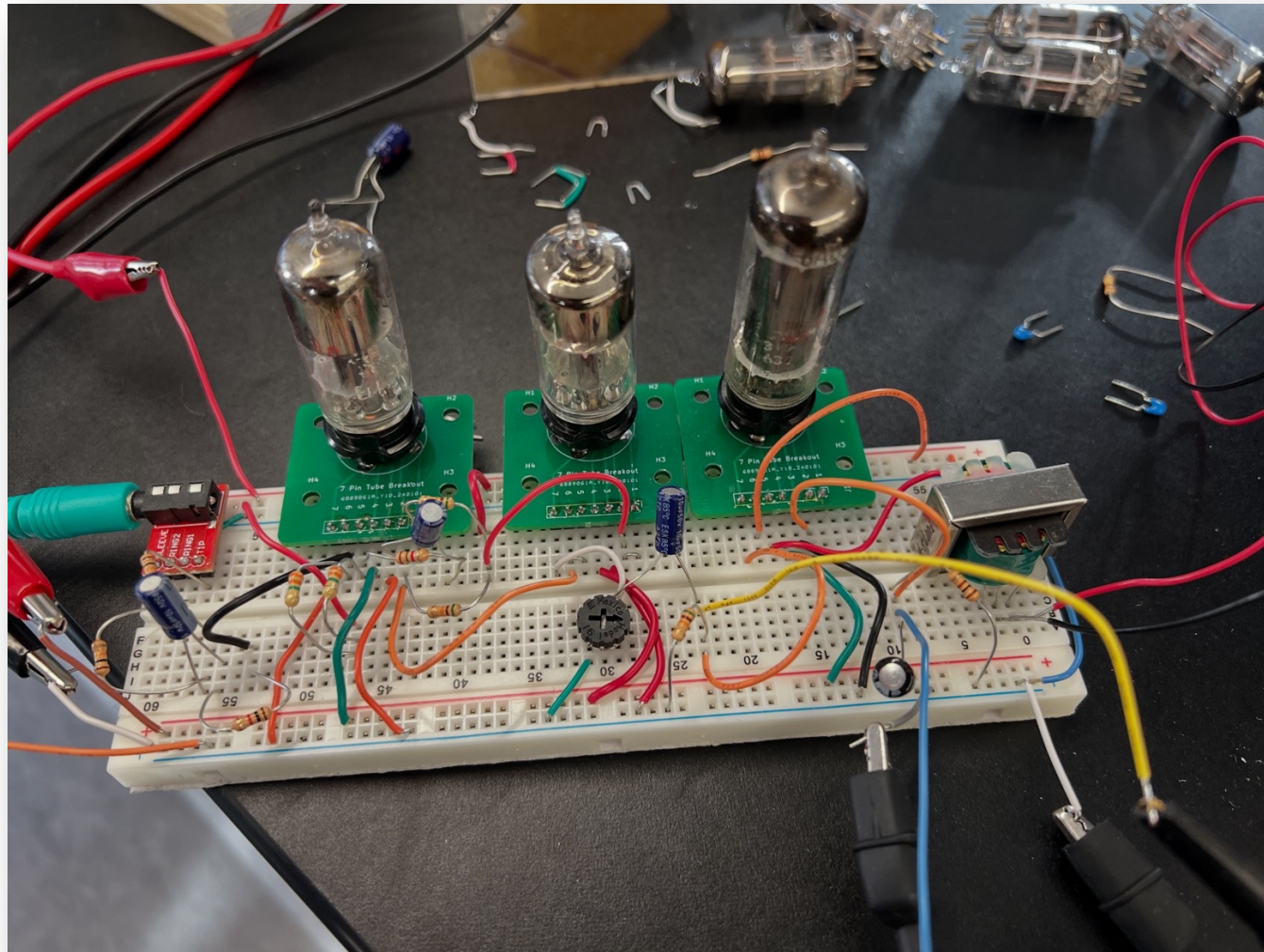



# Lecture 4

Tube and Early Transistor Electronics

# Lab 4: Tube Amp



# Lab 4: Tube Amp

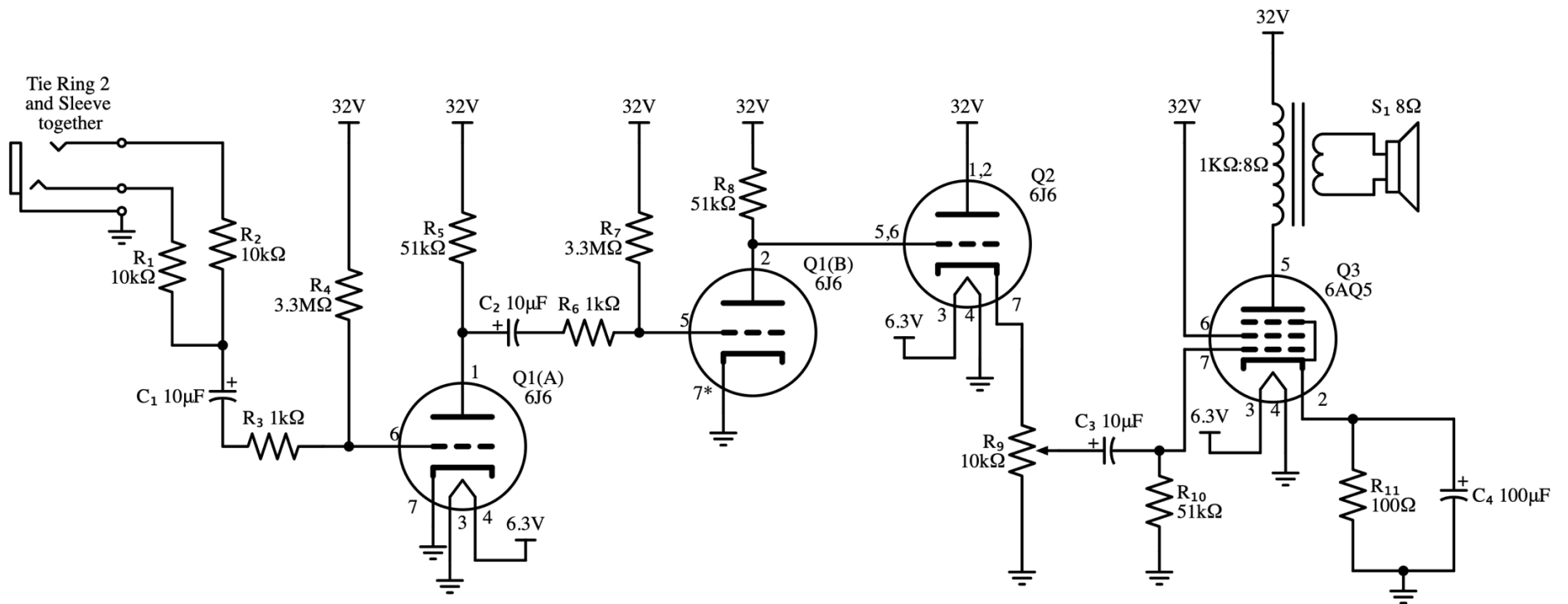


But first...



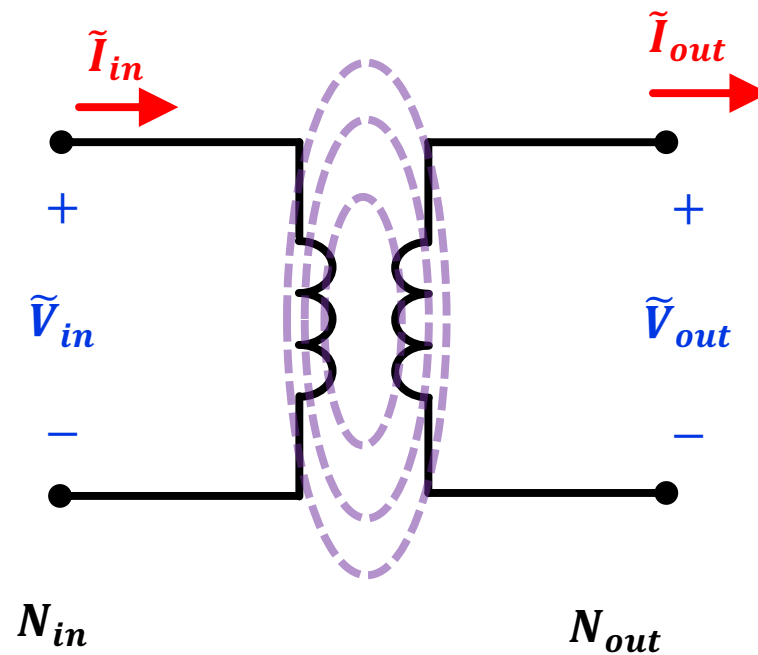
# The Transformer

- OK, so what can we use the transformer for? We can't amplify
- Several big uses:
  - Power conversion
  - **Electrical Isolation**
  - Impedance Matching
  - Coupling Stages
  - Phase Inversion



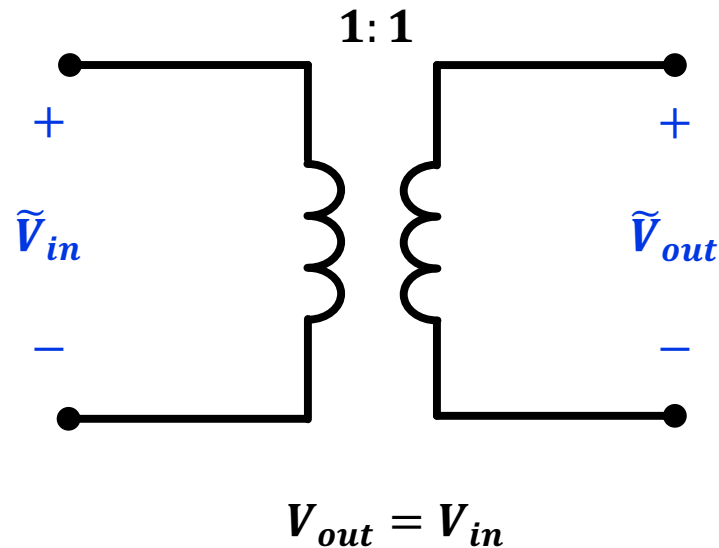
# Transformers: Isolation

- A transformer-ed power supply is electrically quite safe.
- Even if you don't need to step up/down voltage, you'll sometimes see 1:1 transformers that exist solely for the purpose of electrical isolation!


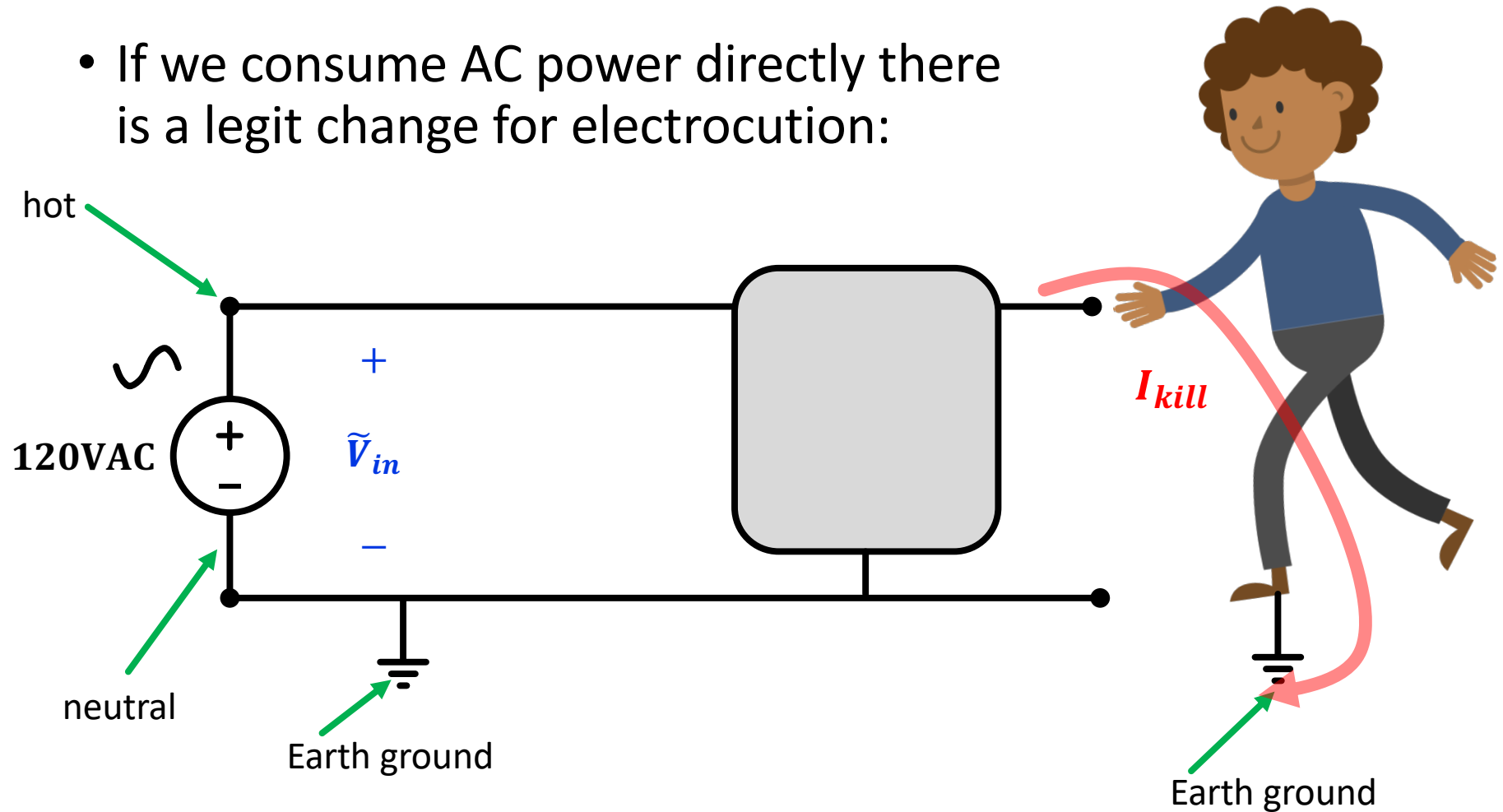
# Transformers: Isolation


- If we consume AC power directly there is a legit change for electrocution:



- If you close the circuit between hot and ground, current flows :/
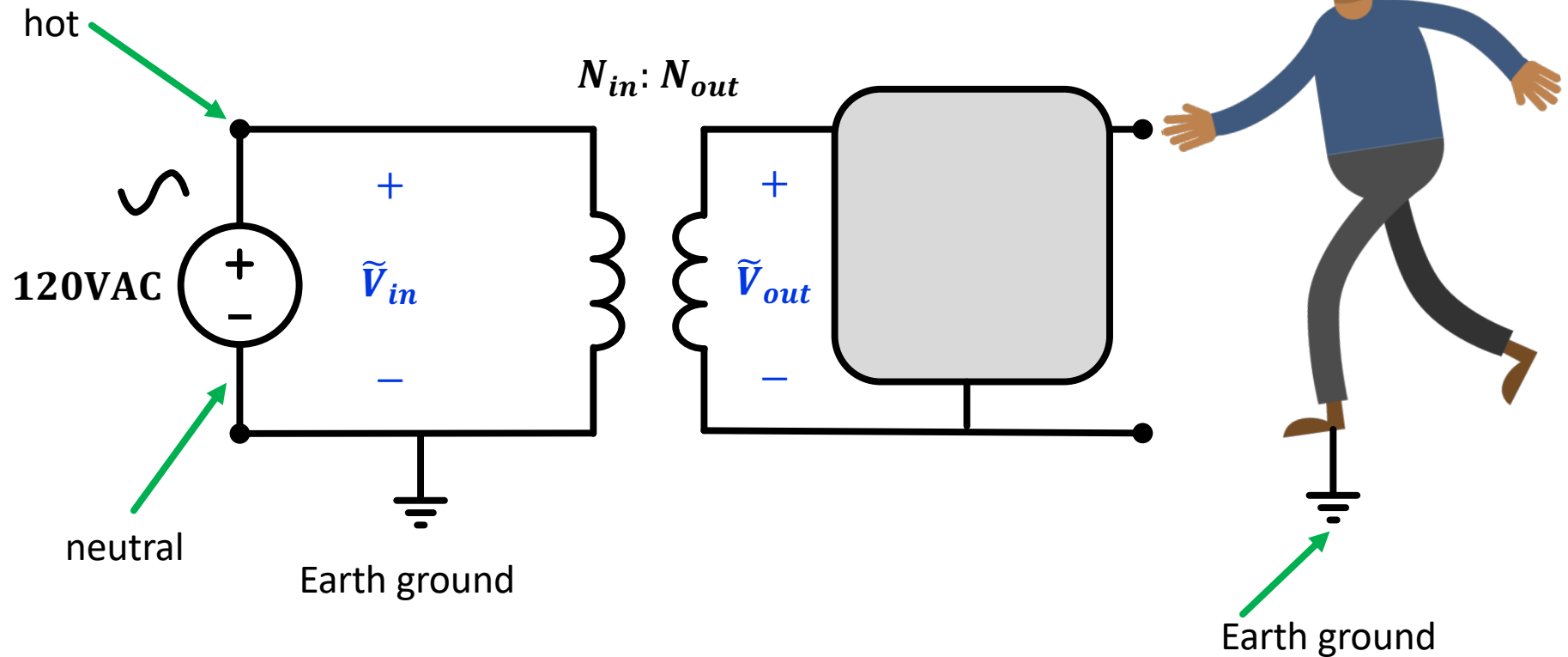
# Transformers: Isolation

- Transformers also provide electrical isolation




- If you close the circuit between hot and ground, no biggie...in your isolated circuit, your local ground is different!

# Interesting Issue

- I get a slight electrical tingle from my macbook when I touch the chassis and a grounded object
- That would suggest there must be some path or lack of isolation or something.
- But we're in the modern era and things are safe, correct?
- There's no more hot chassis(es)?

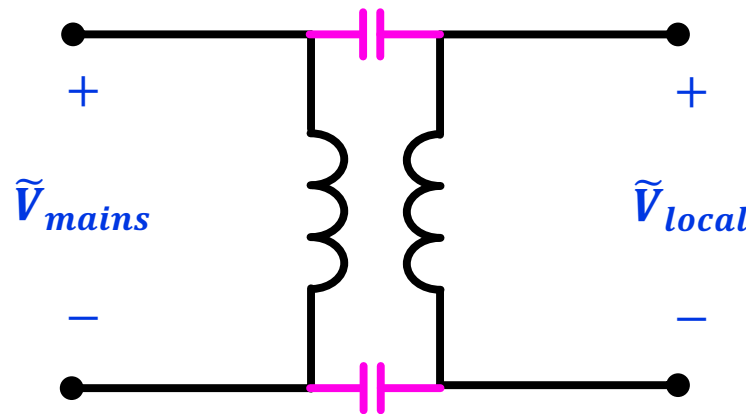
# Where the Leakage Comes From

- Modern power supplies run at very high frequencies (100's of kHz).
- Doing so lets the transformers be much smaller so you save on iron (and other benefits too)
- They do have full “official<sup>TM</sup>” isolation via some transformers, but these types of transformers will have parasitic capacitance between the two windings



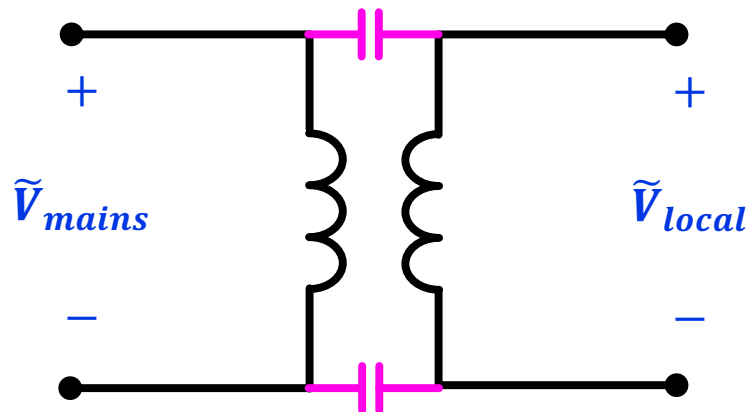
# Where the Leakage Comes From

- This parasitic Capacitance is small, but because of its presence and involvement with the inductances of the coils of the transformer you can get some oscillatory action.
- Since  $C$  is small that means the frequency the caps and coils like to oscillate at together will be large:
- This high frequency behavior can get everywhere  $f = \frac{1}{2\pi\sqrt{LC}}$  and cause noise




# Solution: The Y Capacitor

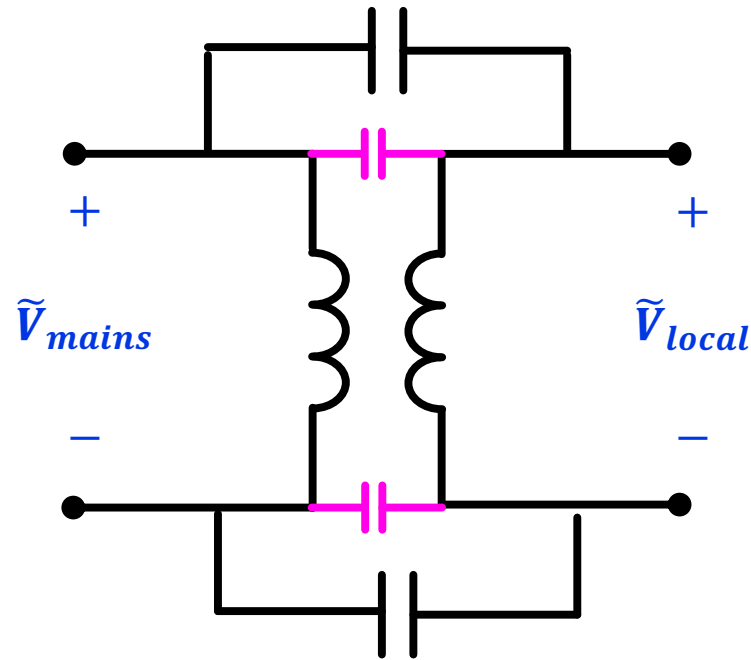

- Put much larger capacitors (nF) in parallel with transformer
- This C adds (in parallel) with parasitic C, making total C much larger...brings the resonant frequency down  $f = \frac{1}{2\pi\sqrt{LC}}$



Issue:

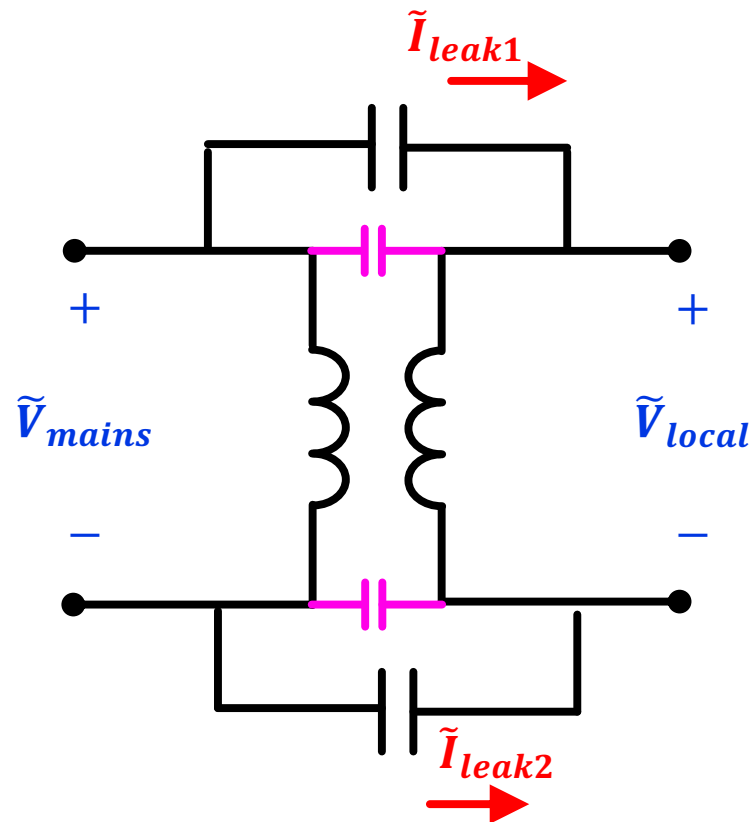


- Bigger capacitors have lower impedances  $Z_c = \frac{1}{j\omega C}$
- So now there is a bigger non-isolation path between the “isolated” side and the mains

# Issue:

- And this means there is the possibility for leakage current to occur if the polarity of an AC plug is flipped and someone touches earth ground
- Thankfully, this is highly regulated. Can't be more than about 50  $\mu\text{A}$  of current
- The Y capacitors must be very good (very high safety rating to avoid failure/shorting).
- But there is some leakage there.
- So my macbook isn't a hot chassis...more like a warm chassis.
- Good discussion:
  - <https://electronics.stackexchange.com/questions/216959/what-does-the-y-capacitor-in-a-smps-do>

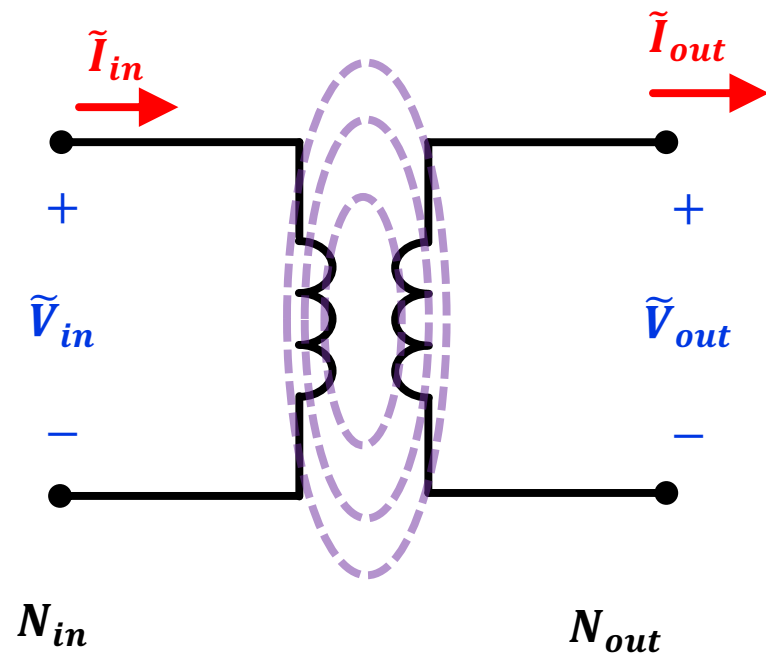
# The Transformer

- OK, so what can we use the transformer for? We can't amplify
- Several big uses:
  - Power conversion
  - Electrical Isolation
  - Impedance Matching
  - **Coupling Stages**
  - Phase Inversion


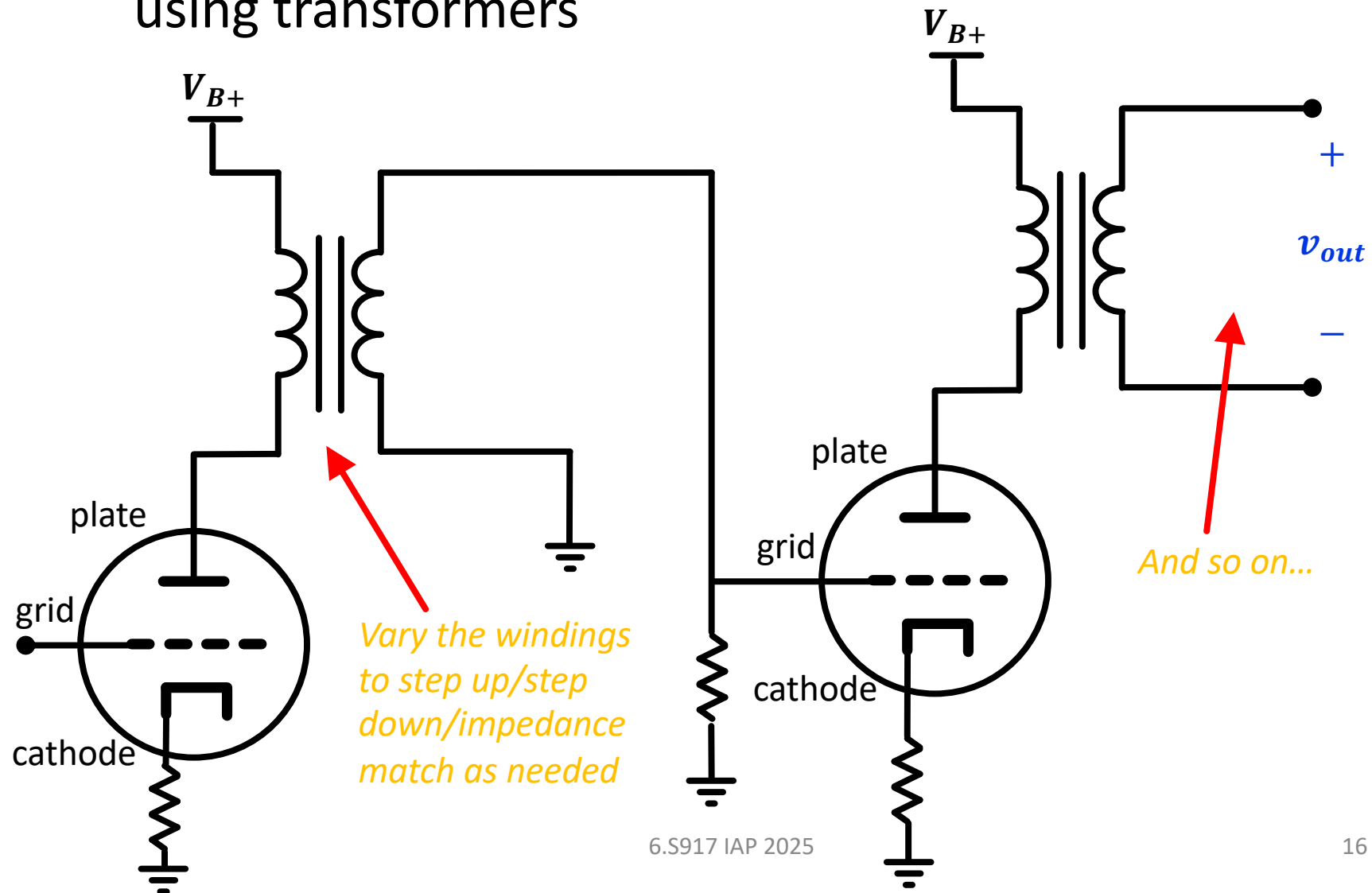
# Linking Tubes (Coupling)

- Many early tube circuits that had more than one tube would “couple” one stage of circuit to the next using transformers




# Transformer Coupling

- A triode with a transformer output could kinda create a system with:
  - High input impedance
  - Low(er-ish) output impedance
    - (which is exactly what we want from Op amps for example)
- Expensive and with time disappeared from all but the most important stages (replace with resistive or capacitive coupling)

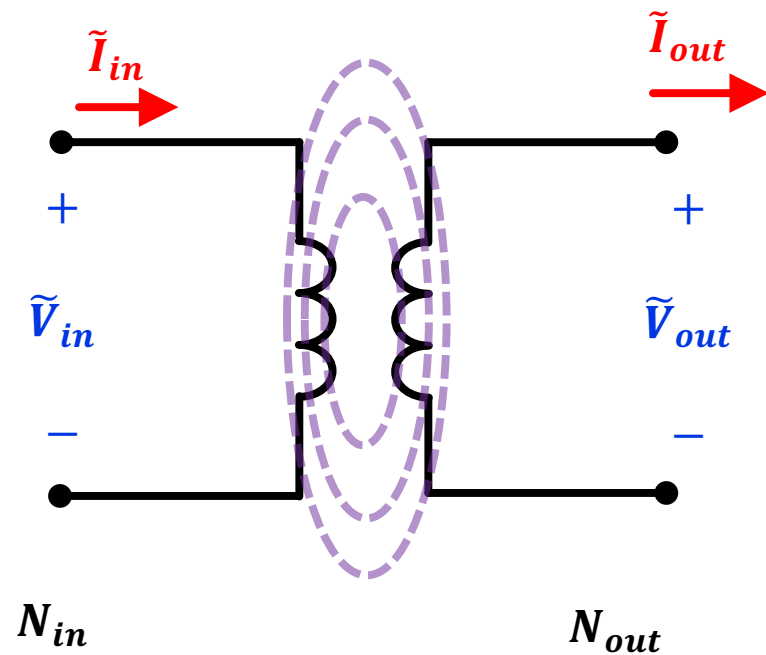
# The Transformer

- OK, so what can we use the transformer for? We can't amplify
- Several big uses:
  - Power conversion
  - Electrical Isolation
  - **Impedance Matching**
  - Coupling Stages
  - Phase Inversion


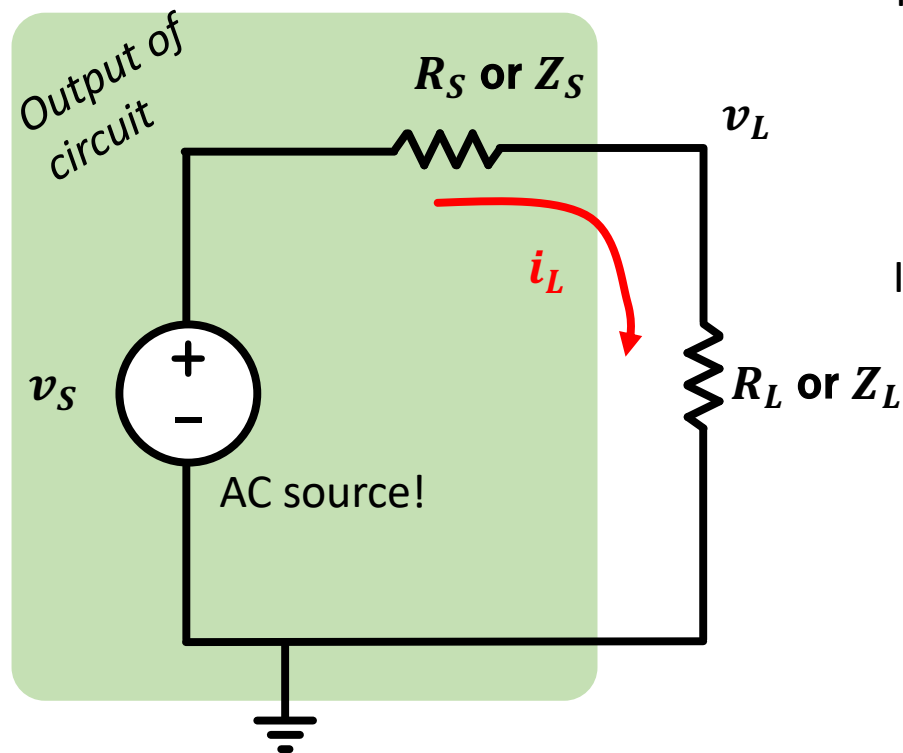
# Transformers: Impedance Matching

- We can always model the exchange of information and energy from one portion of a circuit to another with a Thevenin circuit driving a load:



If concerned about passing voltage onto load:  
focus on  $R_L > R_S$  and ideally  $R_L \gg R_S$

If concerned about passing max power into load:  
focus on trying to get as close as possible to  $Z_L = Z_S^*$

# Transformers: Impedance Matching

- We can always model the exchange of information and energy from one portion of a circuit to another with a Thevenin circuit driving a load:

Like before:  $\frac{V_{out}}{V_{in}} = \frac{N_{out}}{N_{in}}$


$$V_{in} \cdot I_{in} = V_{out} \cdot I_{out} \quad \therefore \frac{I_{out}}{I_{in}} = \frac{N_{in}}{N_{out}}$$

But now:  $I_{out} = \frac{V_{out}}{R_L}$

Therefore:  $I_{in} = I_{out} \frac{N_{out}}{N_{in}} = \frac{V_{out}}{R_L} \frac{N_{out}}{N_{in}}$

Or rewrite as:
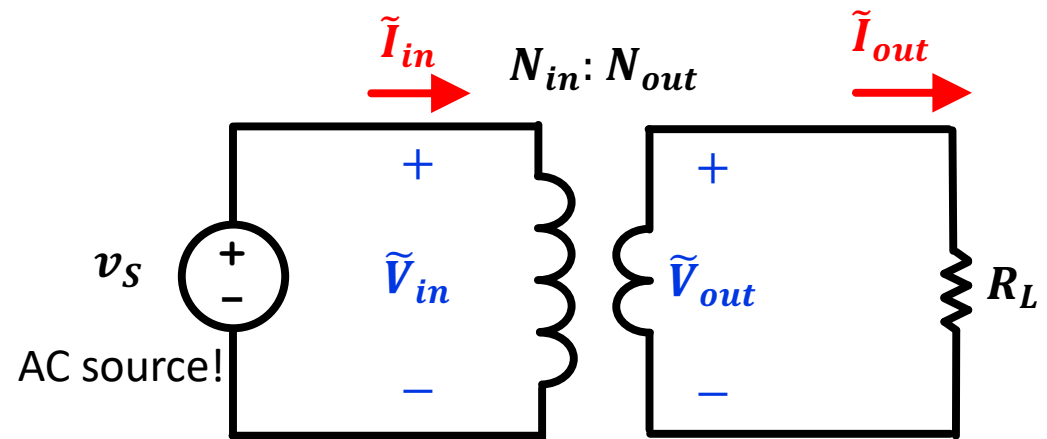
$$I_{in} = \frac{\frac{N_{out}}{N_{in}} V_{in}}{R_L} \frac{N_{out}}{N_{in}}$$




We could define  $R_{in} = \frac{V_{in}}{I_{in}}$ :

So therefore:  $R_{in} = R_L \left( \frac{N_{in}}{N_{out}} \right)^2$


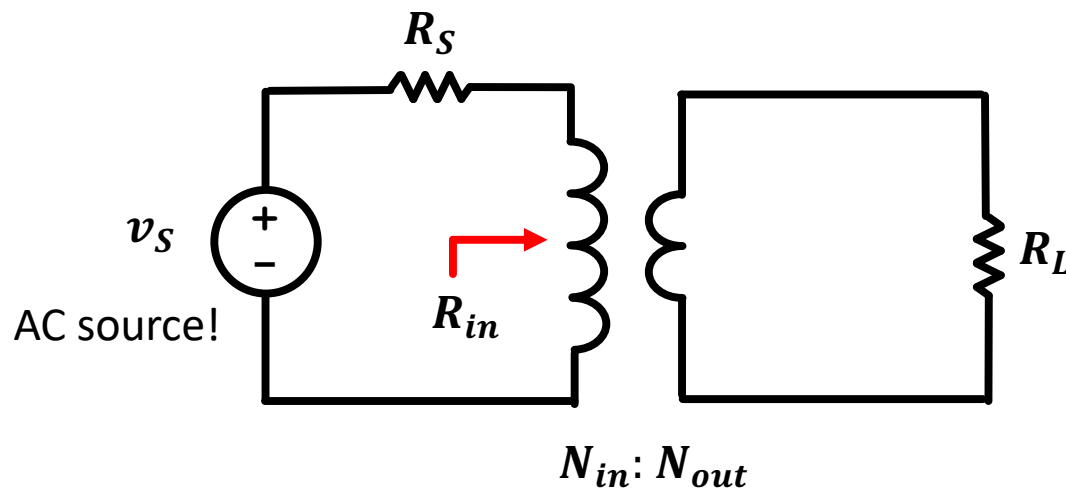
# Transformers: Impedance Matching

- A transformer can change how a particular load “looks” to a source:



$$R_{in} = R_L \left( \frac{N_{in}}{N_{out}} \right)^2$$


Works more generally for impedance too:

$$Z_{in} = Z_L \left( \frac{N_{in}}{N_{out}} \right)^2$$

- Is  $R_L$  too low (like might be the case in a speaker)? Use a step-down transformer to increase the resistance
- Is  $R_S$  too high (like is sometimes the case in an antenna)? Use a step-up transformer to decrease the resistance

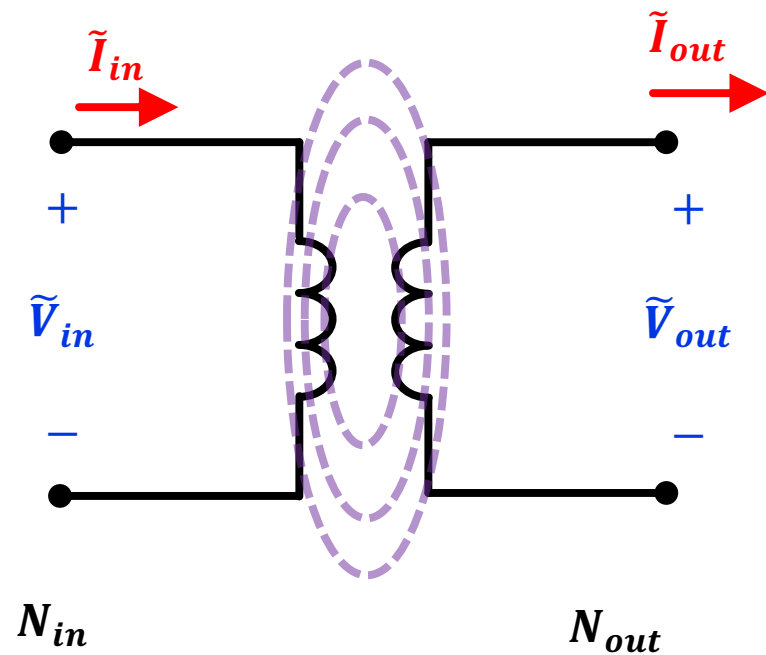
# The Transformer

- OK, so what can we use the transformer for? We can't amplify
- Several big uses:
  - Power conversion
  - Electrical Isolation
  - Impedance Matching
  - Coupling Stages
  - **Phase Inversion**


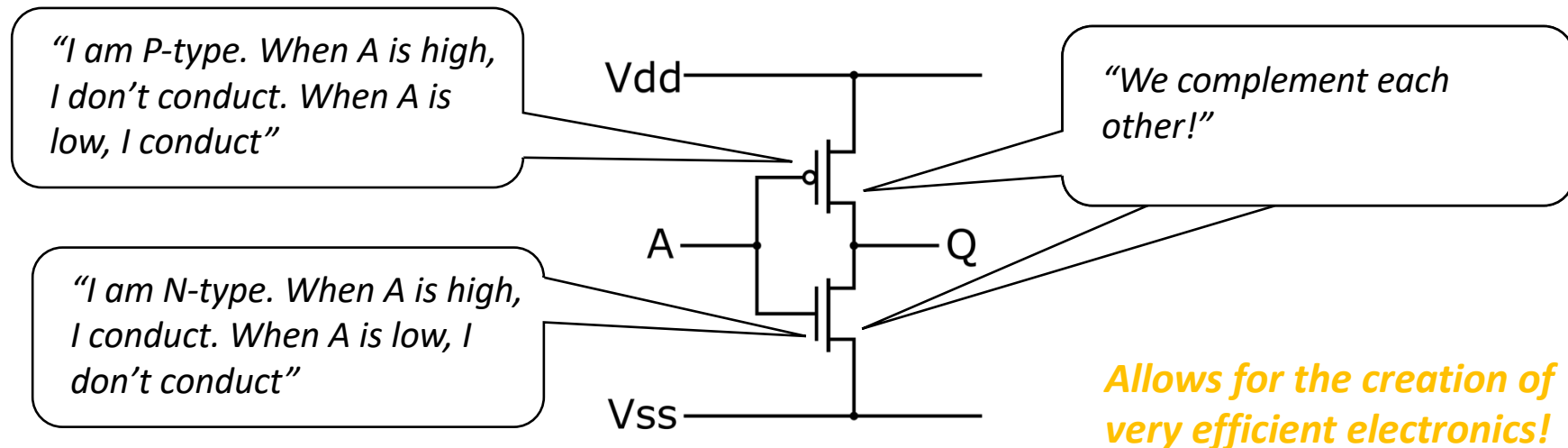
# Problem: Tubes only have one “type”

- In the future (>1950s) we'll have N-type and P-type devices, working off of electron and hole charge carriers, respectively
- Allows us to develop amplifiers that work in complementary fashion
- Consider a CMOS inverter for example



# Tubes only have one “type”


- Tubes only work off of electrons as carrier
- No “P-type” tube

*“I am P-type. When A is high, I don’t conduct. When A is low, I conduct”*

Missing




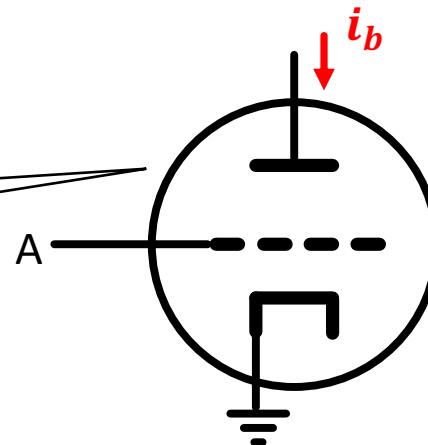*“I am N-type. When A is high, I conduct. When A is low, I don’t conduct”*



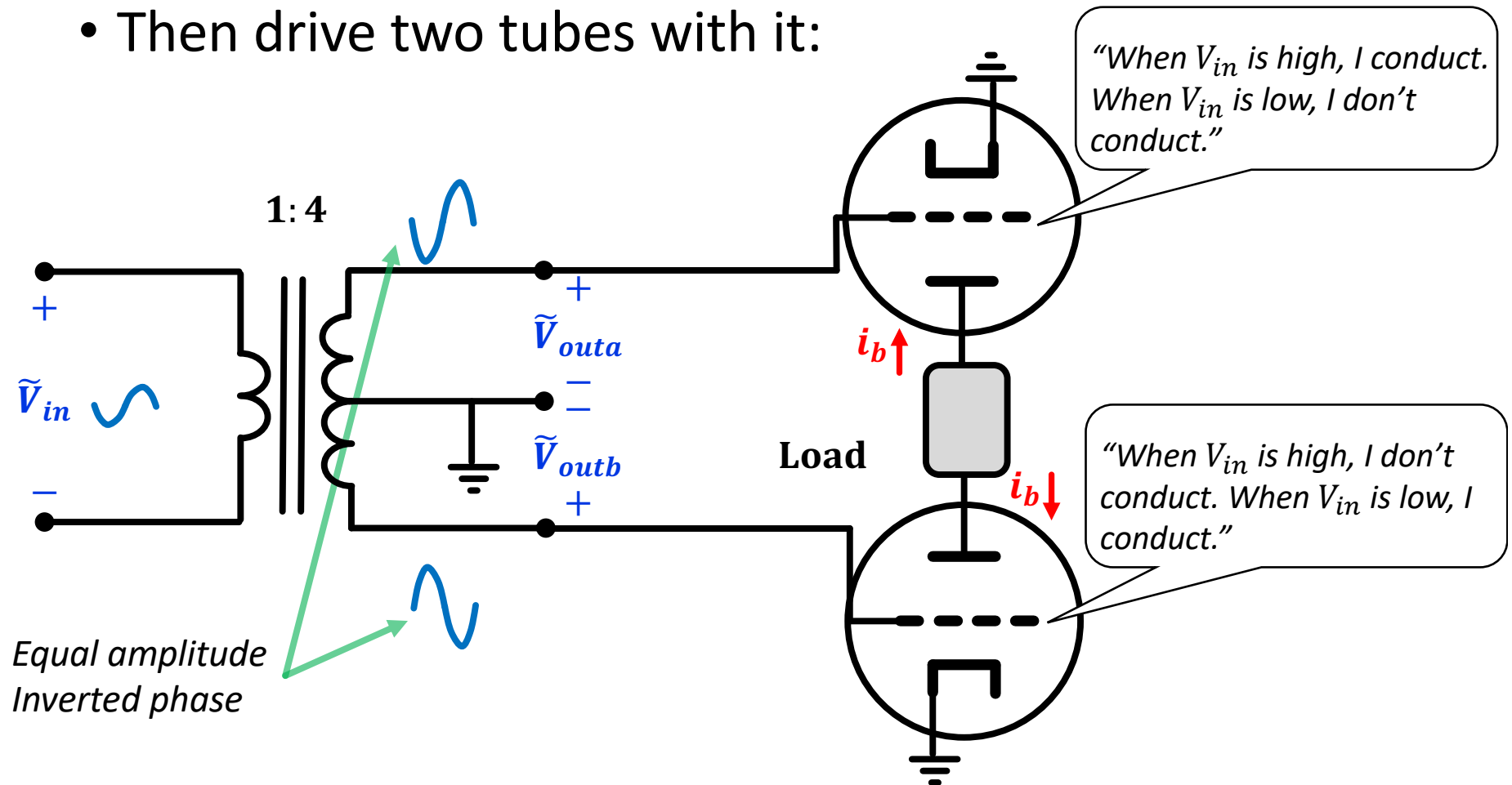
# Solution: Use a Transformer

- Use a Center-tap to Ground to create two completely out-of-phase signals from input signal.
- Then drive two tubes with it:




# 1928 Bosch Radio Receiver Schematic

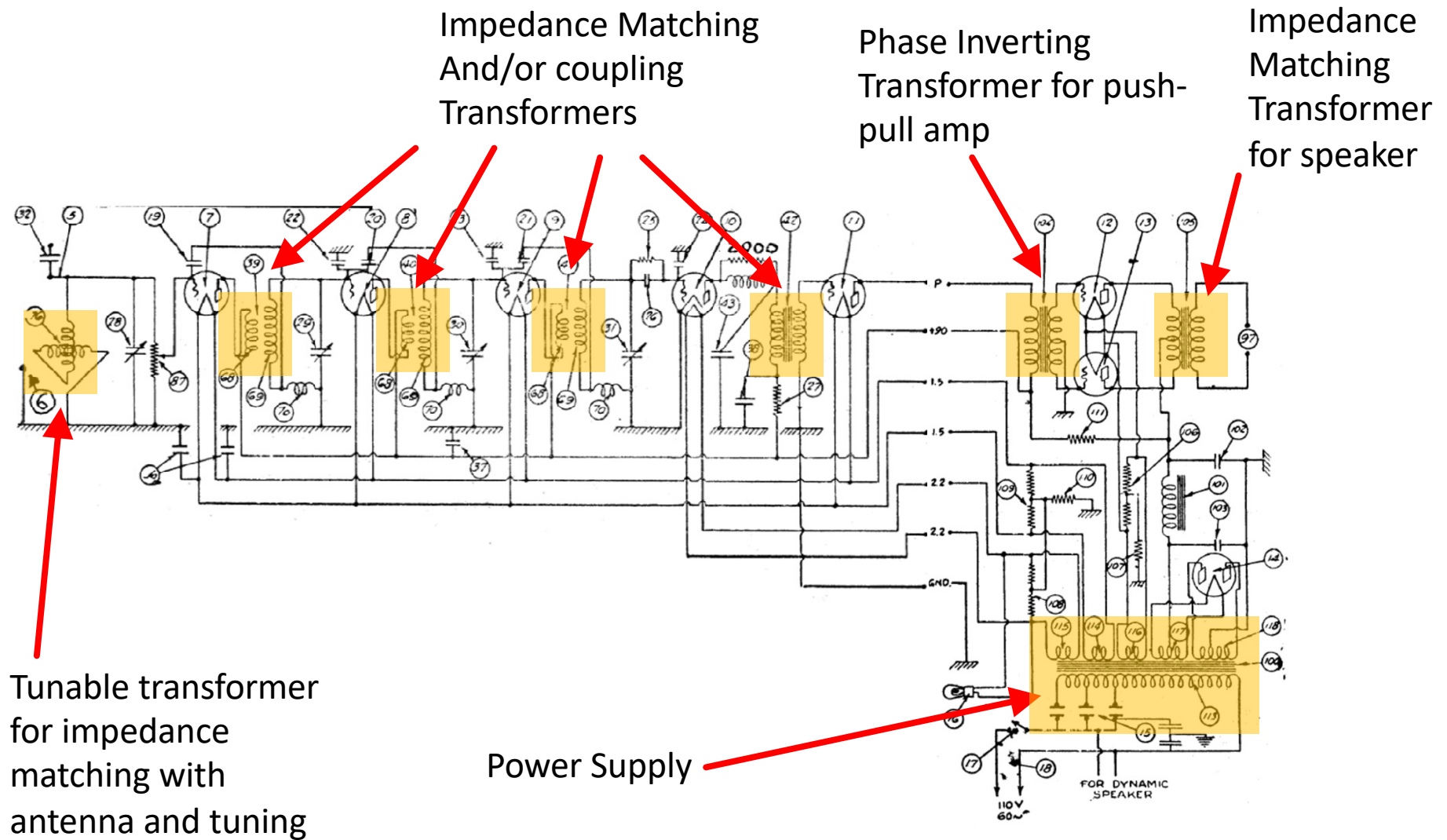

# Designing with Tubes

# Lab 4

- Make an Audio Amplifier!

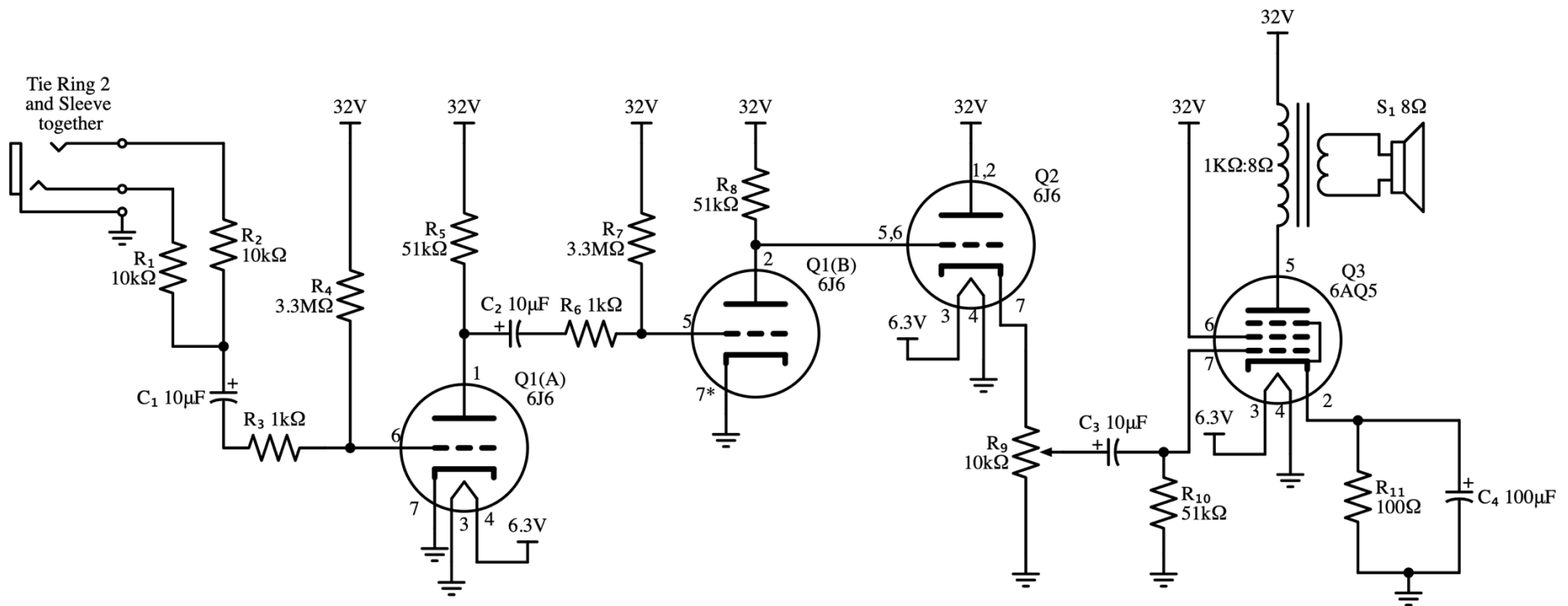





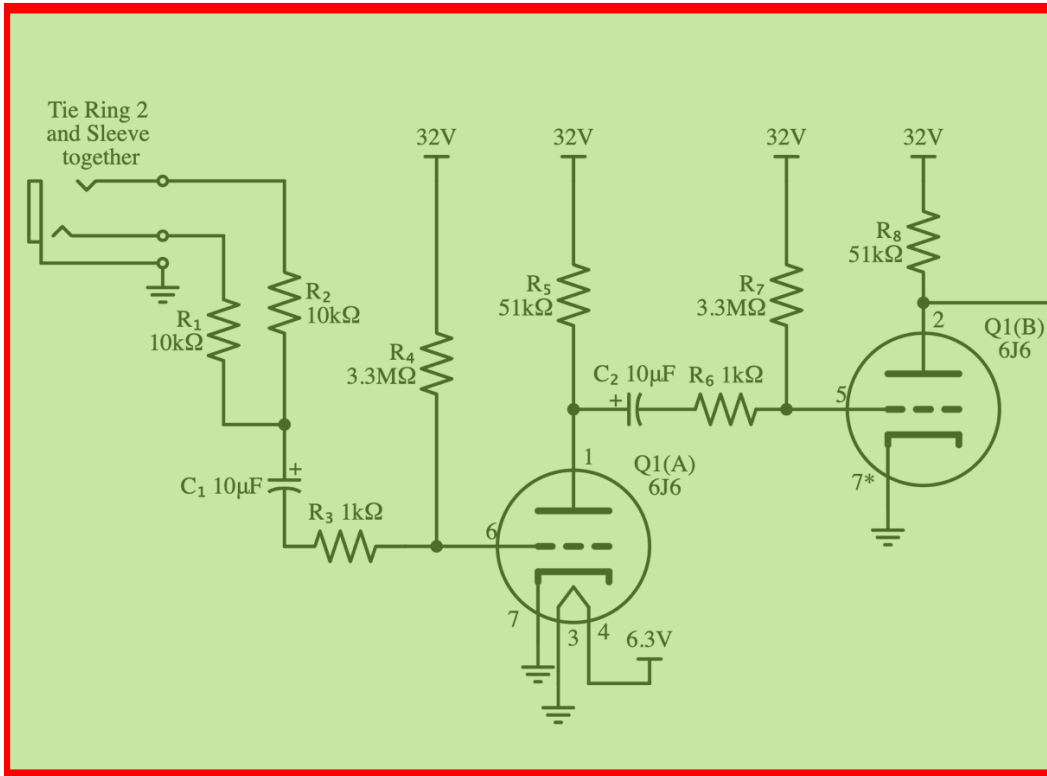
# Lab 4

- Make an Audio Amplifier!

*Buffer stage  
(link preamp to  
power amp)*



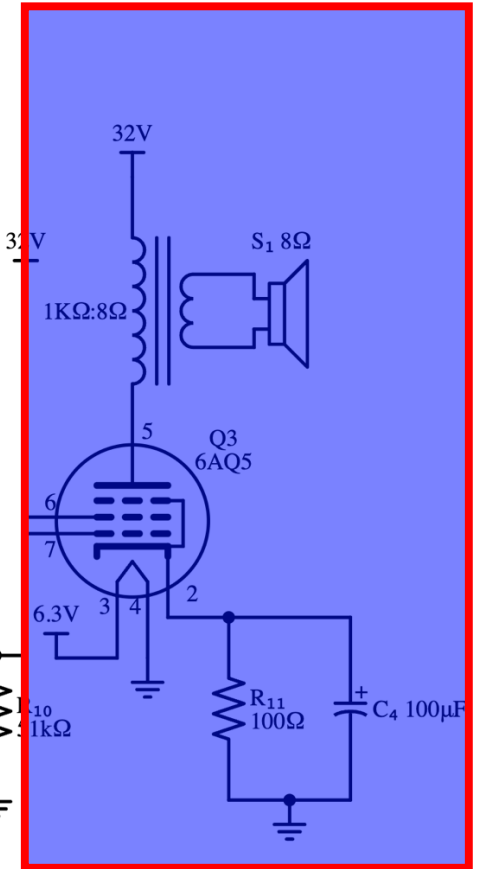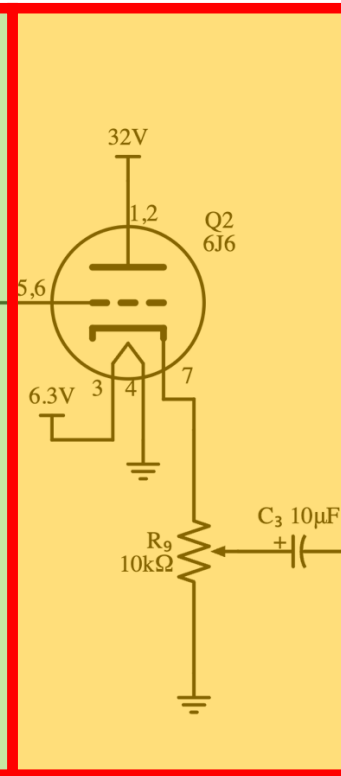
*Preamplifier (largely concerned with  
increasing voltage of signal)*



*Power Amplifier (largely  
concerned with moving as  
much energy into the load as  
possible)*


# Basic Triode Setup

- Our Basic Triode setup:

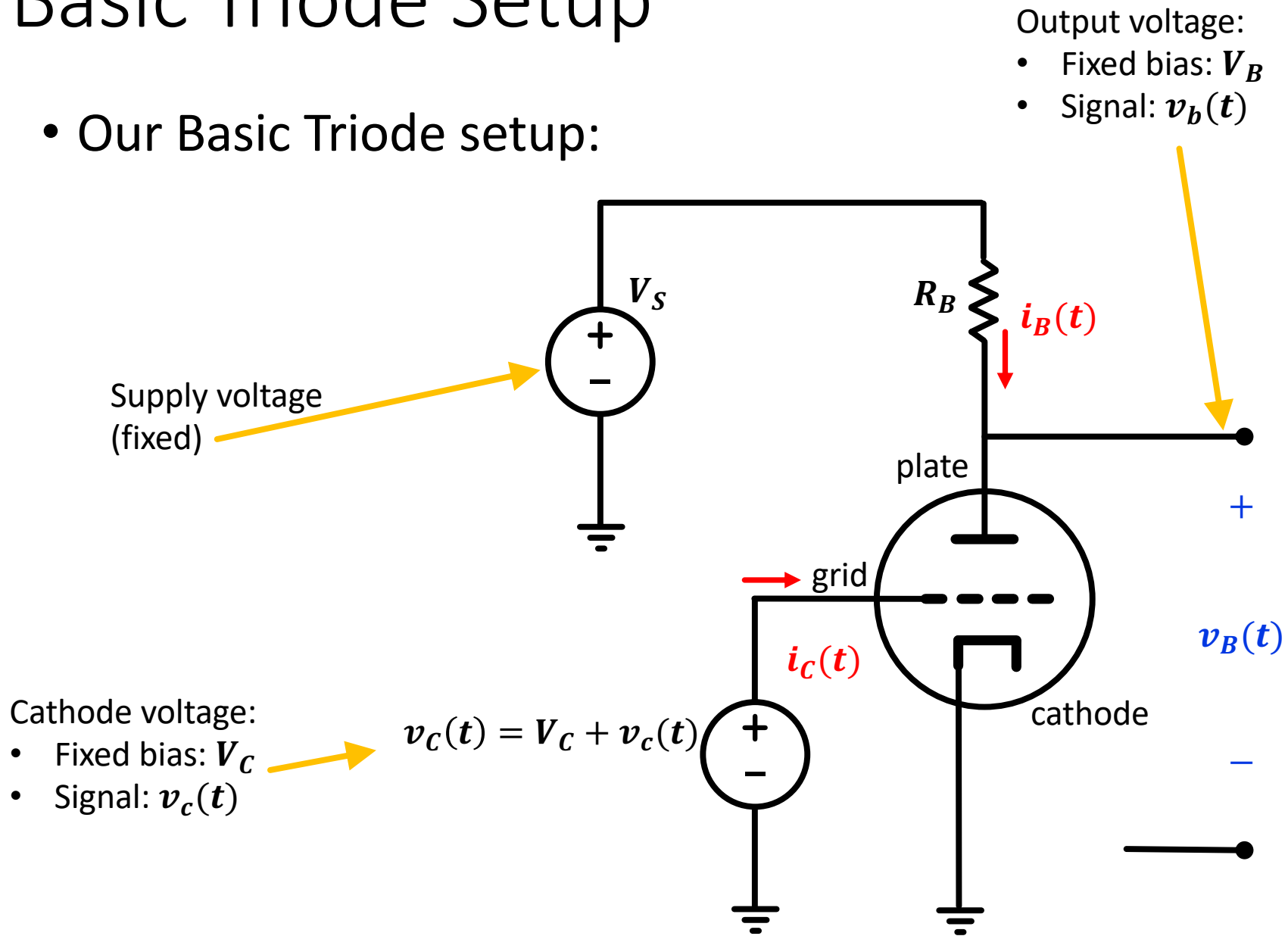

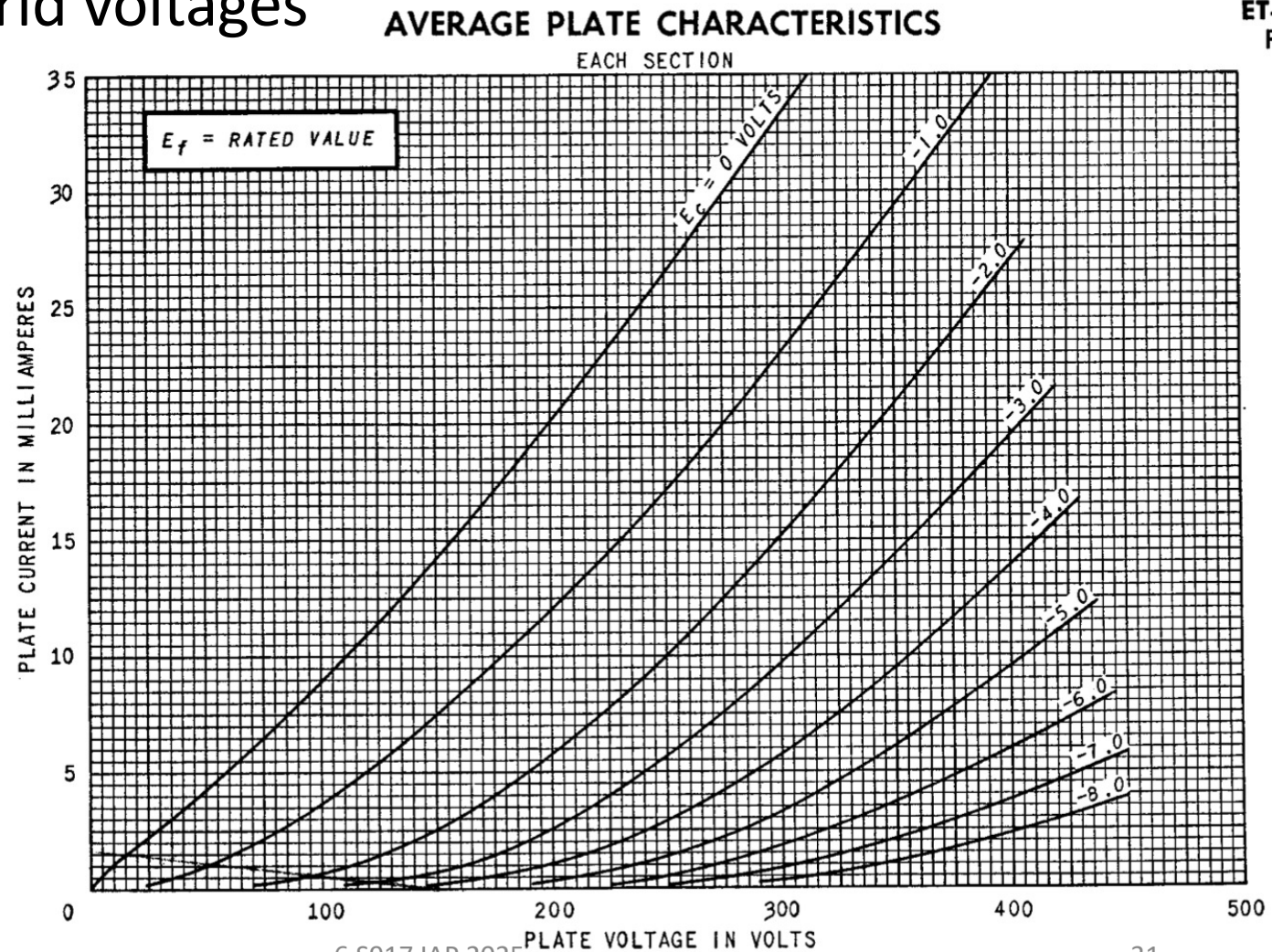
# 12AT7 Curve #1

- Plate current as a function of plate voltage for specific grid voltages


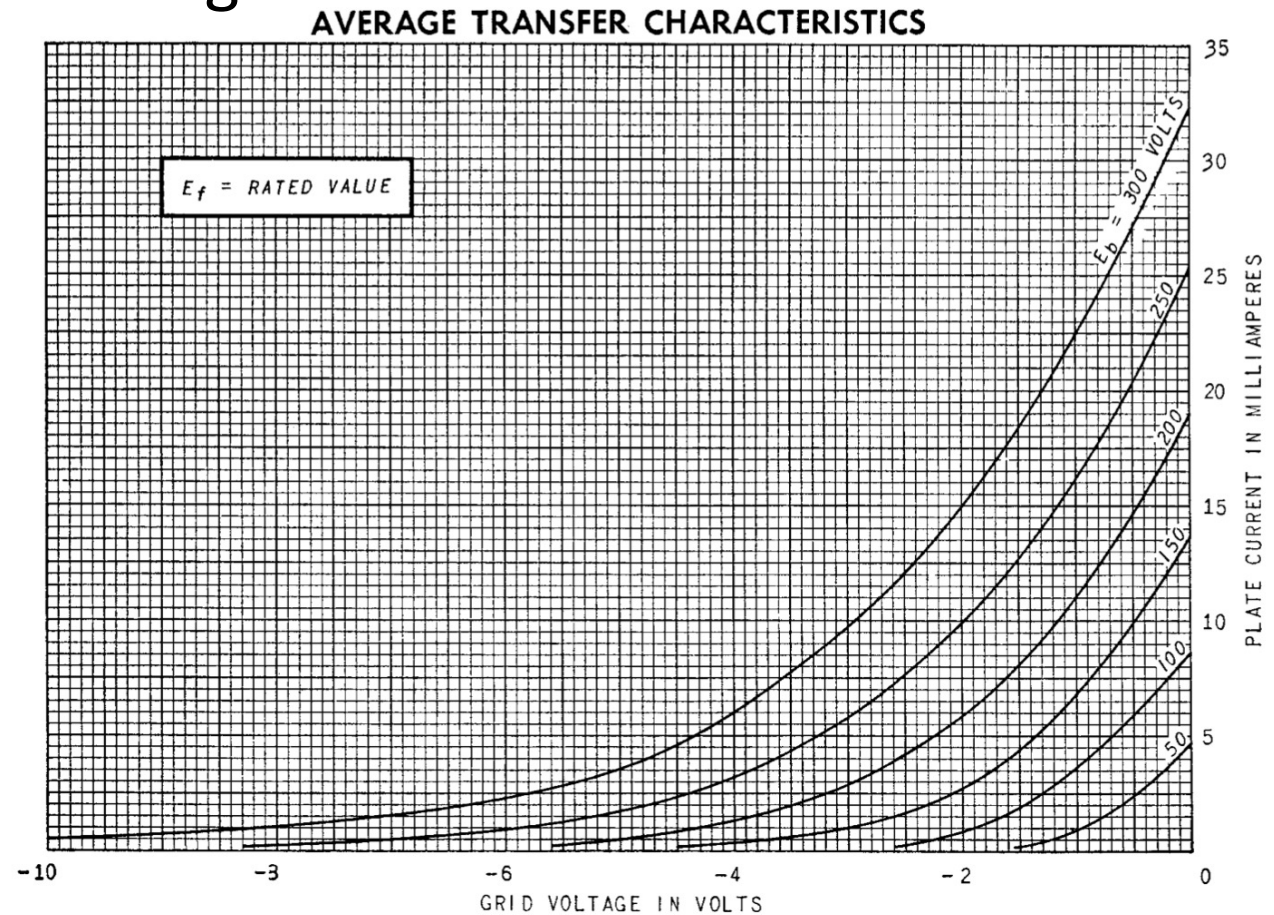
# 12AT7 Curve #2

- Plate current as a function of grid voltage for specific plate voltages




# All together

- The two plots are slices across two of the three axes
- The general rough pattern is


$$I_B = P \left( V_C + \frac{V_B}{\mu} \right)^{3/2}$$

*Whole mess of  
physical constants*

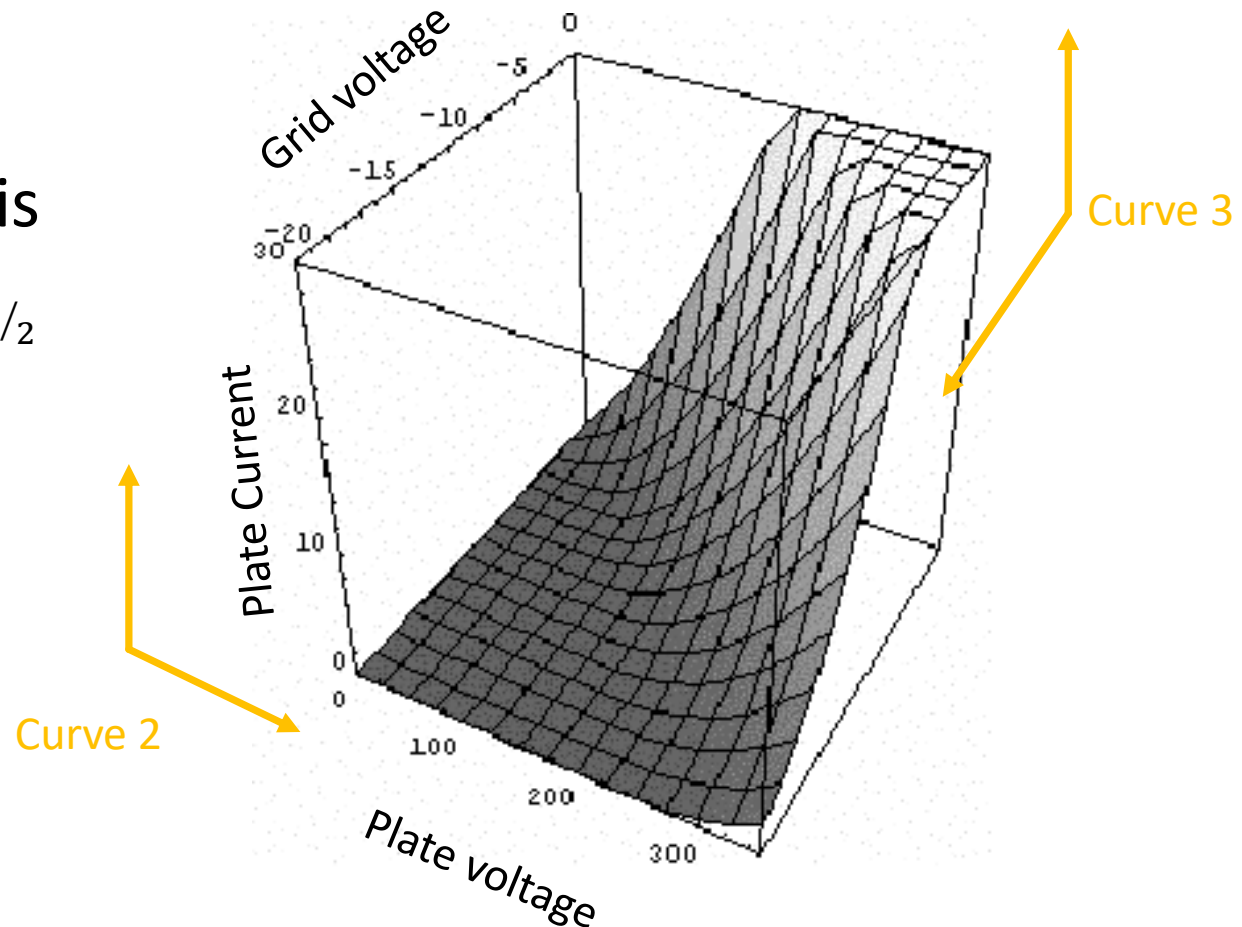

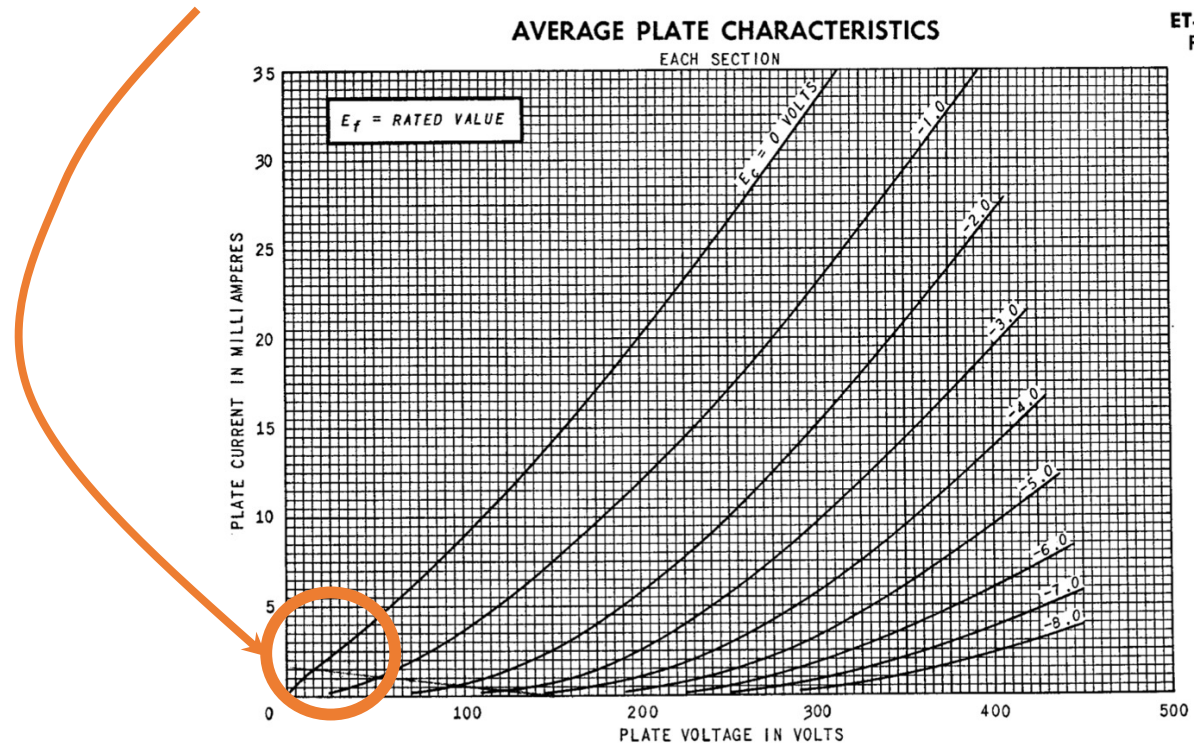
# Problem with these plots...

- They're all way too zoomed out.
- We'll be running our tubes in "starvation" mode in this class for safety ( $V_B \leq 50V$ )


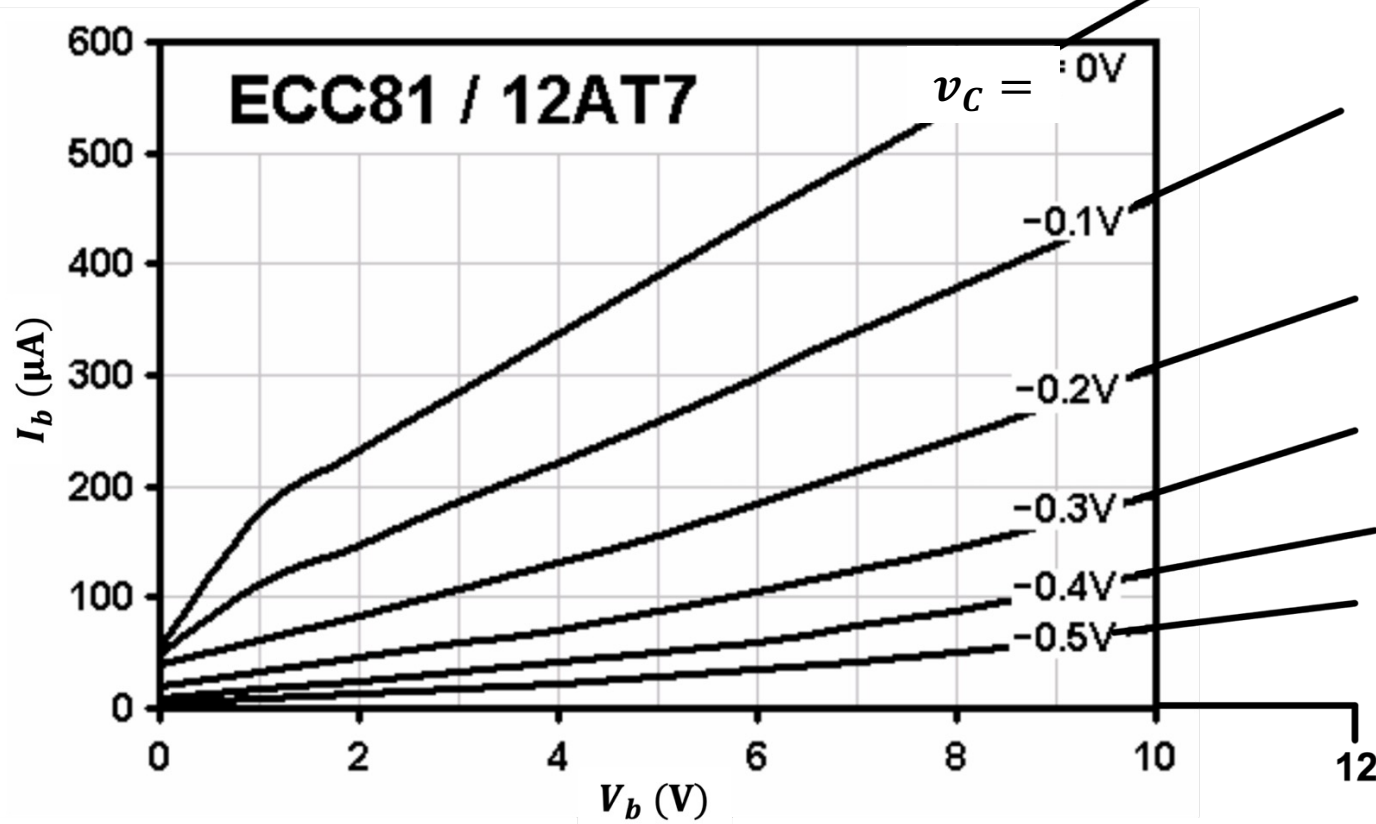
# Thankfully Zoomed-in Plots exist

- We're not the first to starve our tubes




Taken and slightly extrapolated from here: [http://www.valvewizard.co.uk/Triodes\\_at\\_low\\_voltages\\_Blencowe.pdf](http://www.valvewizard.co.uk/Triodes_at_low_voltages_Blencowe.pdf)



# OK So How Do We Use that Plot?

- Our Basic Triode setup:

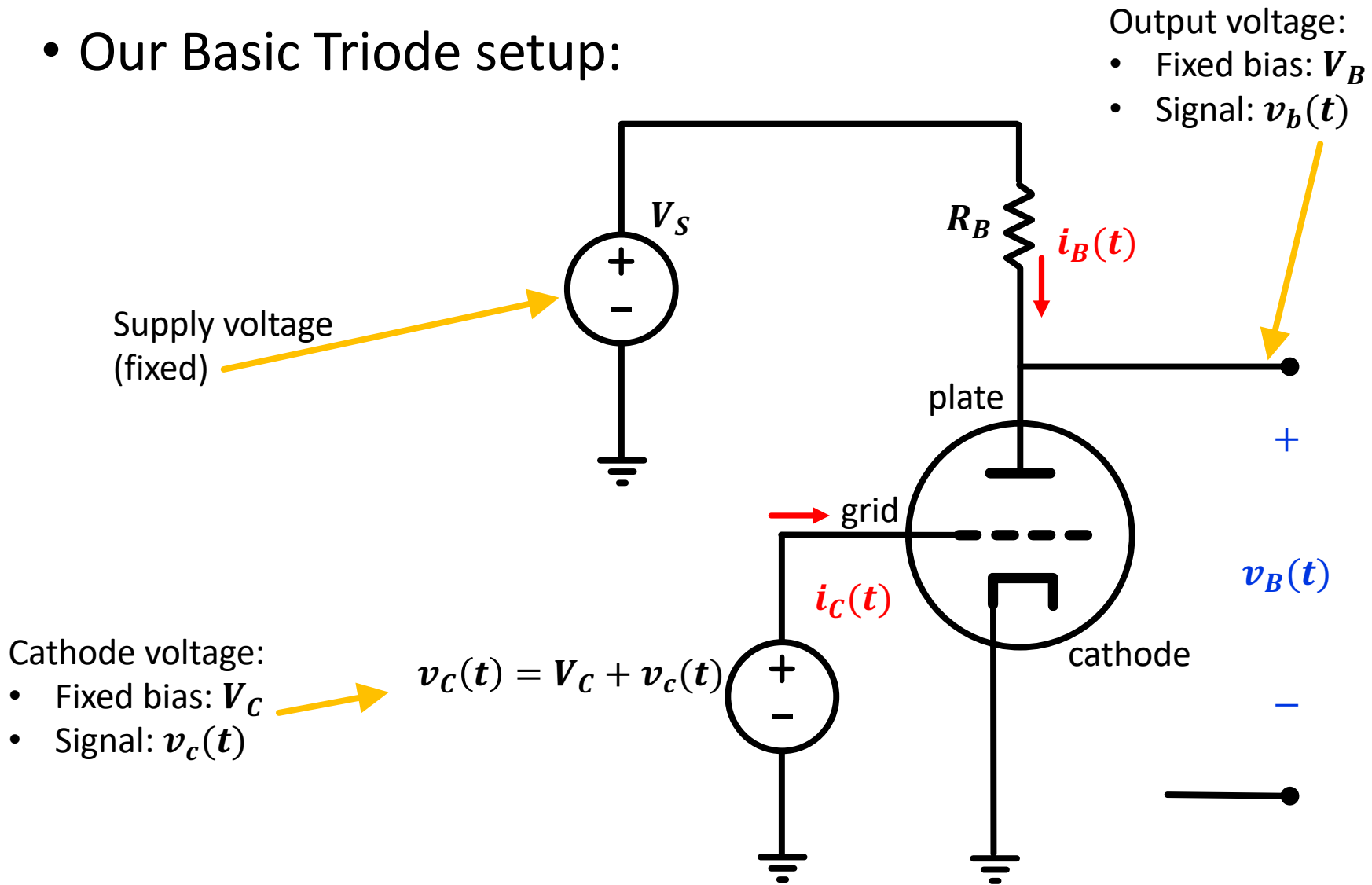




# We need to find out where to bias the tube

- Biasing a device is “positioning” it electrically speaking so that it will respond from that point to incoming signals
- Where we position it will affect things like its:
  - Gain
  - Frequency response
  - Input and output impedances
- It is a complicated choice to make so you have to be comfortable just rolling with things and assuming you might have to change it.

# To Start We pick an $R_B$


- What value? I don't know. I give up.
- It comes with practice/time/experience. Let's pick two different values and see how they will “land” on the I-V characteristics:
  - 24Kohm
  - 47Kohm
  - 240 Kohm

# Remember the Load Line!

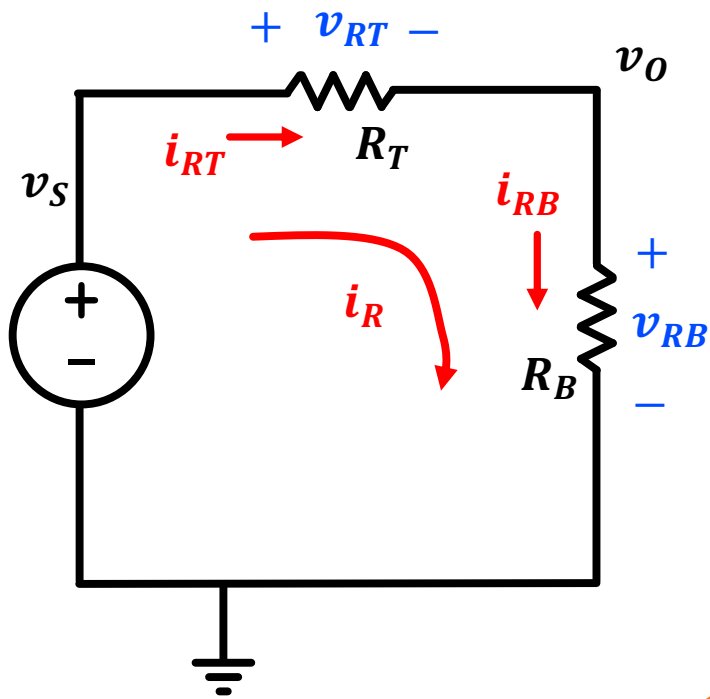


What  $i_R$  would be if  $v_O=0$   
according to  $R_B$  (answer: 0)

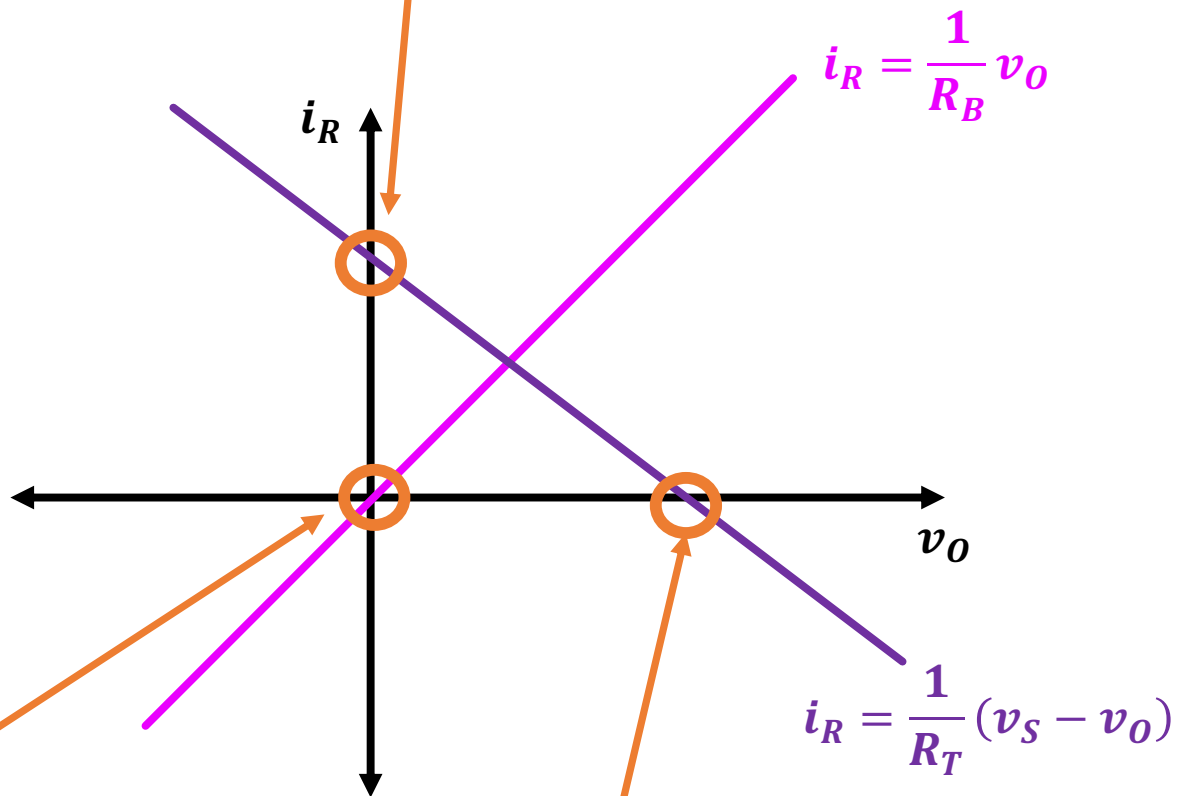What  $i_R$  would be if  $v_O=0$   
according to  $R_T$  (answer:  $\frac{v_S}{R_T}$ )



What  $v_O$  would be if  $i_R=0$   
according to  $R_T$  (answer:  $v_S$ )

Applying that here:

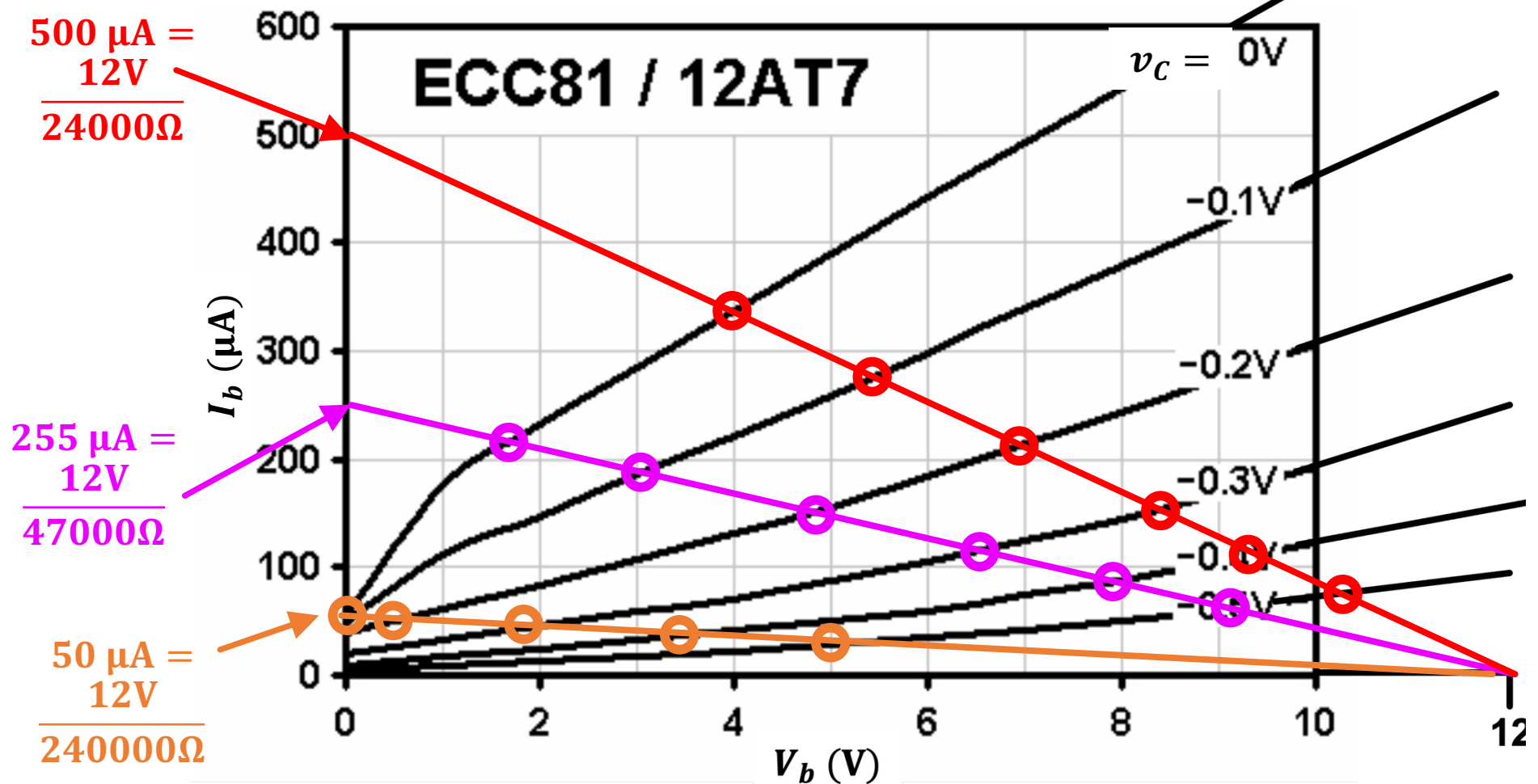


Taken and slightly extrapolated from here: [http://www.valvewizard.co.uk/Triodes\\_at\\_low\\_voltages\\_Blencowe.pdf](http://www.valvewizard.co.uk/Triodes_at_low_voltages_Blencowe.pdf)
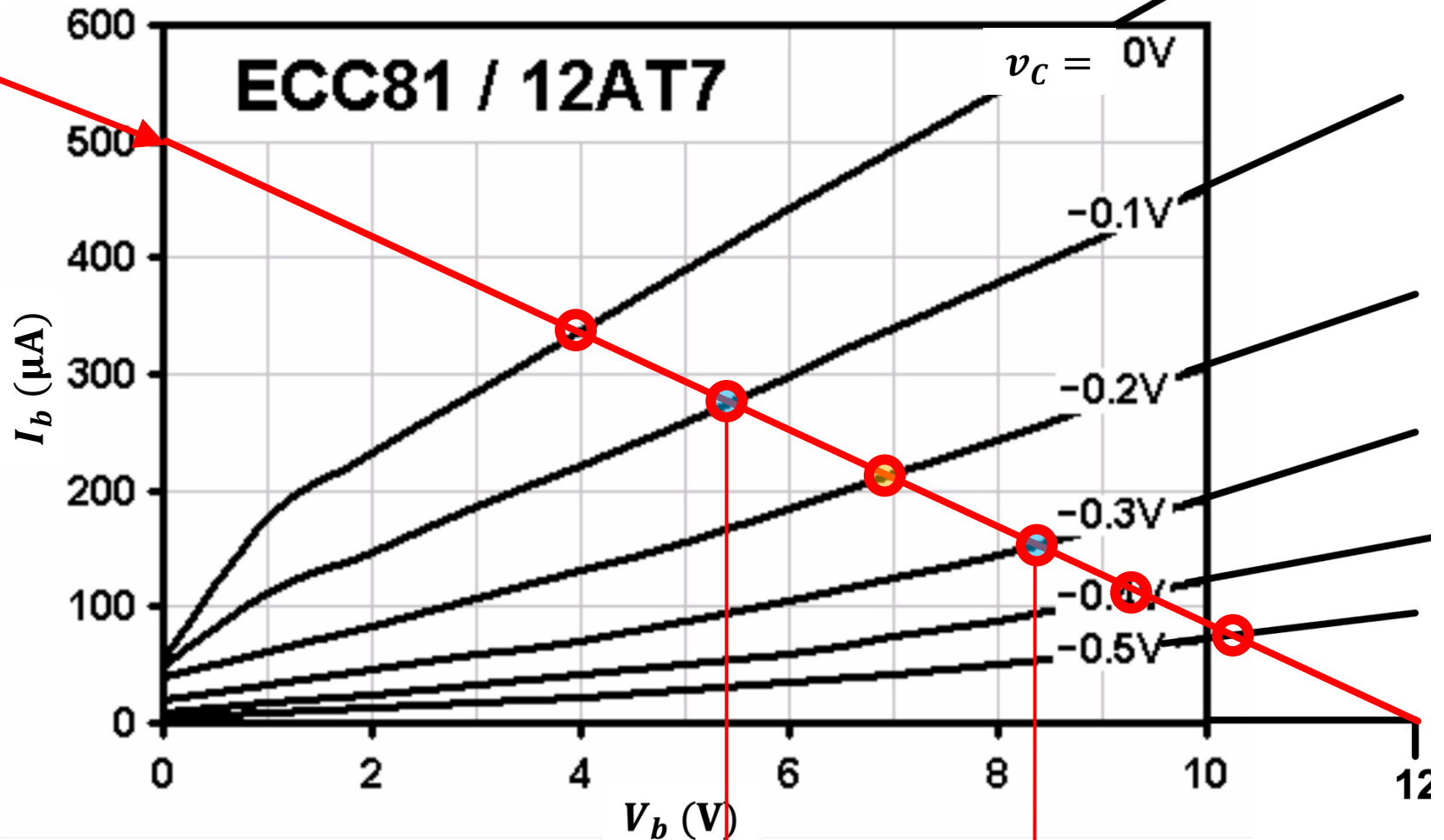
# The next step is to pick an operating point


- This is a “Solution” on each load line that you want to analyze around
- Eventually we would bias the triode to sit there when no signal is present, and any signal coming in would deviate from that point, moving you up and down the load line
- We could then analyze how the output would look

$$500 \mu\text{A} = \frac{12\text{V}}{24000\Omega}$$




$$A_v = \frac{\Delta V_b}{\Delta V_c} = \frac{8.25\text{V} - 5.25\text{V}}{-0.3\text{V} - -0.1\text{V}} = -15$$
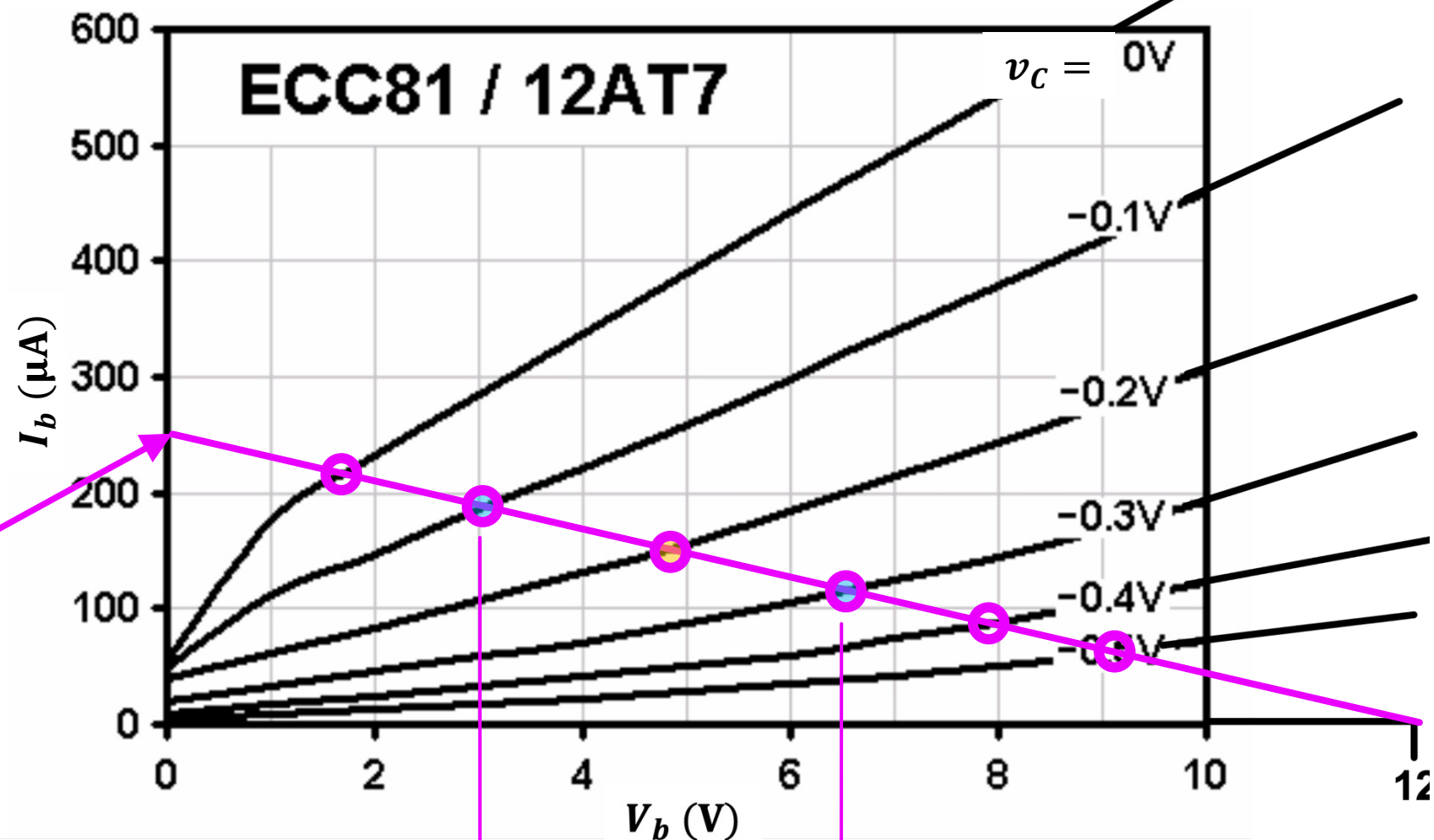
$$255 \mu\text{A} = \frac{12\text{V}}{47000\Omega}$$


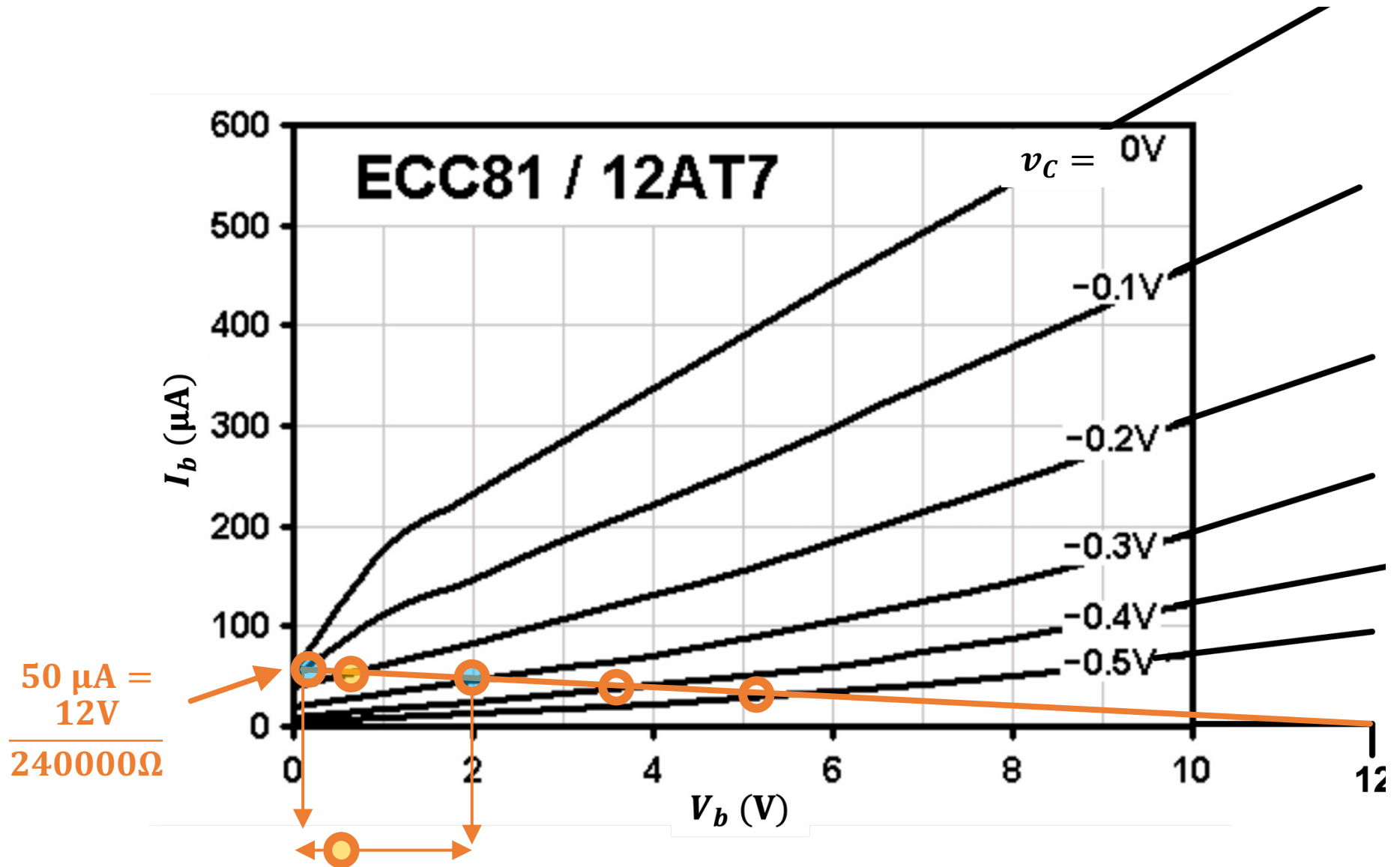
$$A_v = \frac{\Delta V_b}{\Delta V_C} \frac{6.5\text{V} - 3\text{V}}{-0.3\text{V} - -0.1\text{V}} = -17.5$$



$$A_v = \frac{\Delta V_b}{\Delta V_c} = \frac{2\text{V} - 0\text{V}}{-0.3\text{V} - -0.1\text{V}} = -10$$



# For an Amplifier we Want:


- We want a good gain (small input wiggle makes large output wiggle)
- We want a symmetric, linear behavior (we want a clean sine wave in to make a clean sine wave out...not a smushed one)

# Results?

- The three different resistors have different behaviors when operating around a bias voltage of -0.2V on the grid:
  - 24K will oscillate back and forth symmetrically with gain of -15
  - 47K will oscillate back and forth symmetrically with gain of -17.5
  - 240K will oscillate back and forth asymmetrically with gain of -10
- Resistor #2 seemed to be the “best”...clean output...biggest gain. Others less asymmetric and/or less gain

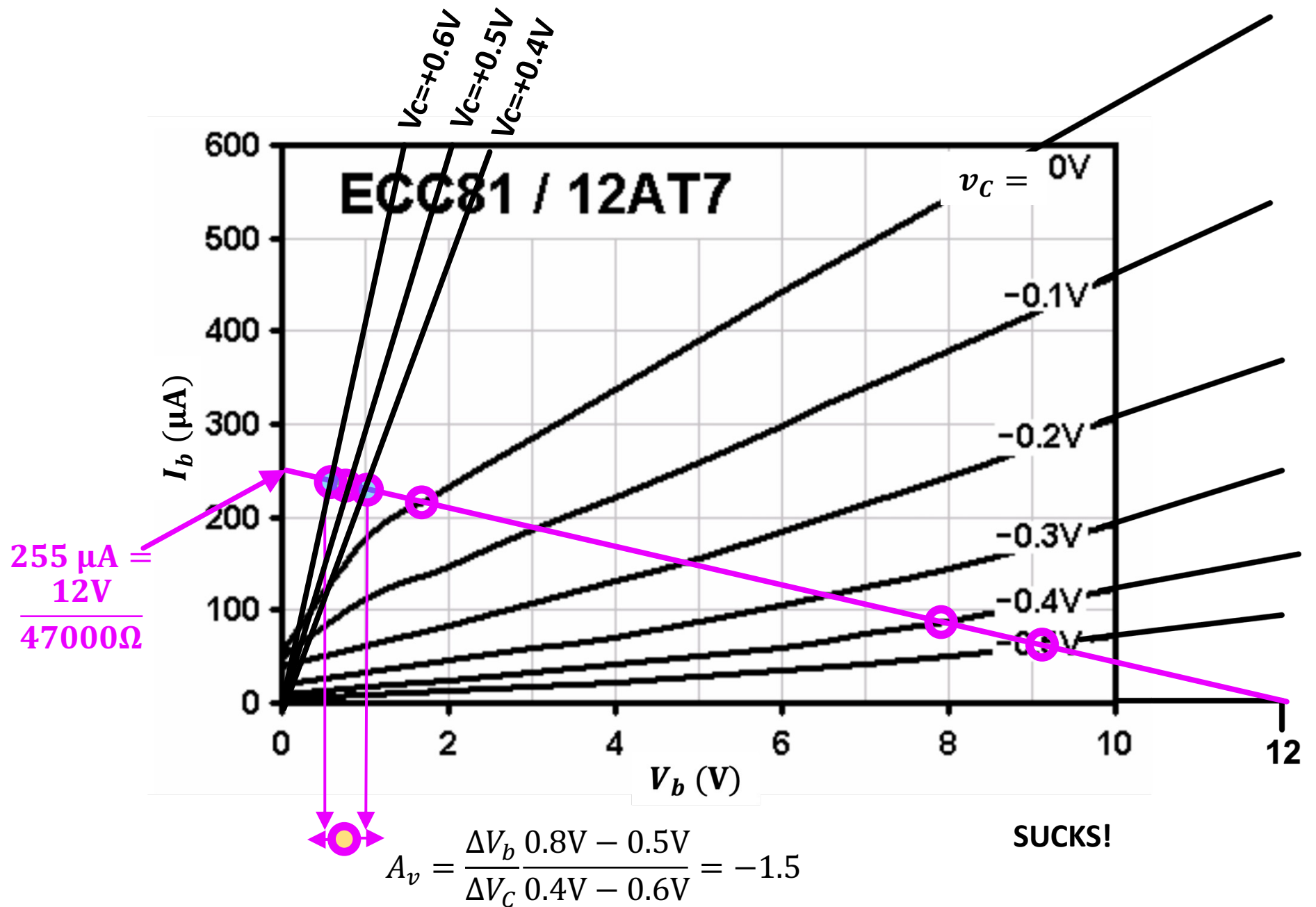
# Why Bias at $-0.2\text{V}$ for grid?

- Because that was a guess. We could choose others. And in combination with other resistors we will get other behaviors.
- What if we biased at  $+0.5\text{ V}$  on the grid instead and used that “winning”  $47\text{K}$  resistor?


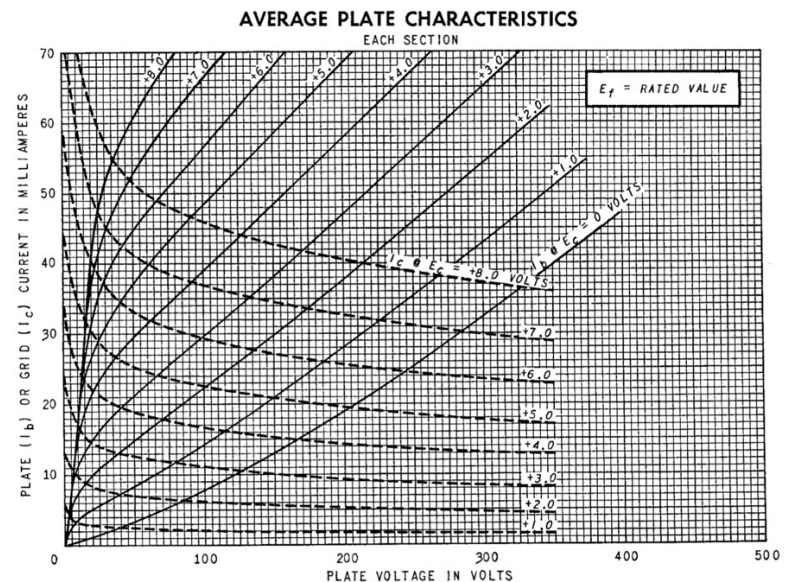
# Also Though...

- At positive grid voltages, current starts to flow into the grid (electrons escape to grid rather than plate...kinda makes sense)
- This is a huge problem for low-voltage tube circuits (and also higher ones too)



So you pick something...

- And you may need to go back and change it later. Design is iterative!
- But let's say for the first stage of our pre-amp we want to operate around a **grid bias of -0.2V**
- How \*DO\* we bias?

# Grid Leak or Cathode Bias


- We almost always want our Grid voltage to be negative compared to our cathode. You get this two ways:
  - Make cathode ground, make grid below ground
  - Make grid ground, make cathode above ground
- In both cases  $V_{grid} - V_{cat} < 0$  and we'll be in the good region of our I-V relationship

# Method 1: Cathode Bias

- Determine at rest what current will be going through cathode.
- Use that current to estimate a resistor needed below it to generate a voltage drop equivalent to the bias we want.



# Method 1: Cathode Bias

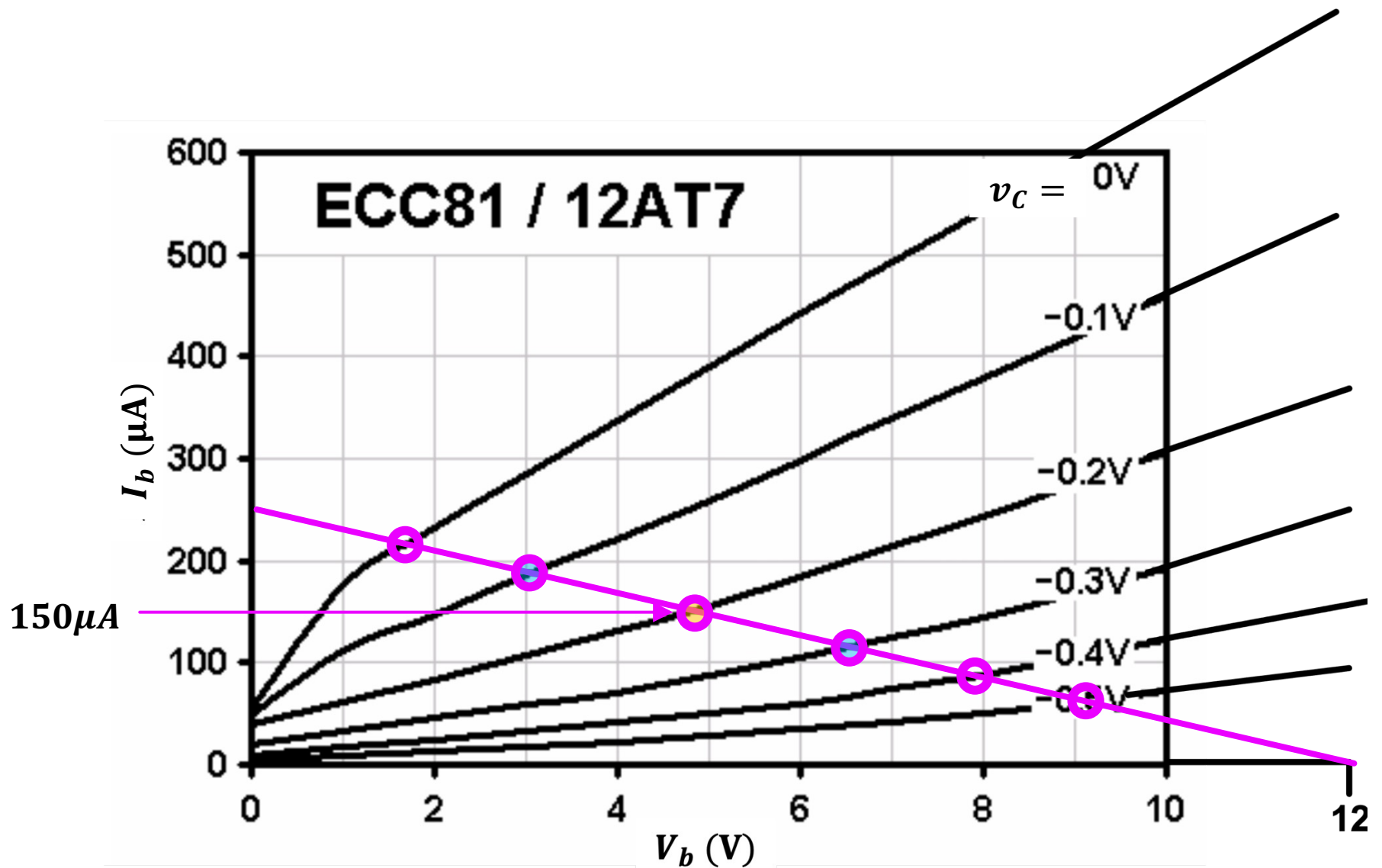

# Method 1: Cathode Bias


- Assuming grid is at Ground, we need a resistor to turn 150  $\mu\text{A}$  into 0.2V
- Thank you Ohm's Law!

$$R_{bias} = \frac{0.2\text{V}}{150\mu\text{A}} = 1300\Omega$$

- So let's build our circuit:

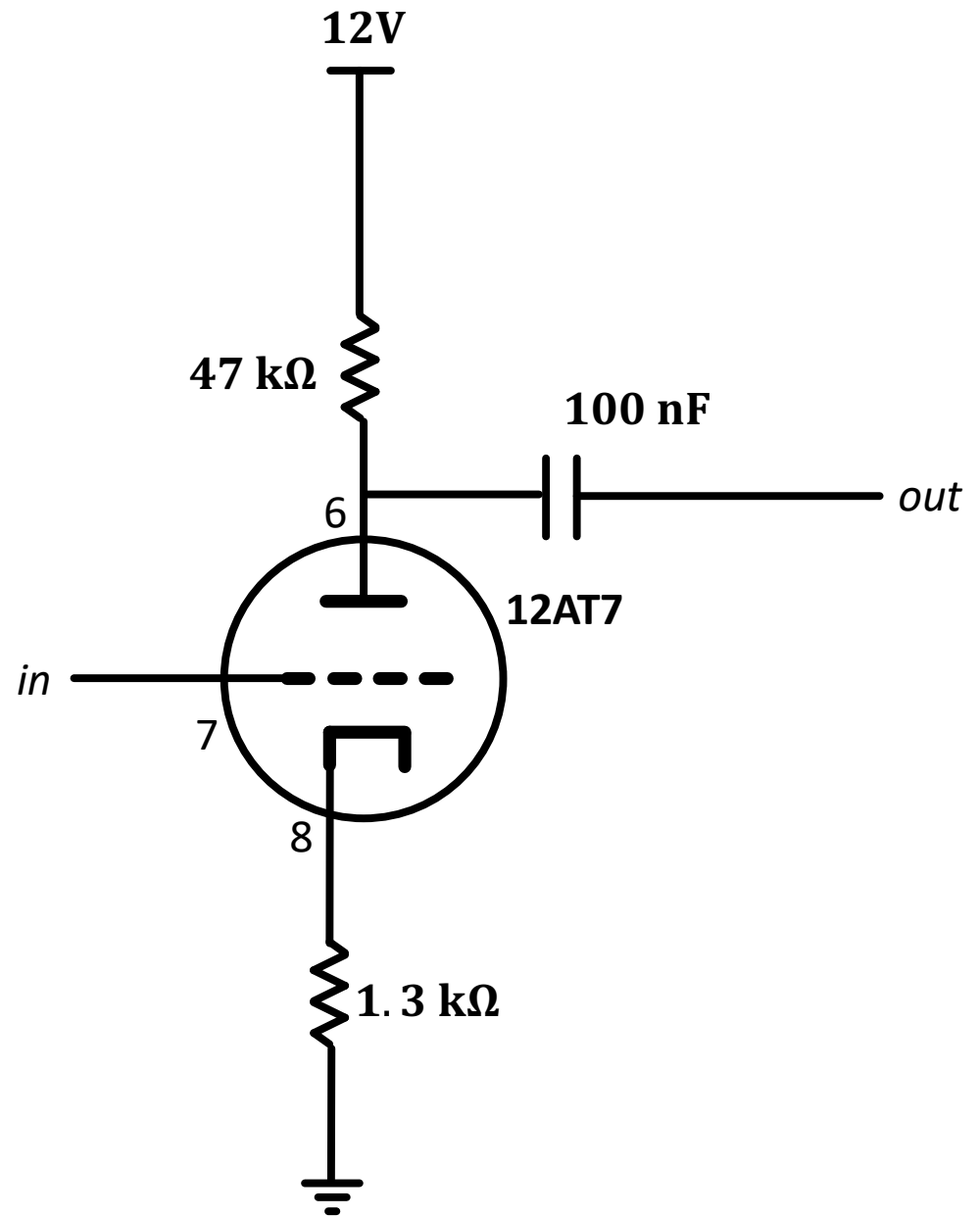
# Cathode Bias

- Noice
- But...
- At audio frequencies the presence of that cathode resistor can eat into our ability to swing up and down...it will essentially modify our load line and bias point


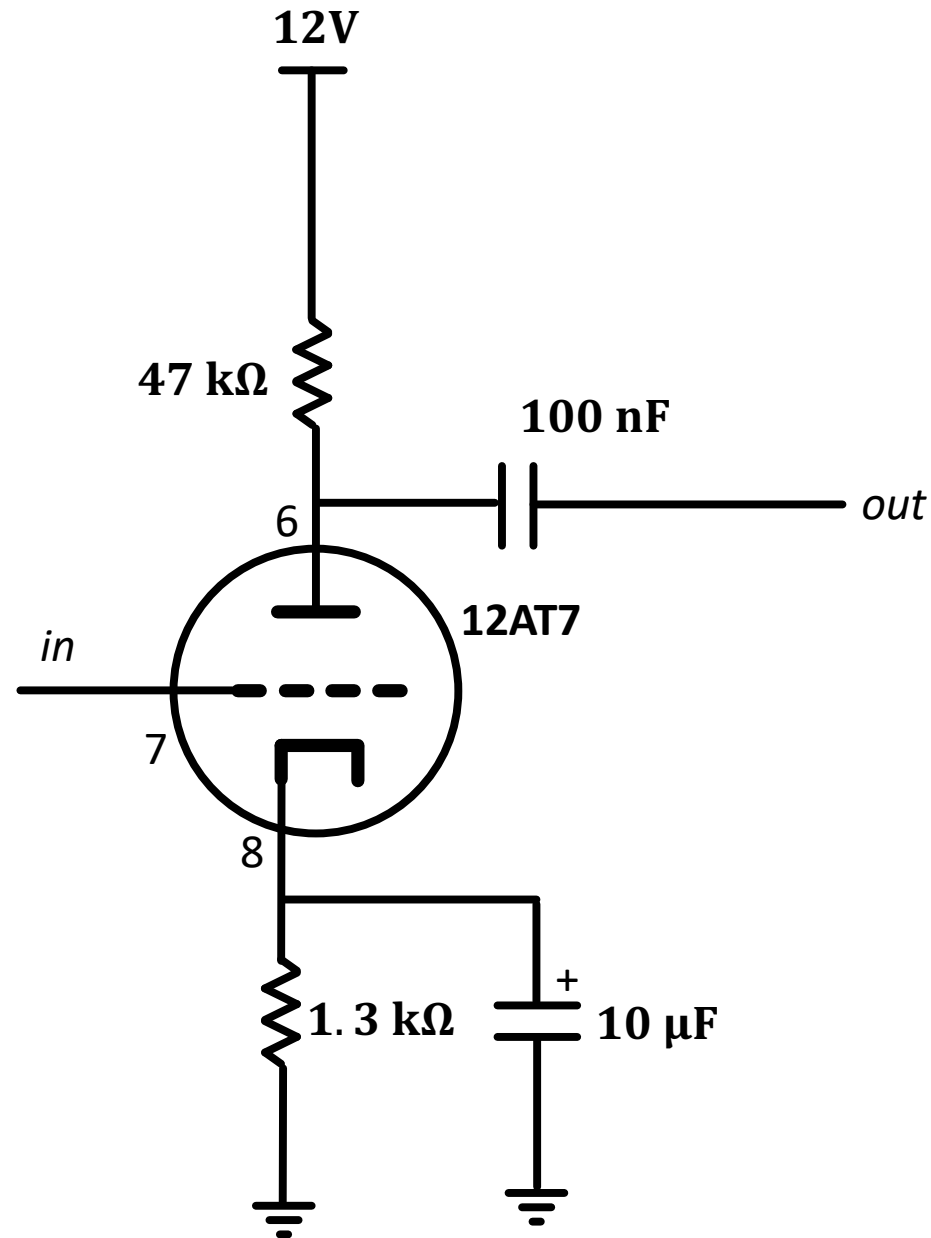
# Cathode Bias

- Solution is to put a capacitor in parallel with the bias resistor
- At DC it is invisible and our biasing is fine
- At AC (audio or whatever), it shorts the resistor out and we don't get the “cathode degeneration”




# Method 2: Grid Leak


- Ground the cathode and then...connect the grid to either ground or (in low volt tube cases)  $V_{cc}$
- This will make the grid a negative voltage
- ...
- ...
- ...
- That doesn't make sense.

# Gridleak Bias

- Just do this

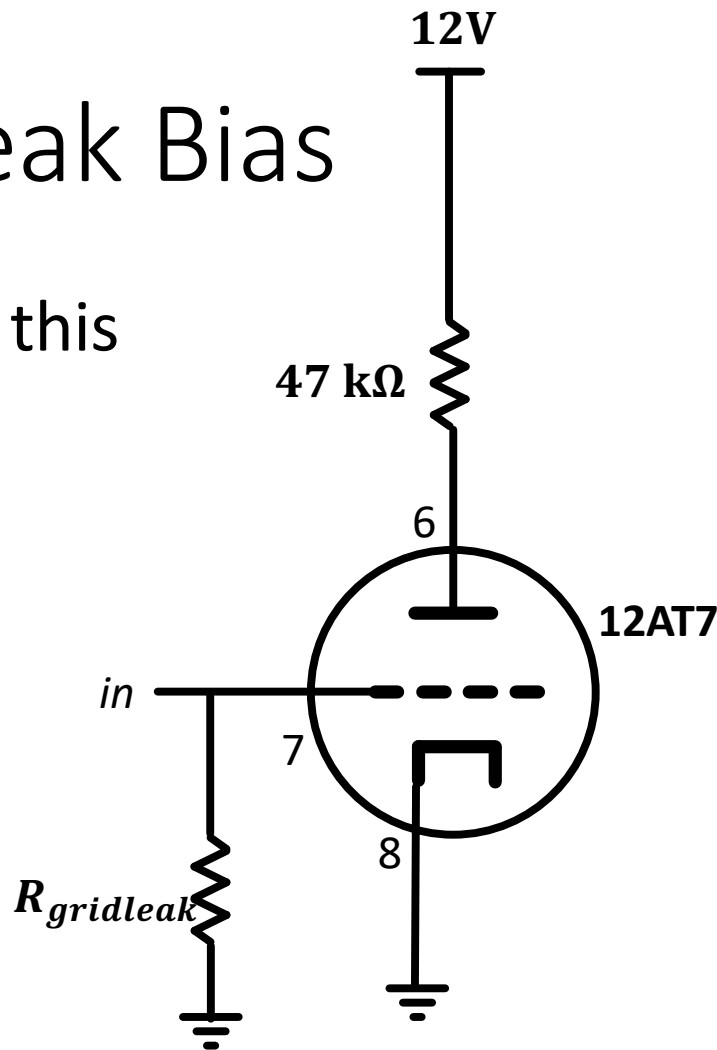


OR

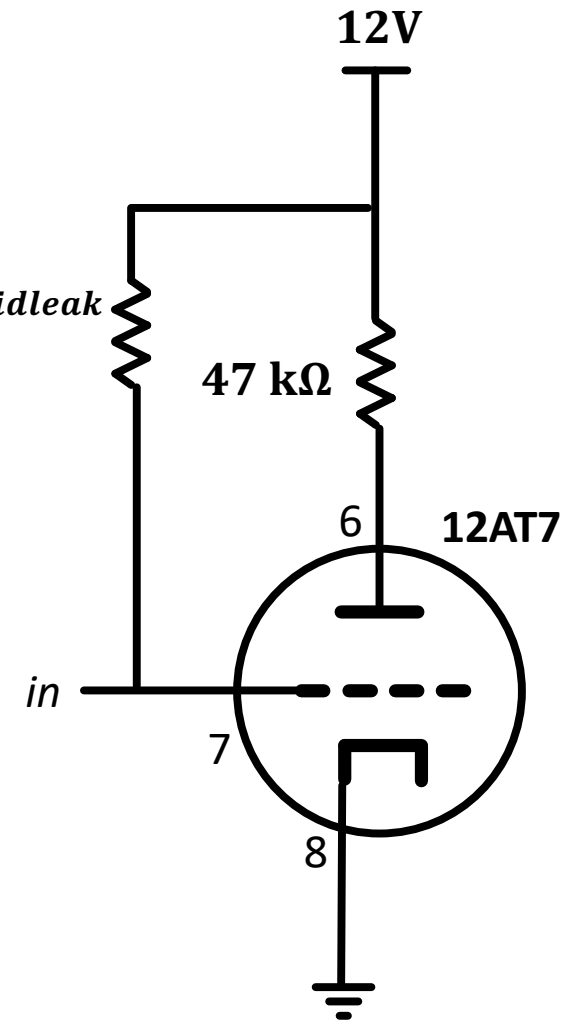

- And you'll get a negative voltage (depends on value of resistor) at the grid but will be negative!
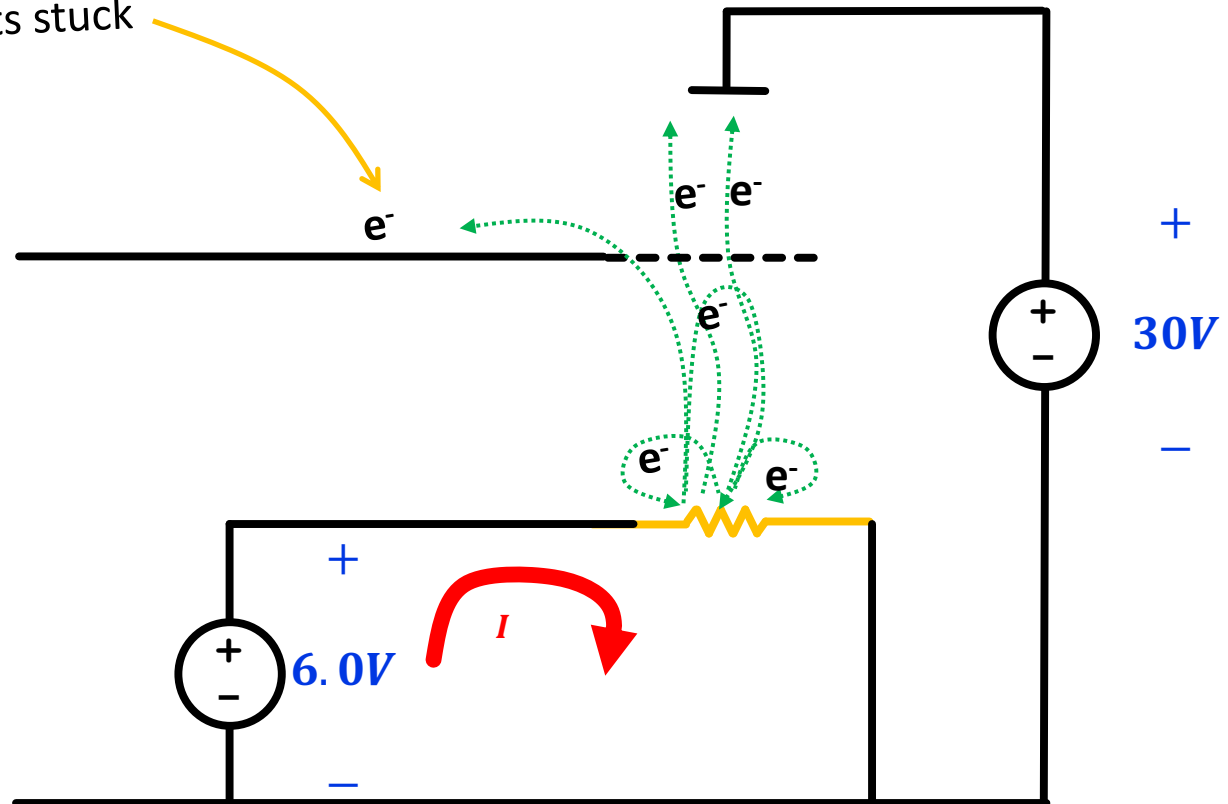
# Remember the “physics”

Occasionally an electron  
lands on the grid, cools  
off, and gets stuck




# Leaking Electrons

- If left alone, eventually enough electrons get stuck on the grid that they make it more and more negative negative to the point that they shut the tube off.
- If we give them an escape route (to anywhere more positive which can either be ground or  $V_{cc}$ ), and you pick the right resistor, you can develop a tuned balance of leaking electrons and a steady negative voltage can be maintained.




# Gridleak Bias

- Just do this

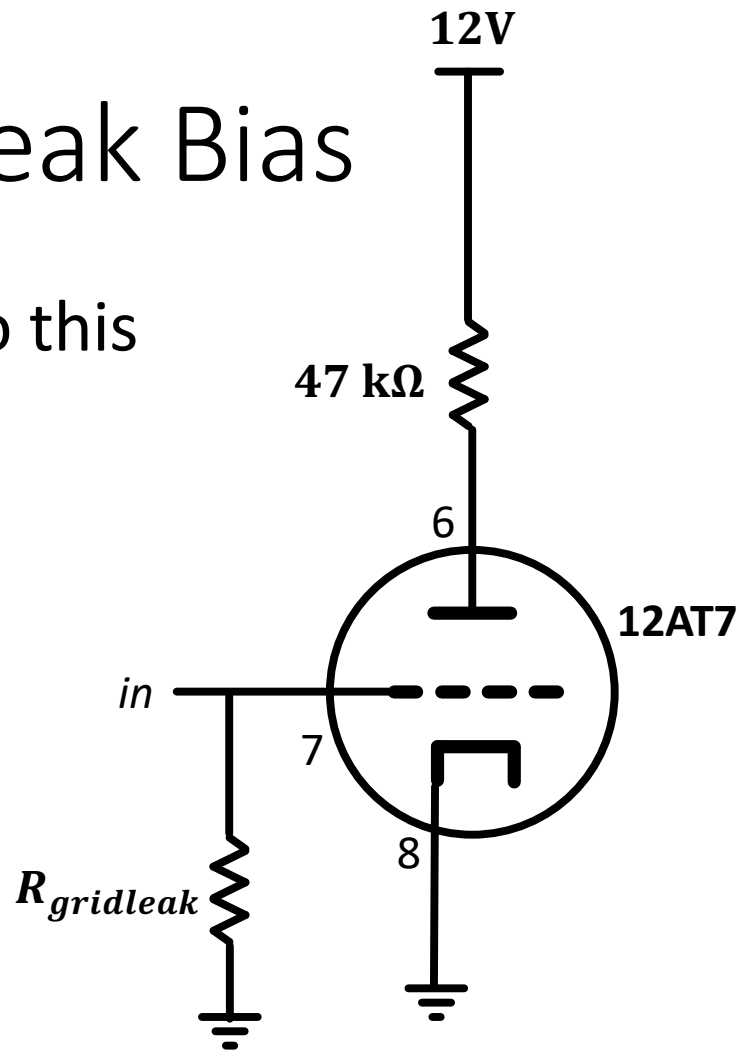


OR

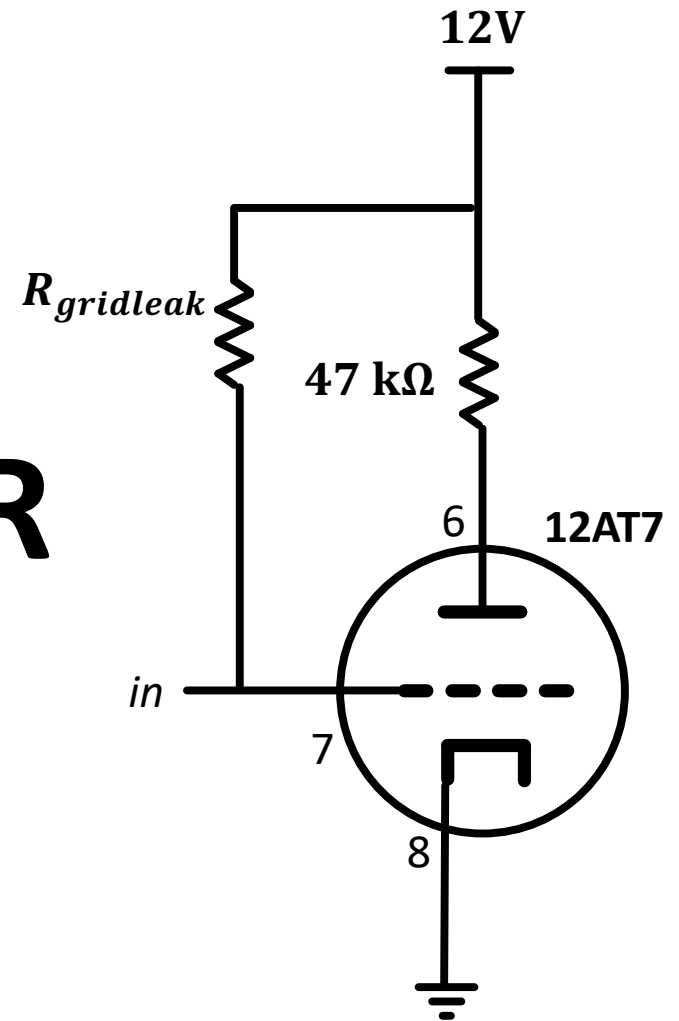

- And you'll get a negative voltage (depends on value of resistor) at the grid!
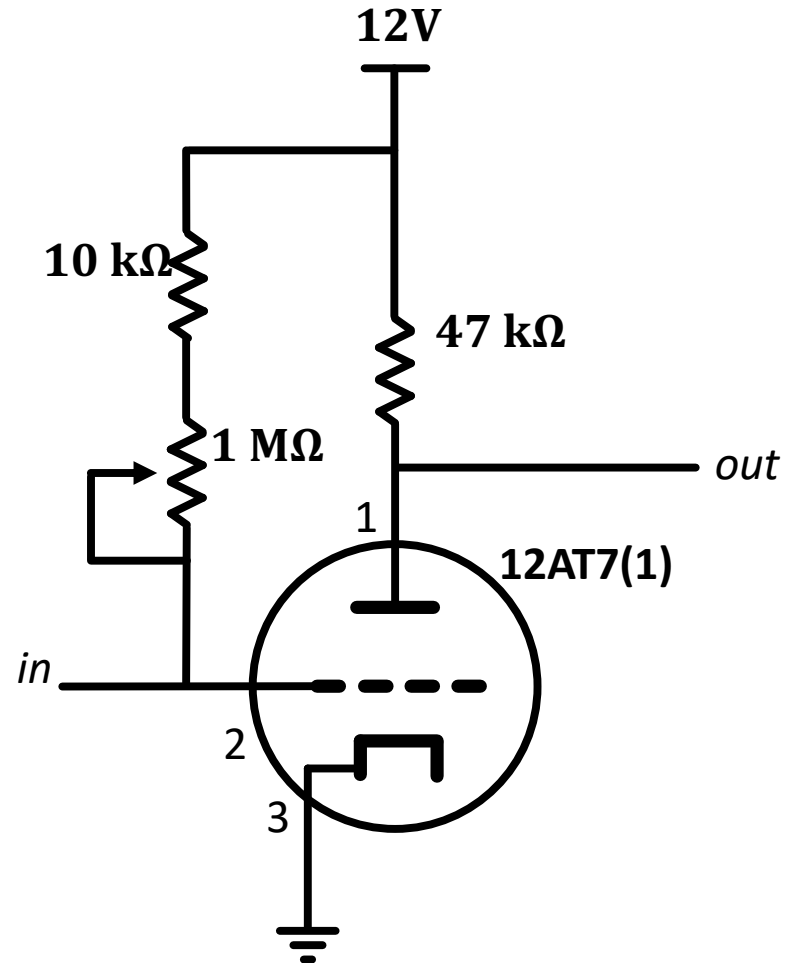
# So grid leak bias:


- Sometimes needs tuning
- But it works.
- It can be unstable, though so often cathode bias is a first choice, but early tube circuits used this a lot
- Also low-voltage sets really benefit from this



*Could also grid leak to ground, but in a starved circuit like ours  
The resistor would need to be much smaller and that would lower input impedance.  
We'll grid-leak to ground on our input stage where impedance doesn't matter as  
much in 2025*

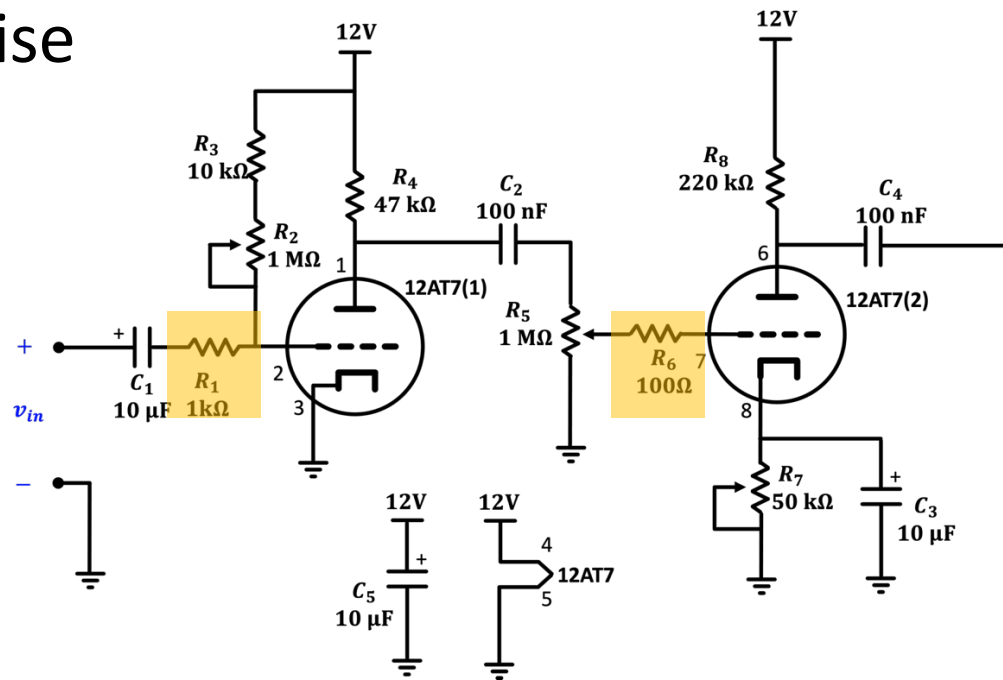
# Grid Stoppers

- More next Tuesday, but rarely connect directly to a tube grid. Instead go through some sort of resistor...maybe 100 to 1000 Ohms.
- Call this a “grid stopper”
- Cuts down on noise


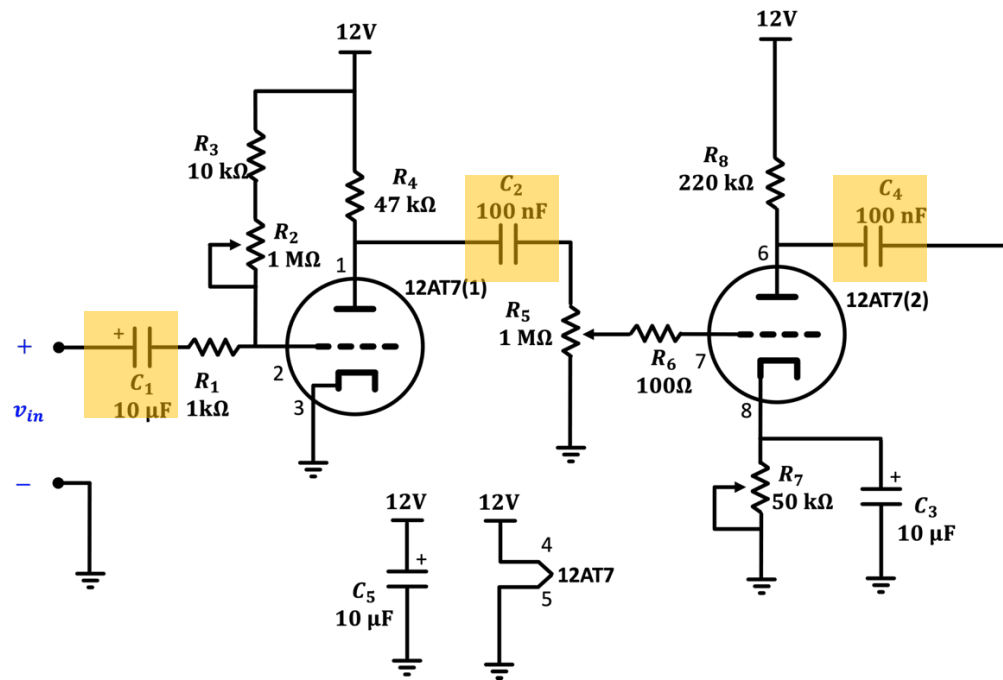
# Capacitive Coupling


- While Early Tube circuits used a lot of transformers or even resistive coupling, capacitive coupling can also be fine
- There's downsides, but as a first intro, they are easy to use
- Let's signals through while preventing the biasing of one stage (DC) affecting the other


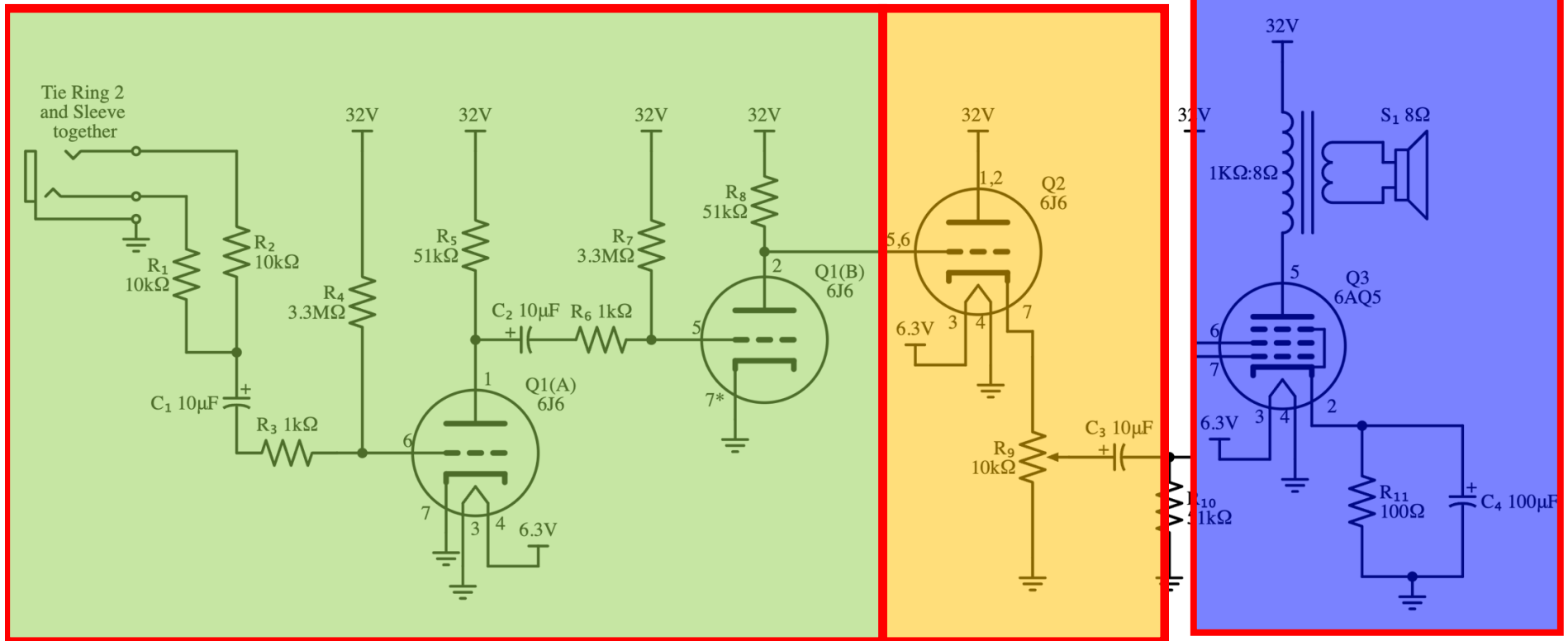
# Lab 4

- Make an Audio Amplifier!

**Buffer stage**  
(link preamp to  
power amp)




*Preamplifier (largely concerned with increasing voltage of signal)*


***Power Amplifier (largely concerned with moving as much energy into the load as possible)***
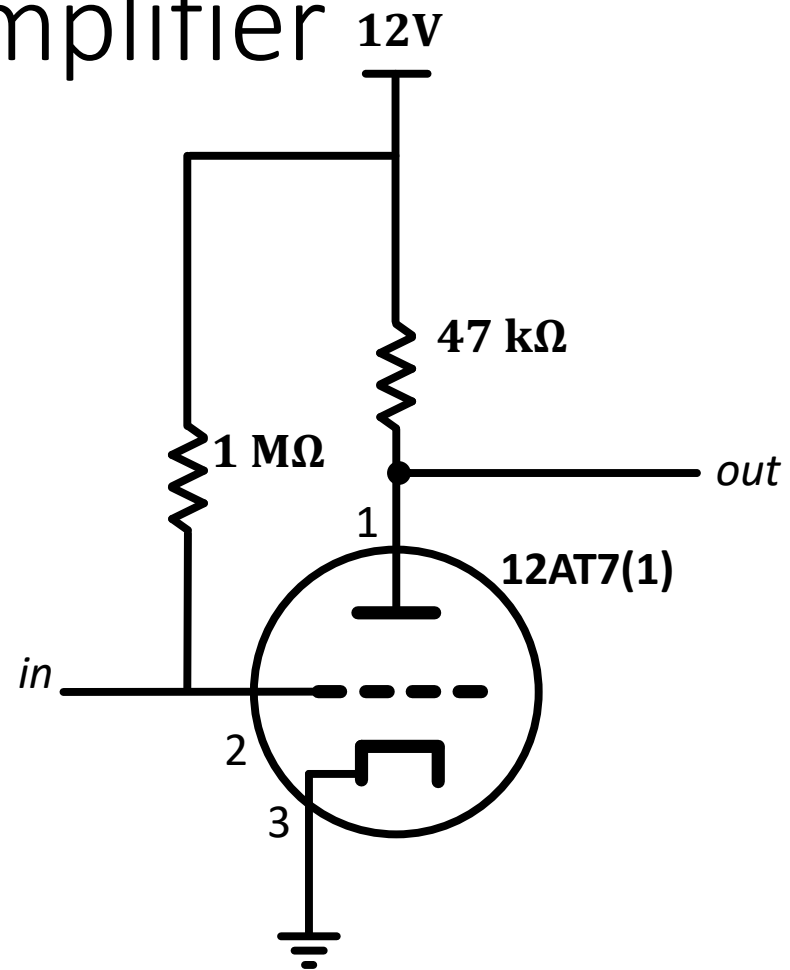
# Common Cathode Amplifier

- The circuit here is a common cathode amplifier...
- You can get decent voltage gain from this but the output impedance can be kinda high
- So if you drive a hungrier load it can have issues



# Common Cathode Amplifier Issues

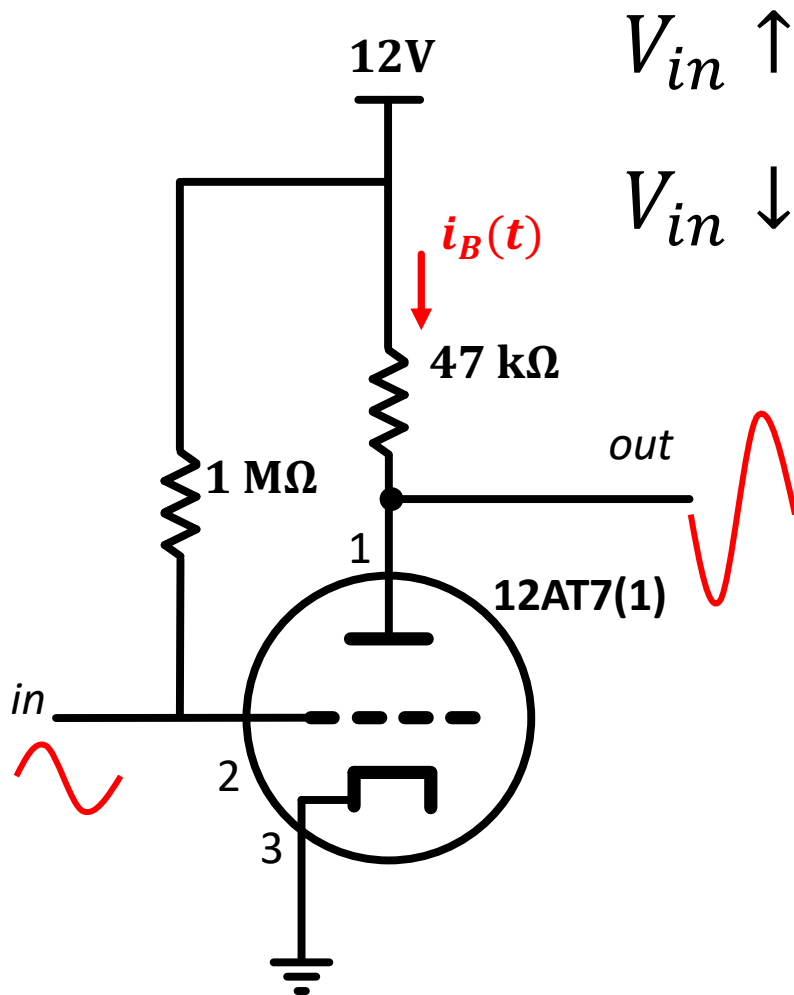


$V_{in} \uparrow \dots \text{means } i_B \uparrow \dots \text{means } V_{out} \downarrow$

$V_{in} \downarrow \dots \text{means } i_B \downarrow \dots \text{means } V_{out} \uparrow$

*This means the output signal is 180 degrees out of phase with input signal*

*And the amplitude of gain is correlated with larger plate resistance!*

# But What happens when driving a Load ?

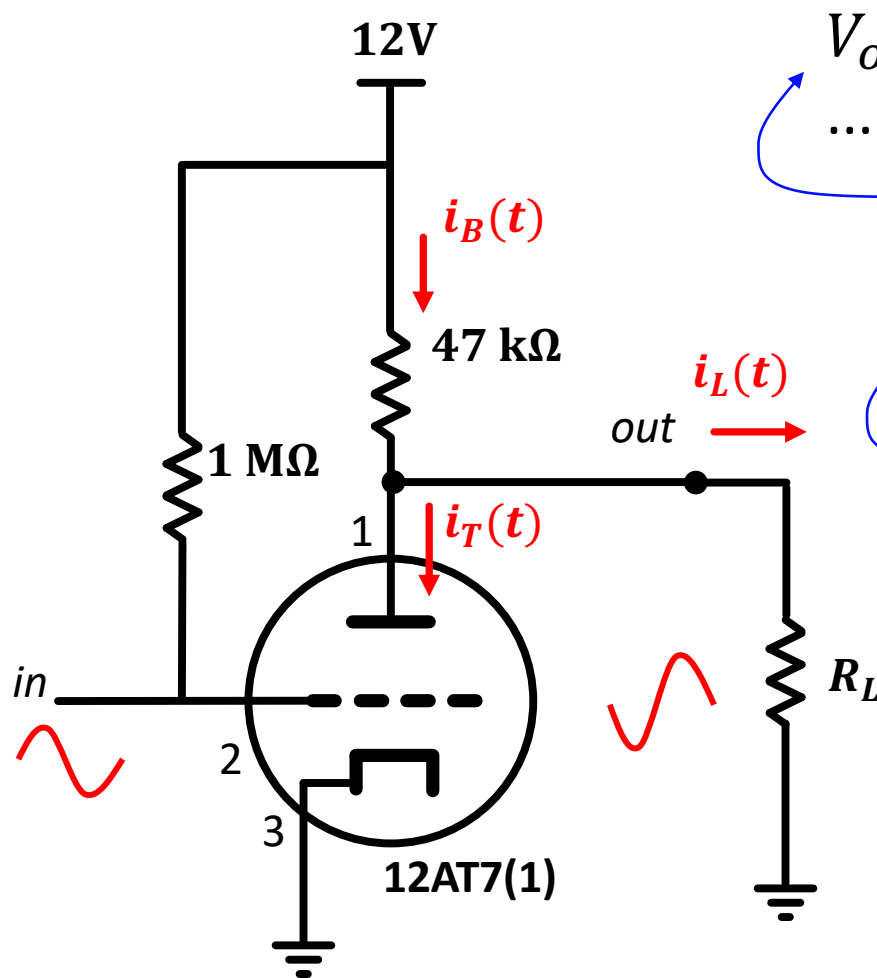

$V_{out} \uparrow \dots$  means  $i_L \uparrow \dots$  means  $i_B \uparrow$   
 $\dots$  means  $V_{out} \downarrow$

*System fights change*

$V_{out} \downarrow \dots$  means  $i_L \downarrow \dots$  means  $i_B \downarrow$   
 $\dots$  means  $V_{out} \uparrow$

*System fights change*

*Basically the presence of any load will impact the output amplitude of the signal*

*Instead of:*




*you might have (or worse):*





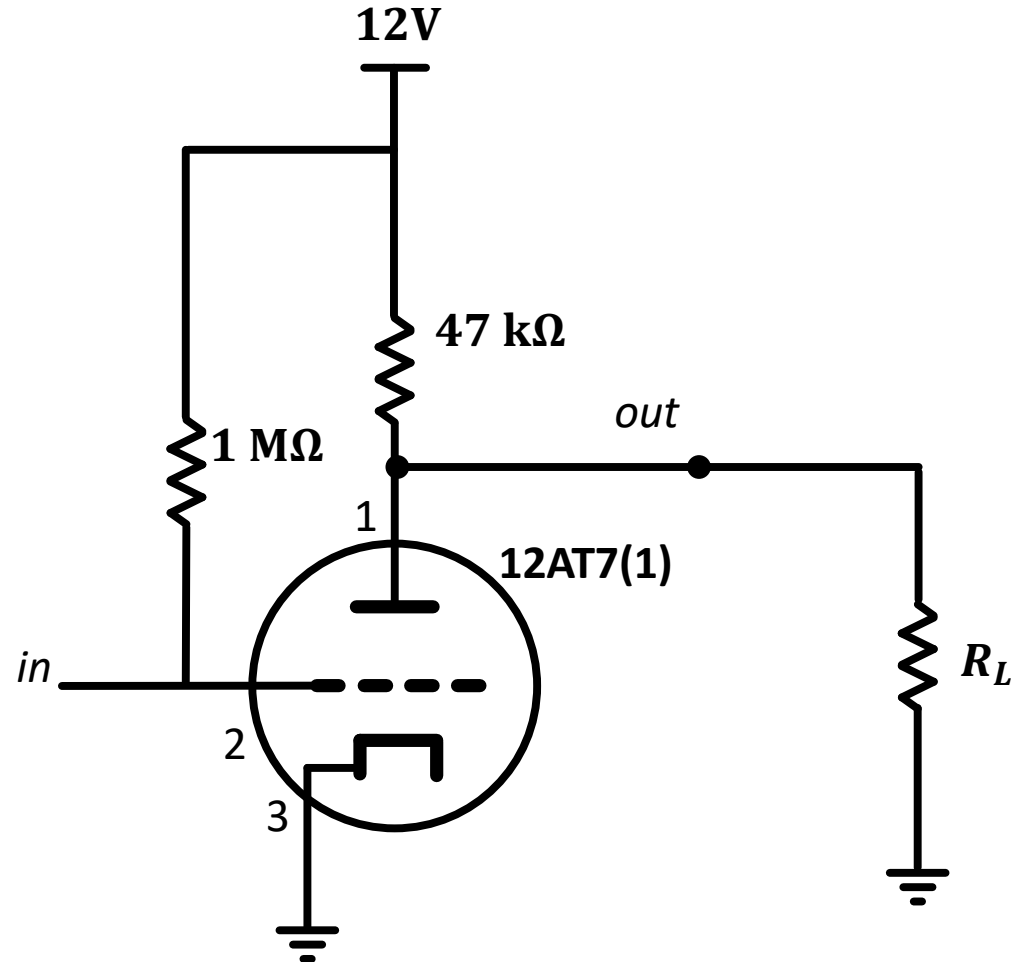
# Common Cathode Amplifier Issues

- The presence of a load at the output matters little when it is very high impedance
- The lower that load gets in terms of impedance, the harder it is to put meaningful signal onto the load



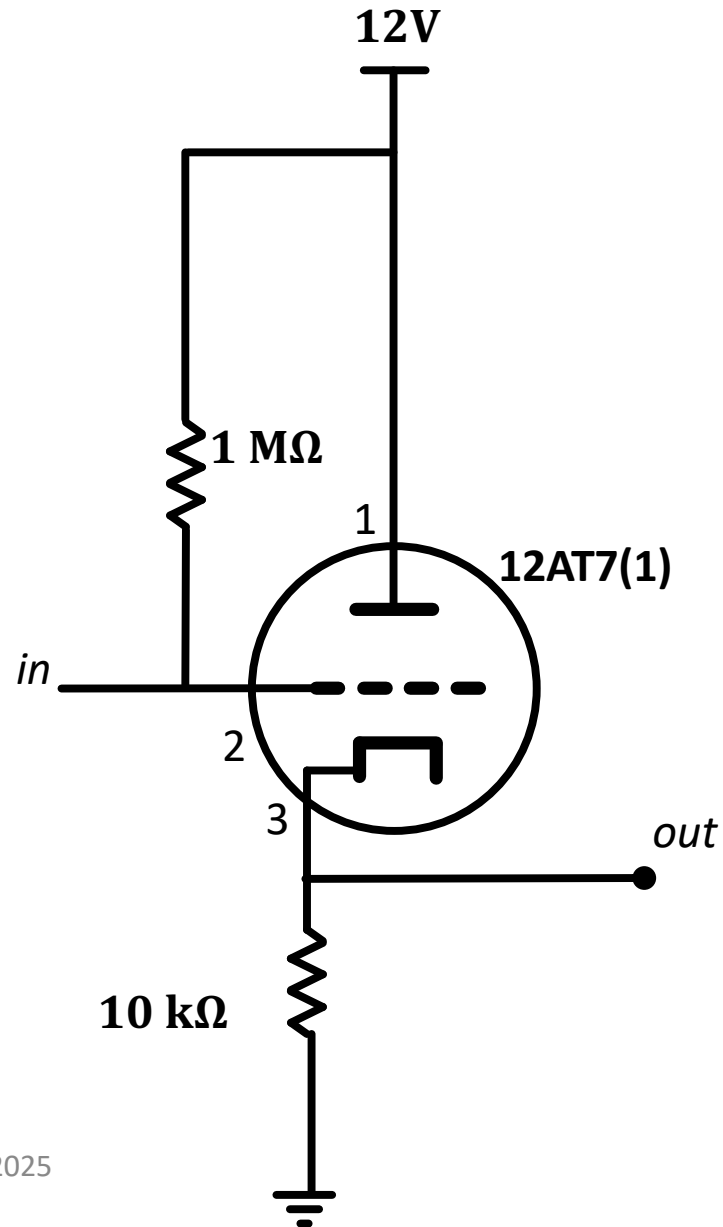
# Common Anode aka Cathode Follower

- Instead of using signal at the plate, we instead use signal at the cathode as output
- This circuit will provide no voltage gain, but can provide significant power gain



# Cathode Follower on its own

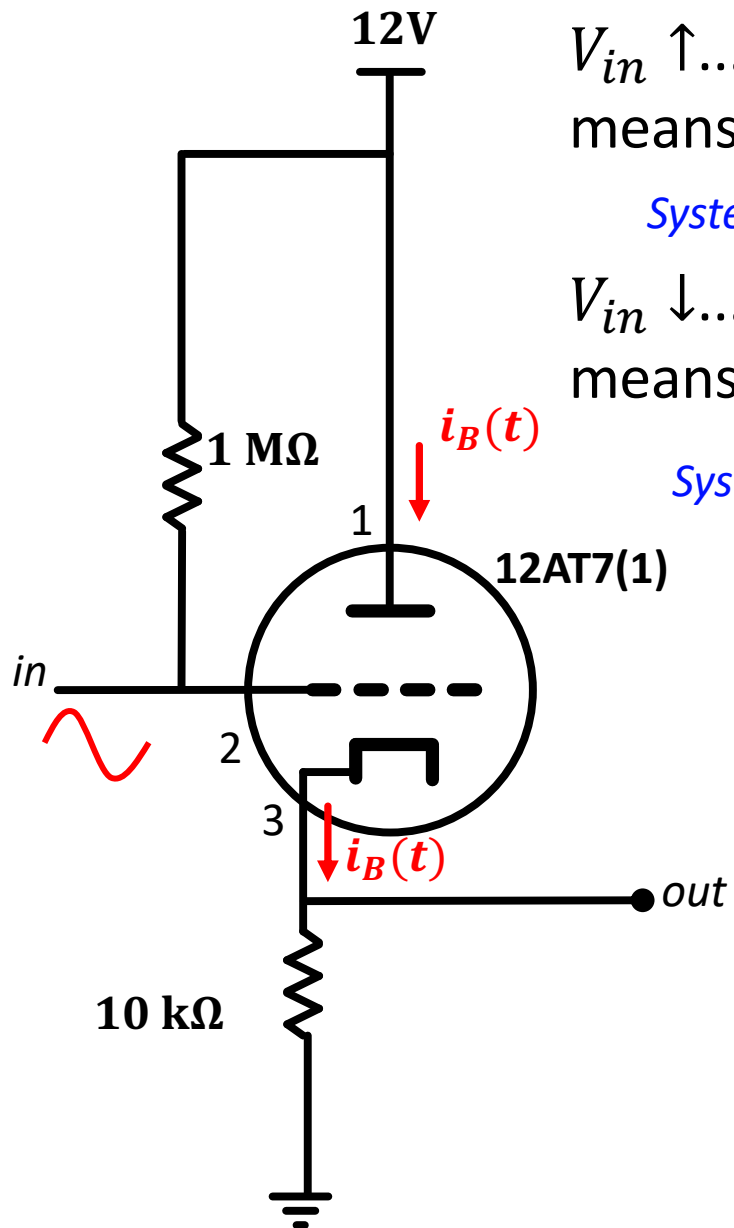

$V_{in} \uparrow \dots$  means  $i_B \uparrow \dots$  means  $V_{out} \uparrow \dots$  which actually means  $V_{in} - V_{out} \downarrow \dots$  means  $i_B \downarrow$


*System has negative feedback which stabilizes*

$V_{in} \downarrow \dots$  means  $i_B \downarrow \dots$  means  $V_{out} \downarrow \dots$  which actually means  $V_{in} - V_{out} \uparrow \dots$  means  $i_B \uparrow$

*System has negative feedback which stabilizes*

*In normal operation a cathode follower has negative feedback which basically forces the voltage at the cathode to “follow” the input voltage*

# Cathode Follower with Load resistor

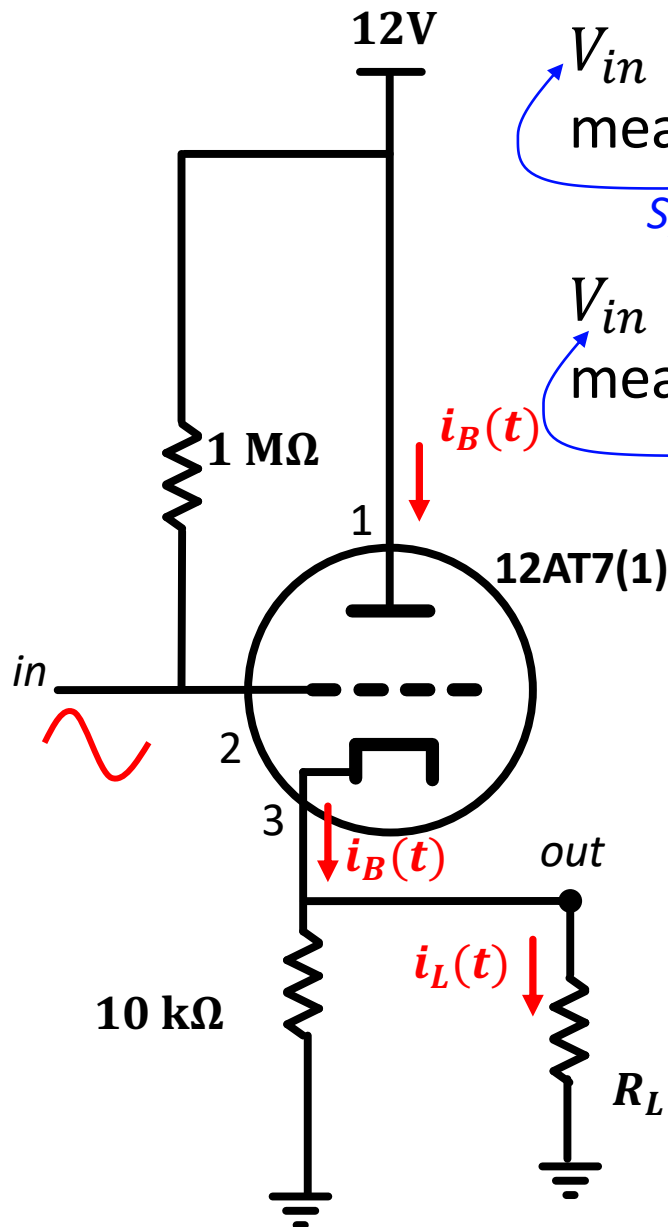

$V_{in} \uparrow \dots$  means  $i_B \uparrow \dots$  means  $V_{out} \uparrow \dots$  which actually means  $V_{in} - V_{out} \downarrow$

*System fights change*

$V_{in} \downarrow \dots$  means  $i_B \downarrow \dots$  means  $V_{out} \downarrow \dots$  which actually means  $V_{in} - V_{out} \uparrow$

*System fights change*


*Even if a load resistor is attached in parallel to the bias resistor, the circuit still roughly works the same because of the negative feedback.*

*The negative feedback isn't destructive like it is in the common cathode amplifier!!!*
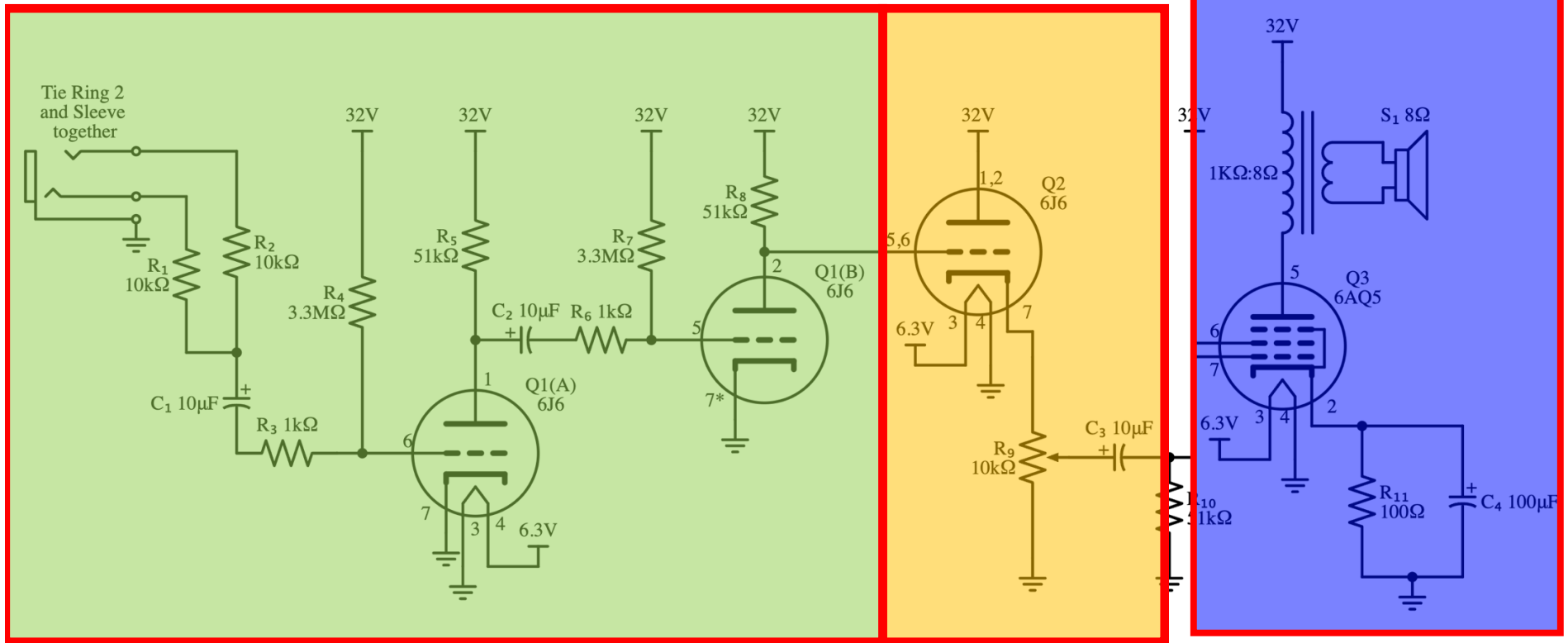
# Lab 4

- Make an Audio Amplifier!

*Buffer stage  
(link preamp to  
power amp)*



*Preamplifier (largely concerned with  
increasing voltage of signal)*


*Power Amplifier (largely  
concerned with moving as  
much energy into the load as  
possible)*

# Other Tubes?

- A low-voltage triode does not have the ability to drive much power.
- In order to drive a speaker with its very low resistance (like maybe 8 or 16 Ohms)...we need devices that can put out a bit more current.
- In lab we'll use a 6AQ5 beam-power pentode
  - I don't have super good low-voltage plots of its behavior so we'll think about a sort of equivalent tube for it instead, the 12K5
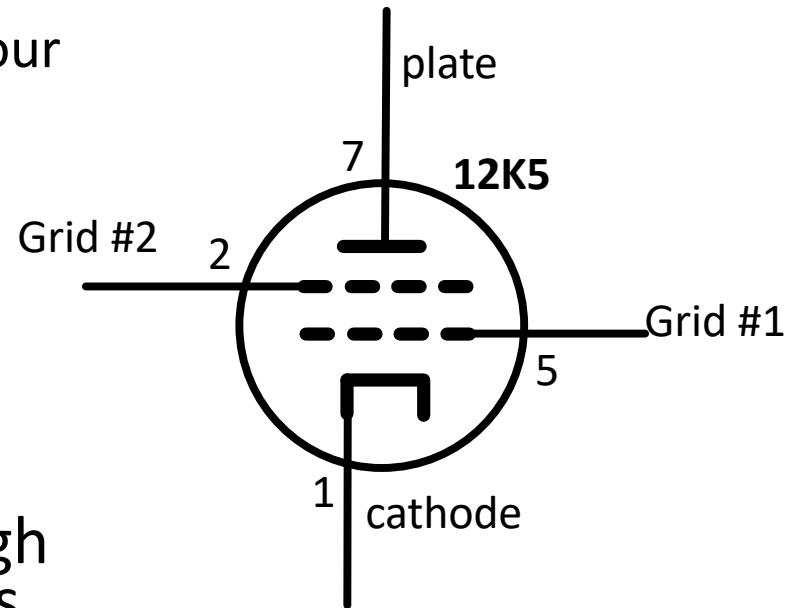
# Another Tube?...the 12K5

- Space-Charge Tetrode
  - Tet is something for "four" ...so four electrodes
- Plate still plate
- Cathode still cathode
- Grid 2 is like our regular triode grid
- Grid 1 can be thought of as an accelerator grid. Attach it to high voltage (12V) and this will let us accelerate the cloud of electrons that builds up near the cathode more effectively towards the plate
- The 12K5 was meant to be used in automobile radios...it was a vacuum tube with actual low-voltage specs!



*This is kind of a weird tube and not used very often*

# Aside Car Electronics with Tubes

- Cars had radios and electronics in them as early as the 1930s.
- Tubes run on high voltages (100's of volts)
- Car batteries have been 12V or 6V for long time
- How did we get high voltage from low voltage batteries?




# Vibrator Power Supplies

- Use a electromechanical switch oscillator.
  1. Coil would charge up, causing relay to close
  2. Closed relay would break current, causing relay to release
  3. Released relay switch would let current start to flow again
- Rumbled while it ran hence name
- Make AC (square wave) from DC...and then run through step-up transformer



# Vibrator Power Supplies

- Simple example:

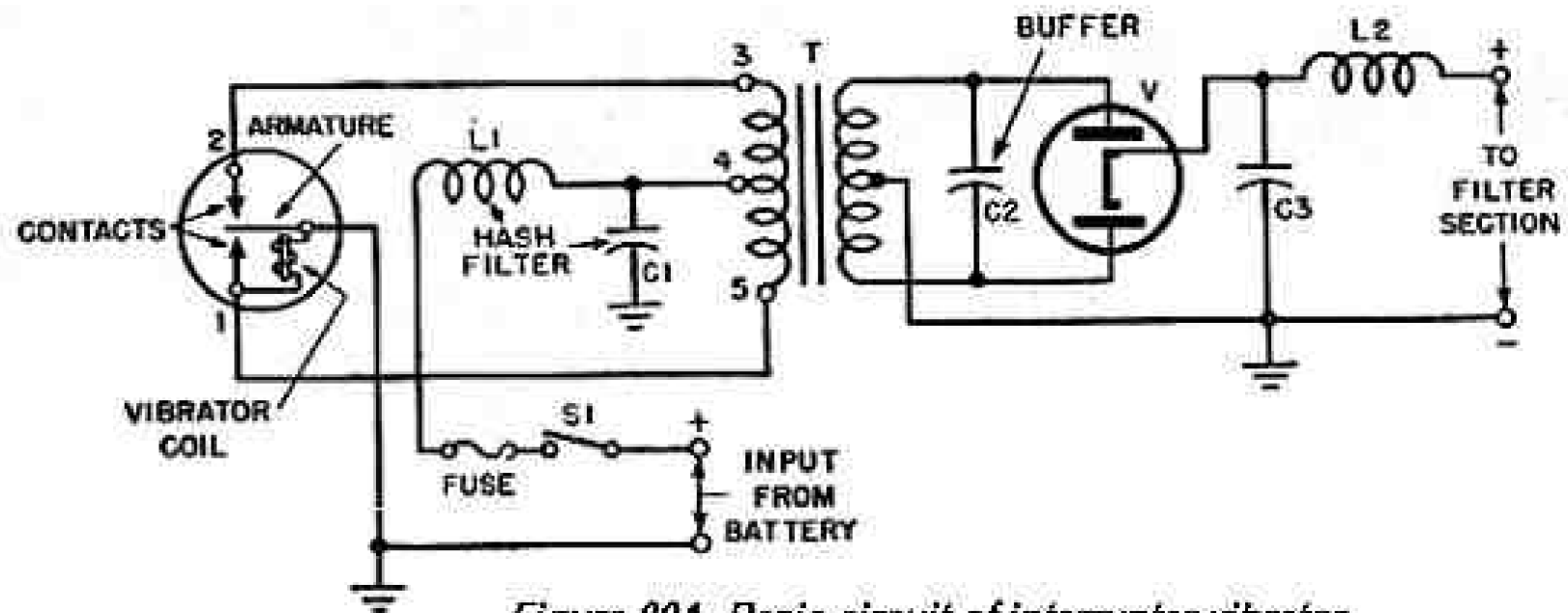


*Figure 80A. Basic circuit of interrupter vibrator.*

# Anyways... About this 12K5 Tube...


- Vibrator power supplies broke a lot (they were mechanical after all and the MechE's are always the ones who fail us)
- So in late 1950's research was done into making vacuum tubes that could actually work sorta well at 12V
- None of these tubes could produce much power, but they could do voltage gain and RF work at a time when newly appearing semiconductors just couldn't
- The 12K5 was meant to be a audio amplifier driver for what would likely be an early germanium or silicon power transistor or something...not meant to drive a speaker directly
- We'll use another low-voltage tube (12CN5) next week to give us a pentode.
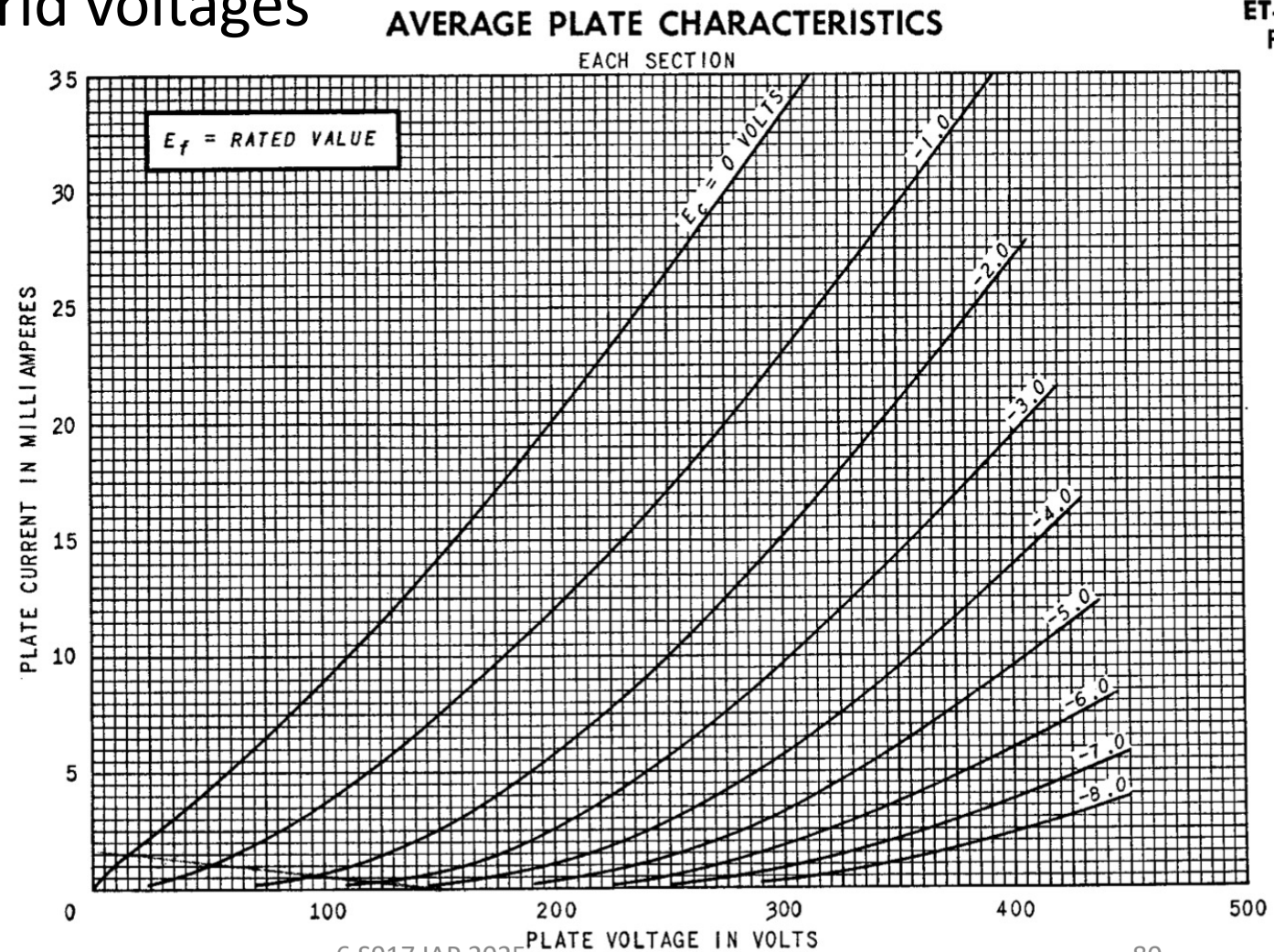
# Remember the Triode Curve...

- Plate current as a function of plate voltage for specific grid voltages





# The Space-Charge Tube is different

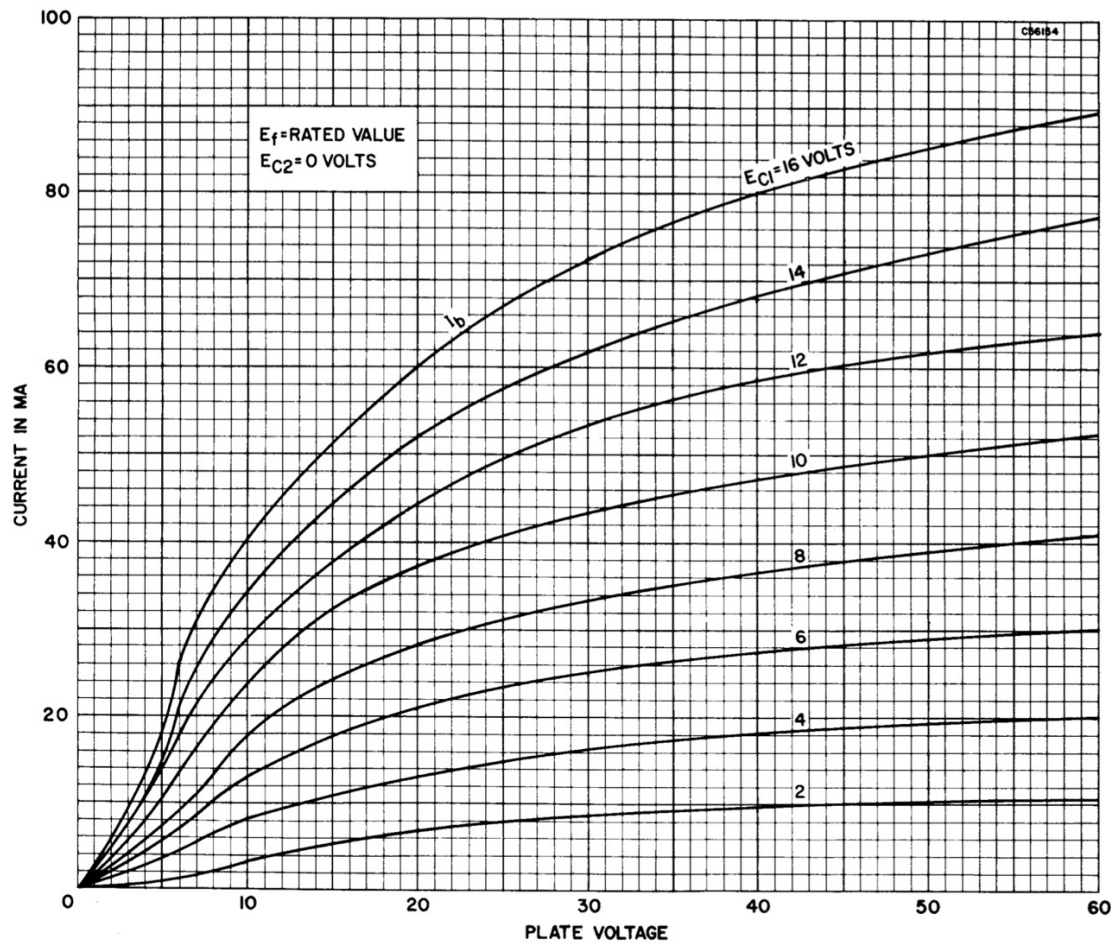

*For a given control grid ( $C_2$ ) value (here 0V), increasing the space charge grid voltage ( $C_1$ ) in the positive direction accelerates the electrons! Increasing the current!*
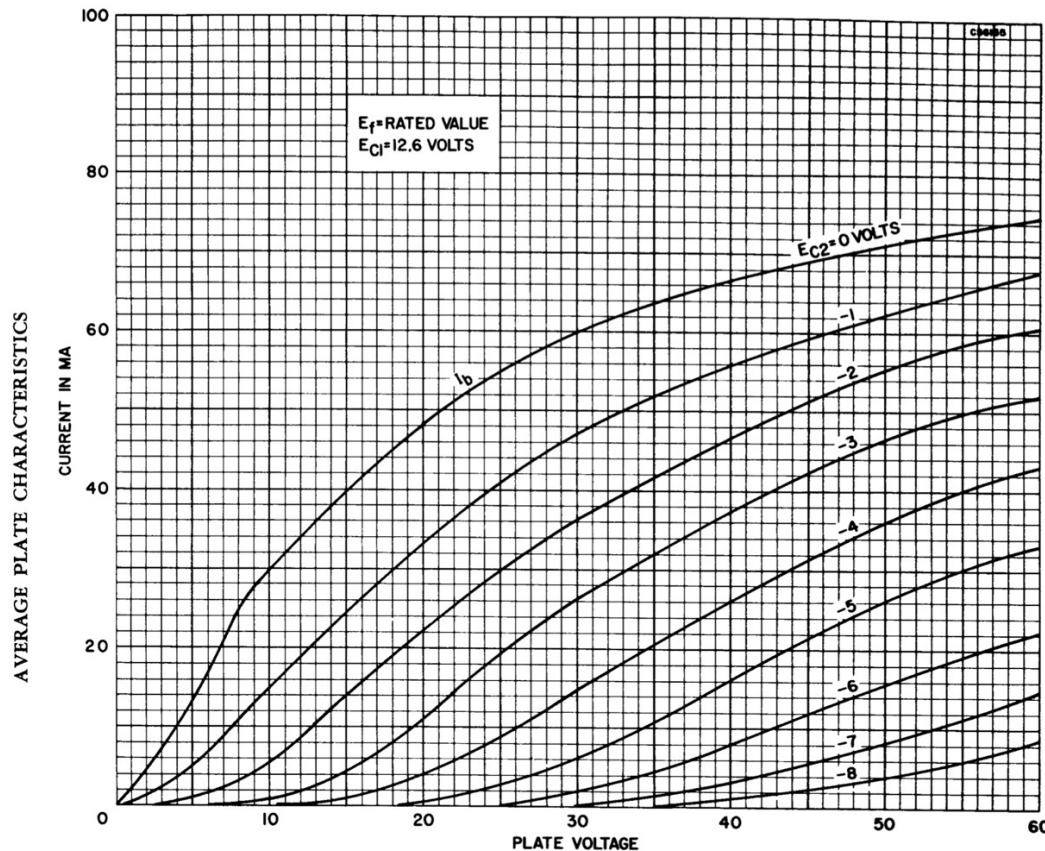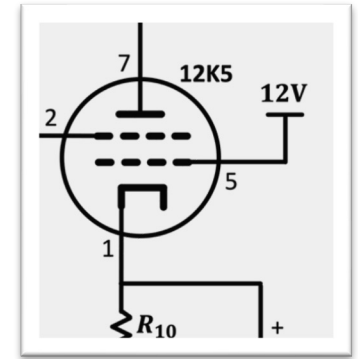
# Just Tie $C_1$ to 12V

- We'll just tie the accelerator grid to 12V since that's easiest. Also there is a nearby (12.6V) plot in the datasheet that we can study then.



*Given the space charge grid is set to 12.6V, plots of plate current  $I_B$  as functions of control grid voltage  $V_{C2}$  and plate voltage  $V_B$  are shown here*


*Control grid voltage  $V_{C2}$  is still negative relative to cathode! Just like in triode!*



# Qualitative Check...


- The 12K5's characteristics look a lot more “transistor-like” than the triode

12K5 tetrode:

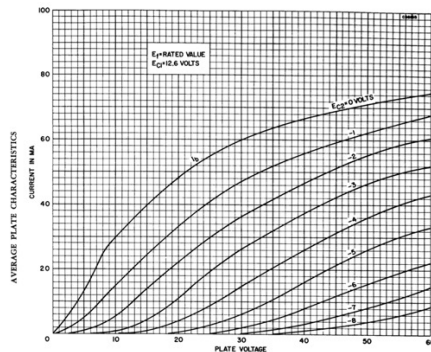


This looks more like this than this

12AT7 triode:

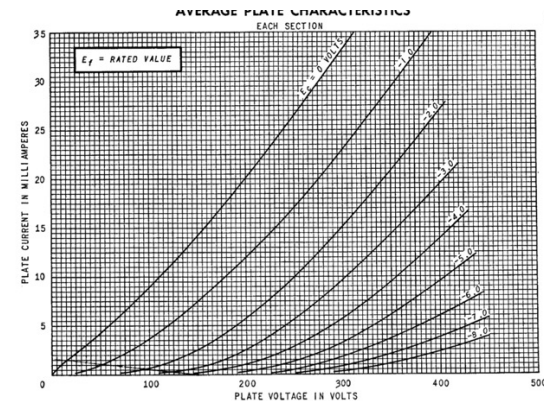



MOSFET:

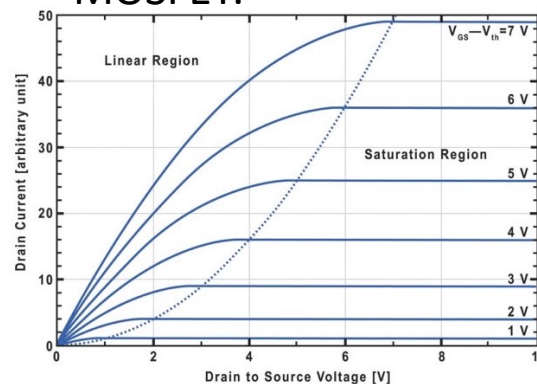

*Sign of things to come (future classes)  
As more electrodes are added, the  
triode curve disappears and the  
“pentode/transistor” curve shows up*

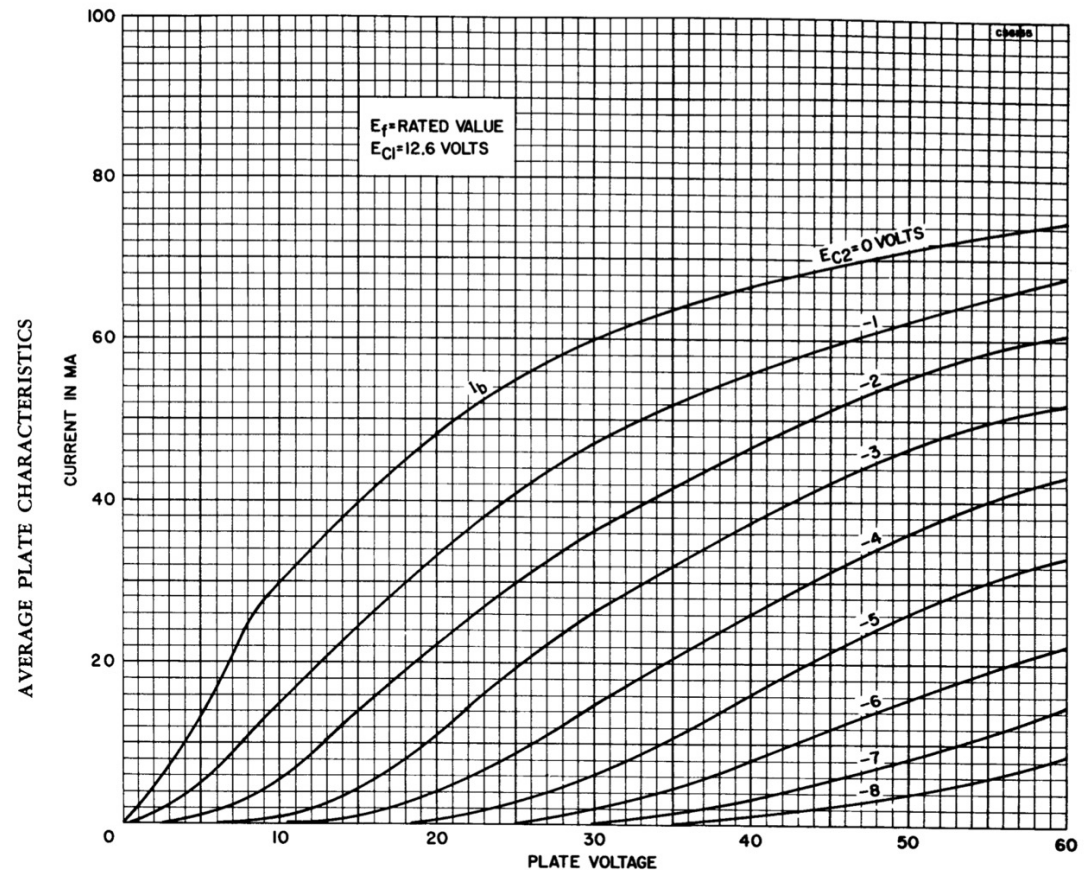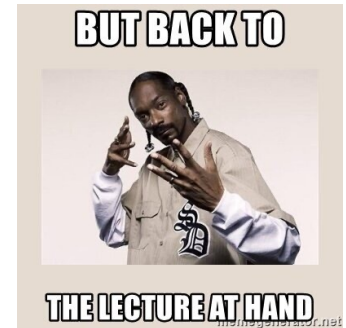
# But Back to the Lecture At Hand

- Where should our load line go?
- We know the  $x$  ( $v_B$ )-intercept: 12V
- What is our slope or  $y$ -intercept?
- What is our Load?





# Tetrode is Driving a speaker.

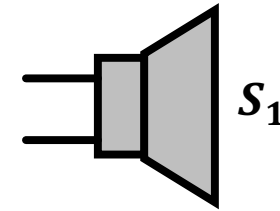

- What is the impedance of a speaker?
- Generally Very Low:
  - 8 Ohms, for example. What will that give us for a load line?


$y(i_B)$ -intercept will be:

$$1500 \text{ mA} = \frac{12\text{V}}{8\Omega}$$

Waaaaaay up there

IS THIS OK?

Iunno this is just a line

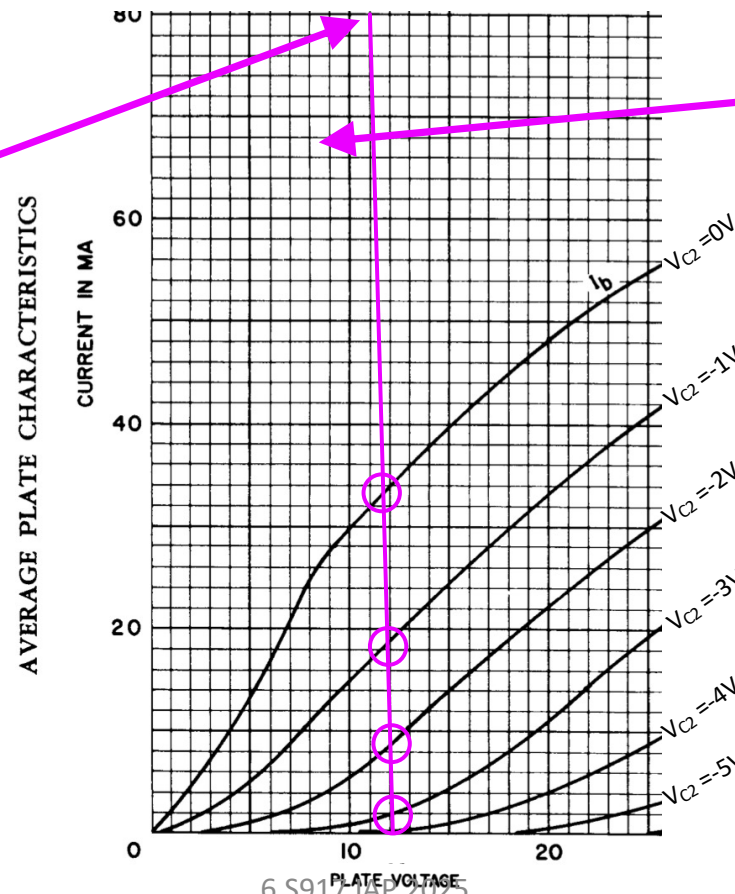

Slope is  $-\frac{1}{R_{\text{speaker}}}$   
This thing is essentially vertical



# Well let's think...

- If the input voltage is biased at -1V and we wiggle back and forth by +/- 1V what do we get?

$$A_v = \frac{\Delta V_b}{\Delta V_{c2}} \frac{11.938V - 11.736V}{-3V - -1V} = -0.1$$

*IS THIS OK?*

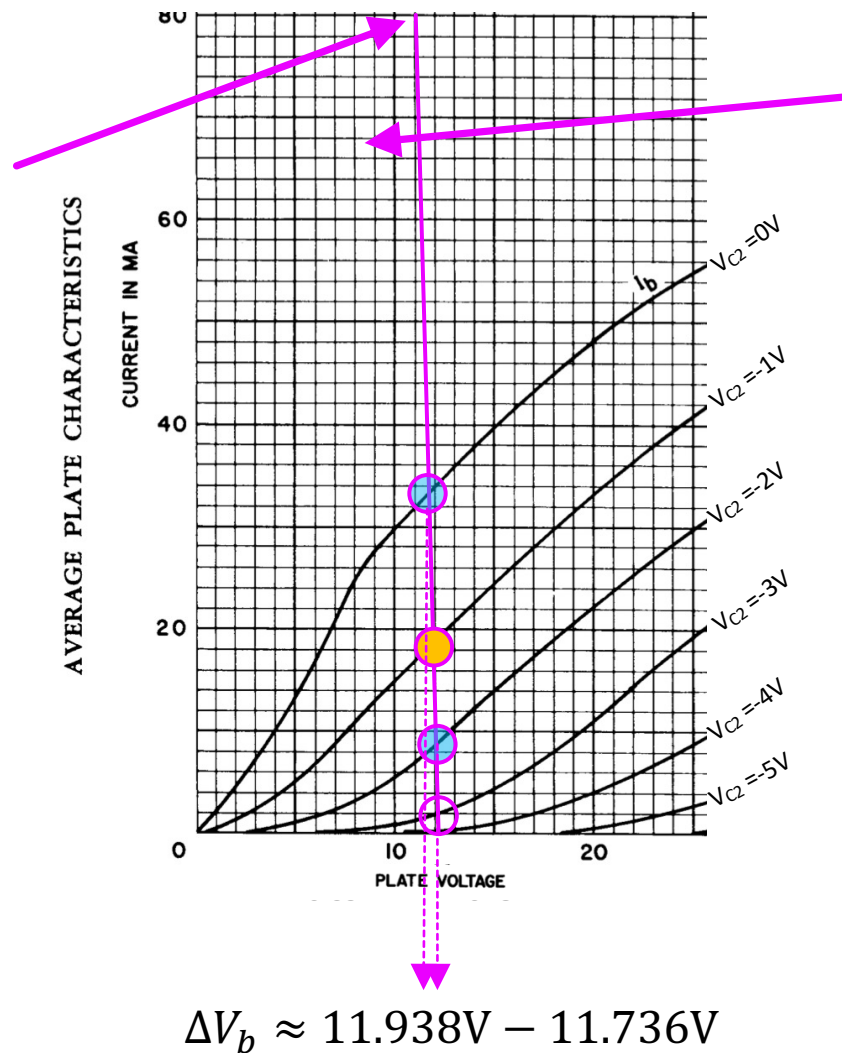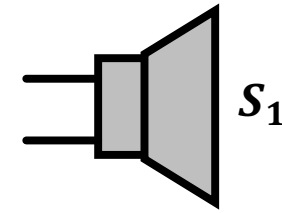**Voltage gain  
isn't really what  
we care about**



# How much power is delivered to load?


- For a  $2V_{pp}$  input sine wave, we get out a  $200\text{ mV}_{pp}$  sine wave into an 8 Ohm Load
- A  $200\text{ mV}_{pp}$  sine wave has an amplitude of 100 mV
- A sine wave with amplitude 100 mV has an  $V_{RMS}$  of 70.7mV
- Power delivered to 8 Ohm load from this signal is  $P_L = \frac{V_{RMS}^2}{R_L} = \frac{0.0707^2}{8\Omega} \approx 620\mu\text{W}$

*IS THIS OK?*

**This is not a lot of power...**  
**So no, this sucks**

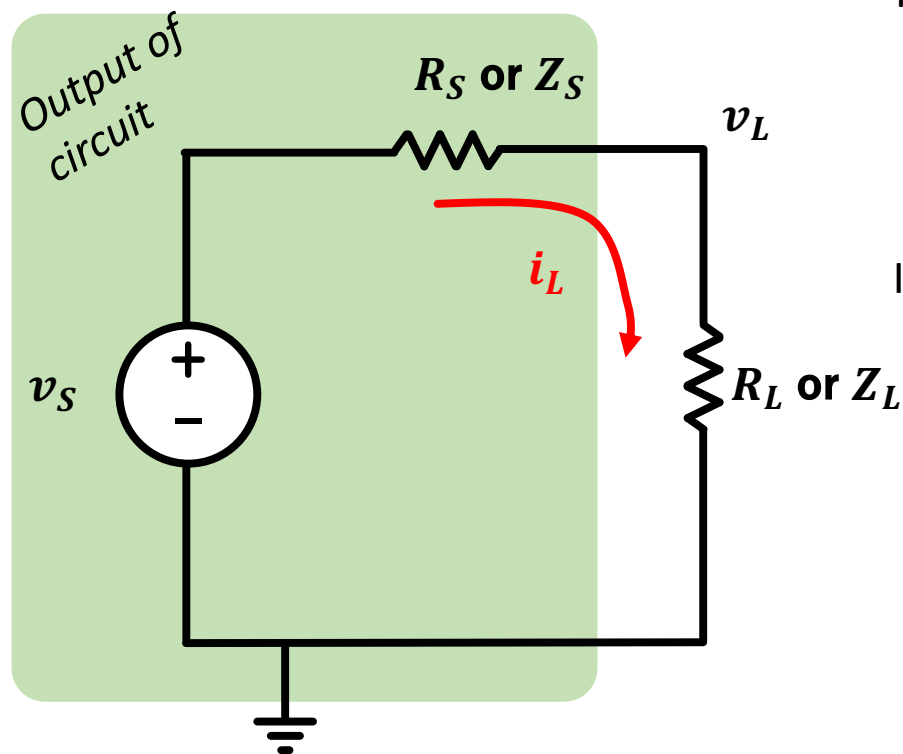
# We need a better impedance

- We can always model the exchange of information and energy from one portion of a circuit to another with a Thevenin circuit driving a load:




If concerned about passing voltage onto load:  
focus on  $R_L > R_S$  and ideally  $R_L \gg R_S$

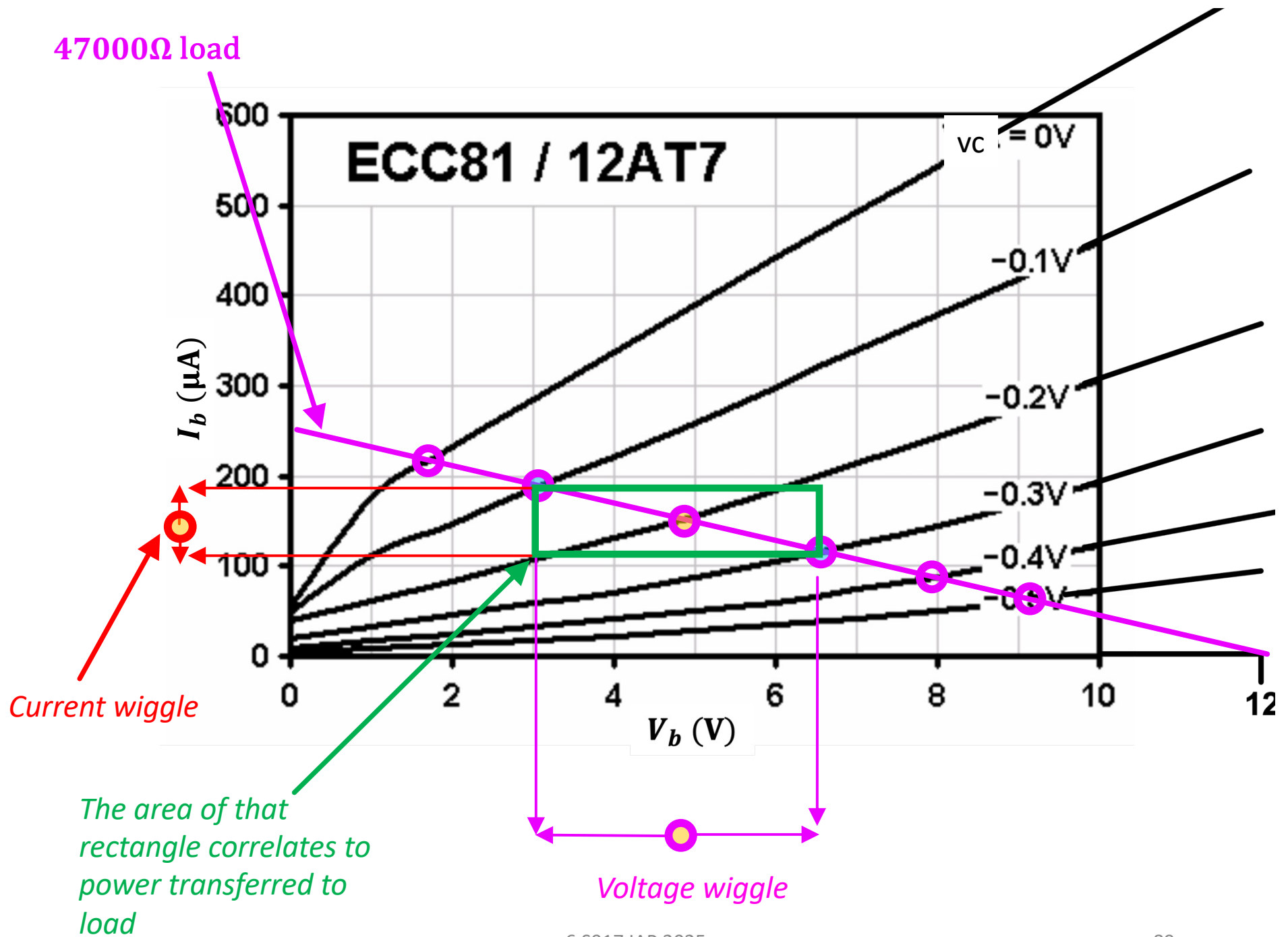If concerned about passing max power into load:  
focus on trying to get as close as possible to  $Z_L = Z_S^*$


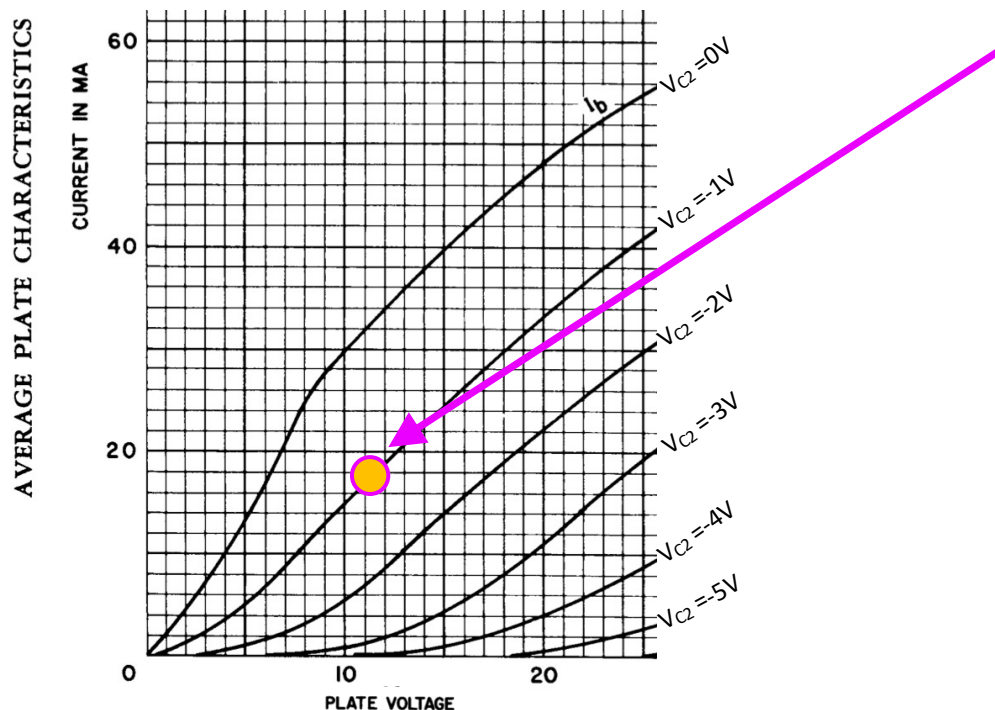
# What is our Output Impedance?

- That is the same as our Plate resistance  $r_p$  we could use the estimated numbers from the data sheet but those are for a particular point in operation. Let's go to the truth (the curves!)




- At whatever point we operate at, the slope will give us our output impedance (or the inverse or it)
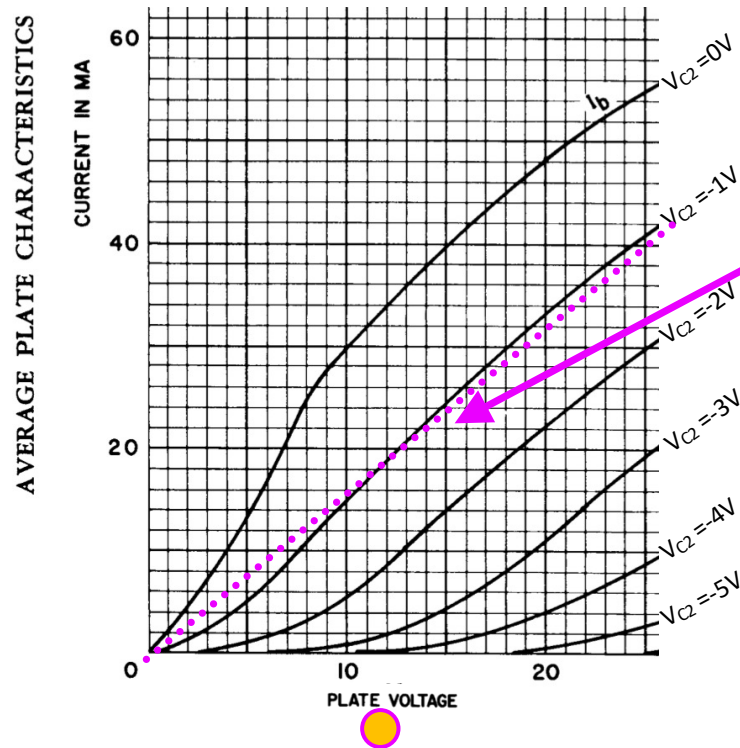
# What is our Output Impedance?


- It is varying but a rough estimate in this area of curves:

$$R_S = 1 / \frac{\Delta I_b}{\Delta V_b} = \frac{25V}{40mA} = 625\Omega$$


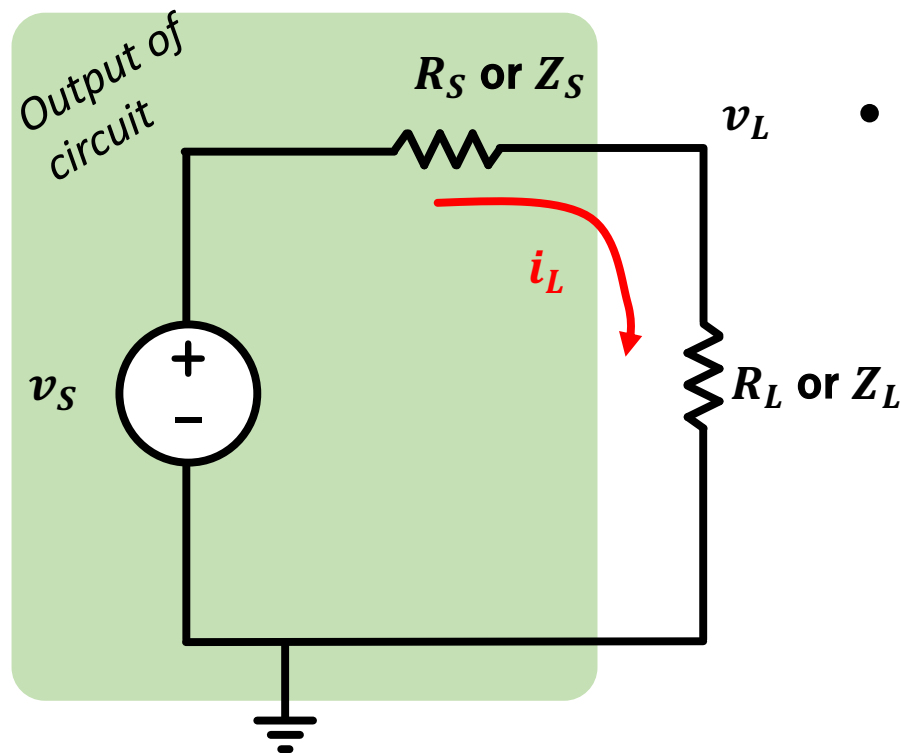
# We need a better impedance

- So currently  $R_S = 625\Omega$  and  $R_L = 8\Omega$
- That is quite a mismatch




- If only there resolve this conflict.
- We need an ombuds component


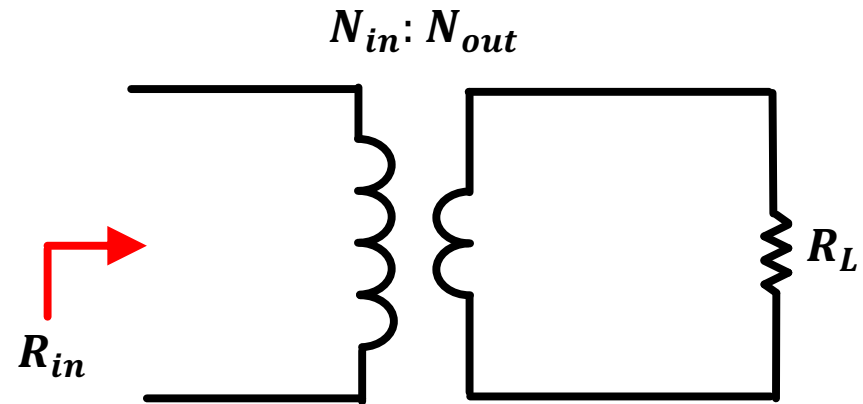
# Use a transformer to Impedance Match


- We've already seen that a transformer can alter the effective impedance seen by a device.
- Let's use one here. We want to make a low-Ohm speaker look like a higher-Ohm device.  
How to do



$$\text{So therefore: } R_{in} = R_L \left( \frac{N_{in}}{N_{out}} \right)^2$$

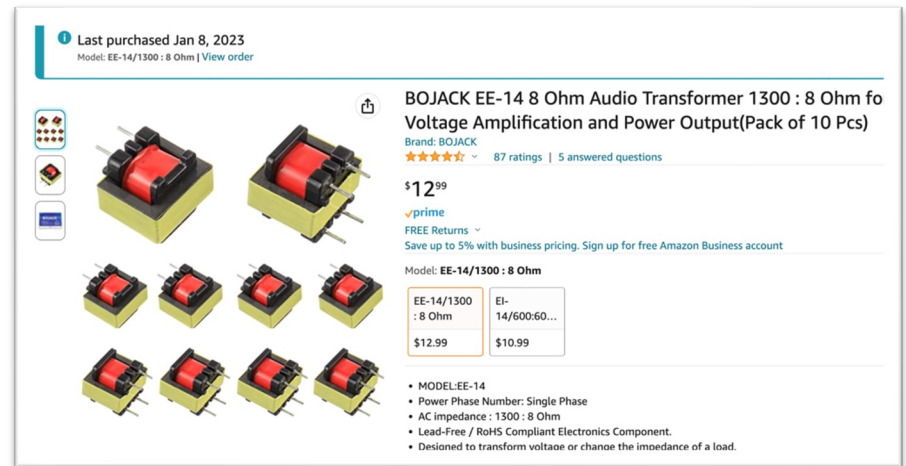
# A common problem

- This is needed quite a bit
- So I tracked down some transformers that are advertised to have a coil winding ratio such that it can make an 8 ohm look like a 1300 ohm
- Not exactly what we need, but not awful and gets us closer... (the load and source are same orders of mag now)
- For sake of argument, let's say this is really a 8ohm:1000 ohm transformer...which is another common model you'll see



*They don't even list the winding ratio since that's not what we care about and we're lazy...they just do the math for us, but it could be backed out...roughly a 13:1 ratio*

So we have this

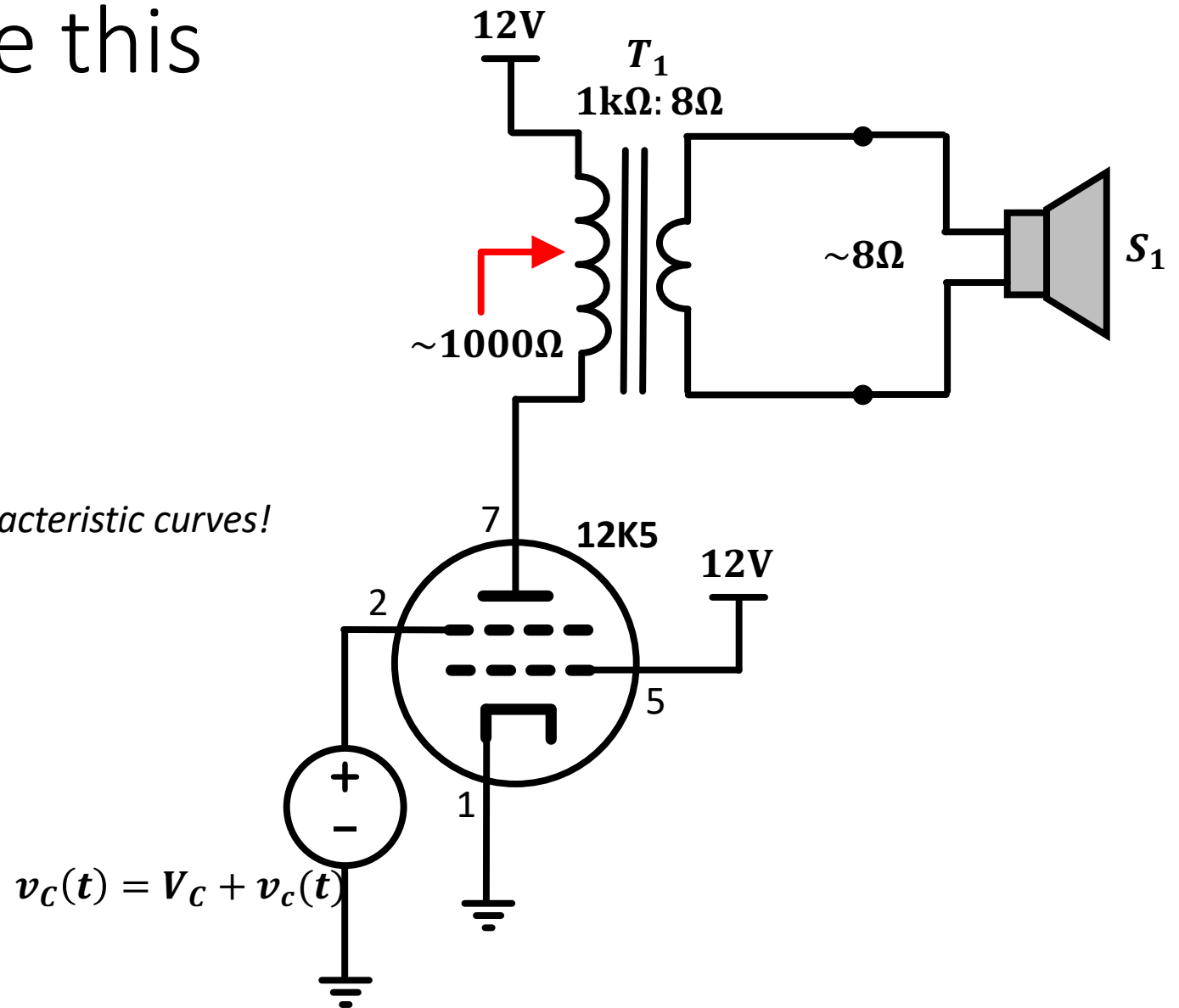


# We are Driving an impedance-matched speaker.

- Load Line:

$y(i_B)$ -intercept will be:
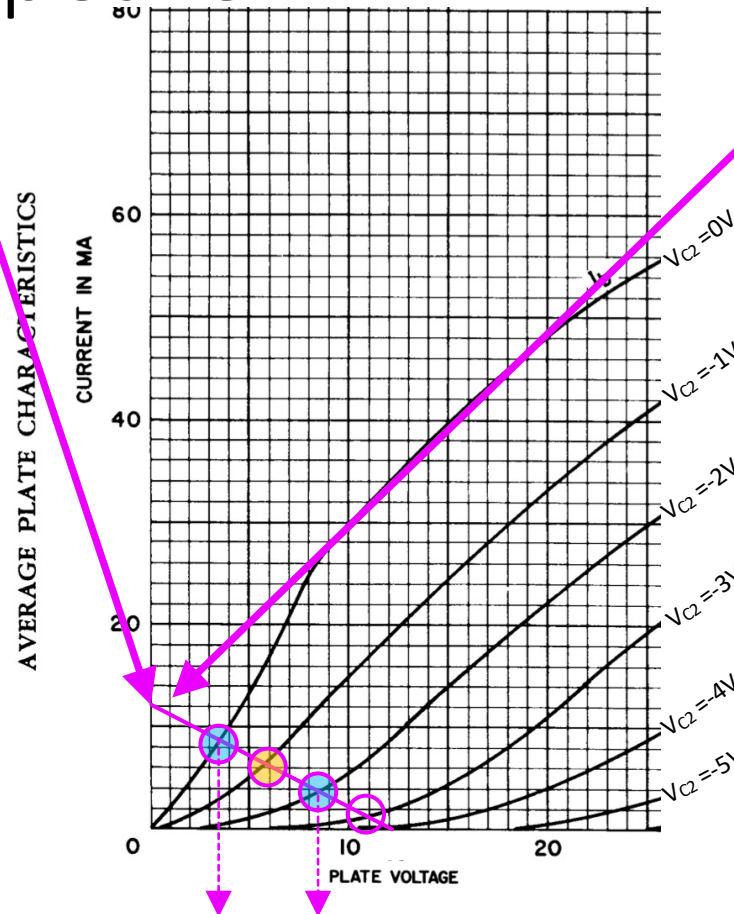
$$12 \text{ mA} = \frac{12\text{V}}{1000\Omega}$$



$$\Delta V_b \approx 8.5\text{V} - 3.5\text{V}$$

Slope is  $-\frac{1}{1000}$   
This thing is essentially vertical

At the bias point of -1V for the grid,

$$A_v = \frac{\Delta V_b}{\Delta V_{C2}} \frac{8.5\text{V} - 3.5\text{V}}{-3\text{V} - -1\text{V}} = -2.5$$

**IS THIS OK?**

**Iunno this is just a number**

# How much power is delivered to load?

- For a  $2V_{pp}$  input sine wave, we get out a  $5V_{pp}$  sine wave into an 10000 Ohm Load
- A  $5 V_{pp}$  sine wave has an amplitude of 2.5 V
- A sine wave with amplitude 2.5 V has an  $V_{RMS}$  of 1.76V
- Power delivered to 1000 Ohm load from this signal is  $P_L = \frac{V_{RMS}^2}{R_L} = \frac{1.76^2}{1000\Omega} \approx 3mW$
- Assuming all the power delivered to the transformer goes into the speaker (reasonable assumption) , that means we're delivering way more power!



IS THIS OK?

5 TIMES THE POWER! OH YEAH\*

\*and we're not even that well matched...if we really cared we'd make our own transformer
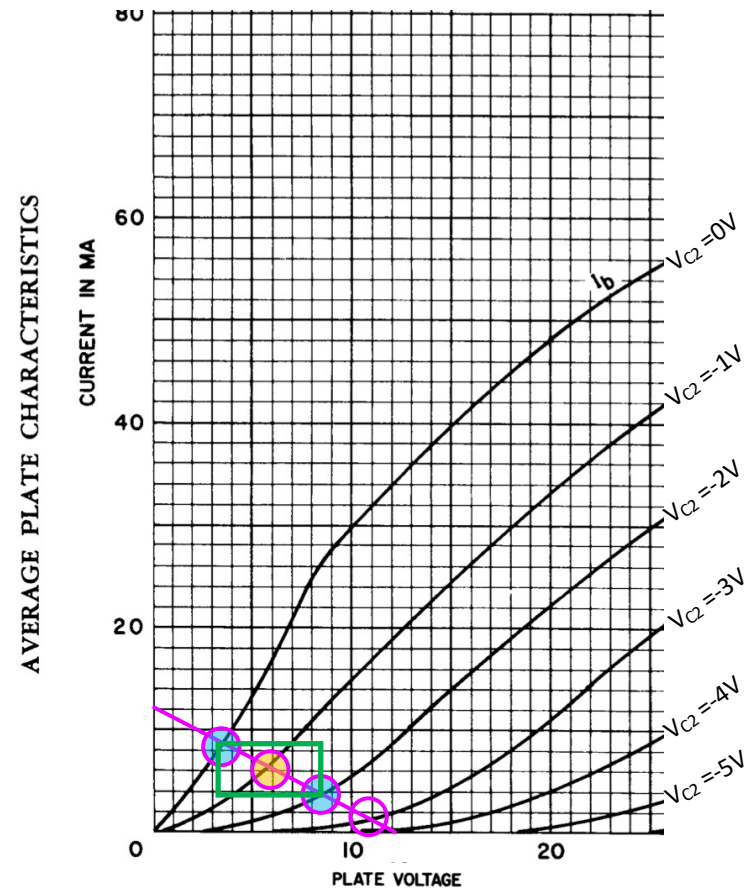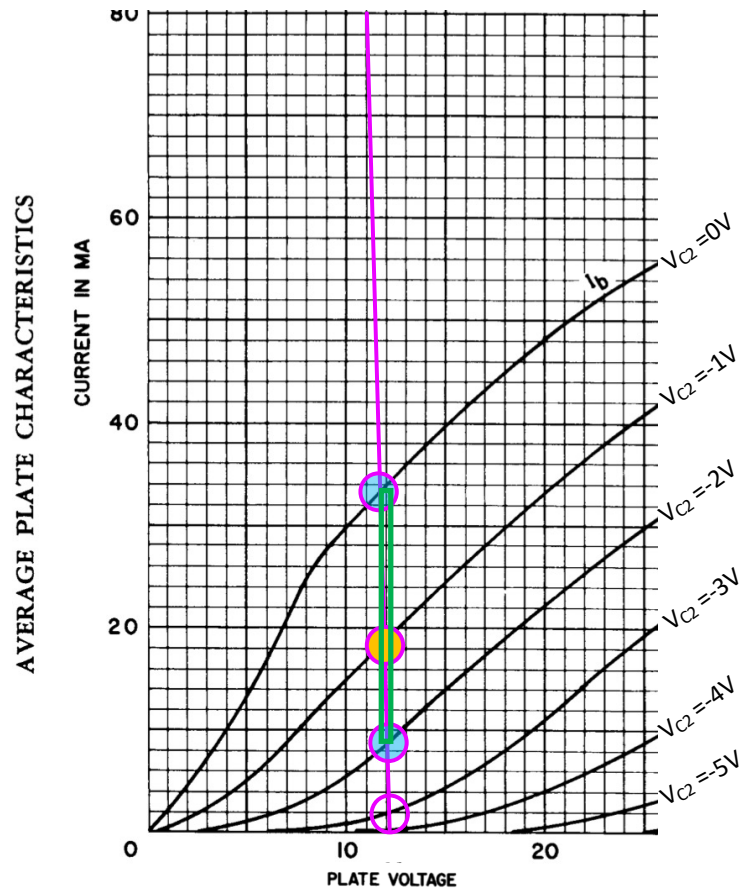
# Interesting


*If you draw rectangles over the sweep sizes for both situations, the impedance matched rectangle has a much larger area, indicative of a much larger power transfer*



# OK Gotta bias this last stage

- Let's do cathode biasing.
- Current will be in the 10-ish mA region
- Let's put a trimmer pot of  $\sim 100$  Ohms on cathode
- This should nudge  $V_{\text{cathode}}$  to around 1V
- So  $V_{\text{grid}} - V_{\text{cathode}}$  will be negative -1V
- Also, like before, put big juicy cap in parallel to short the cathode resistor at audio frequencies so it doesn't eat into our audio swing
- And put a grid stopper resistor for some filtering


Done:

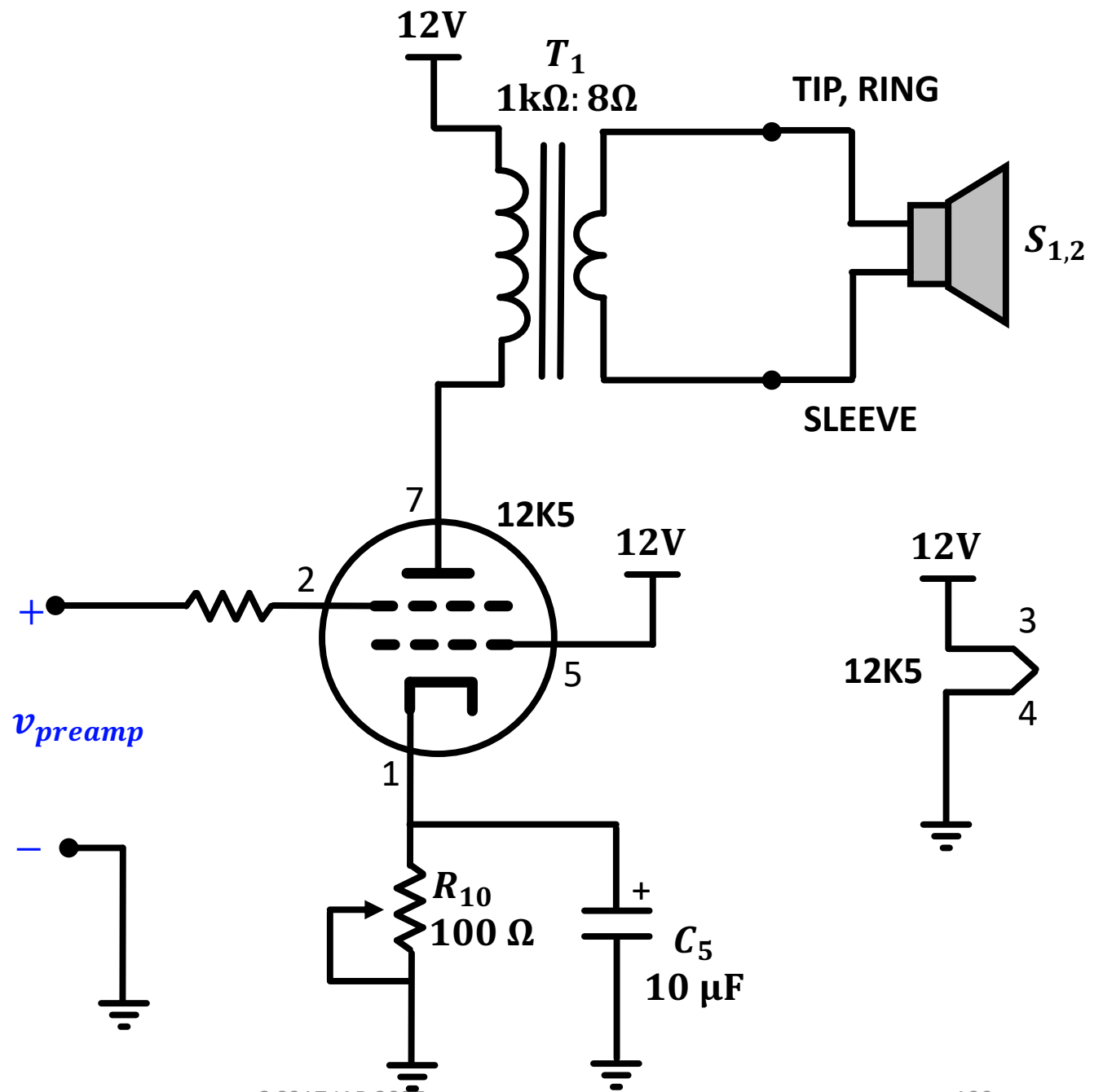


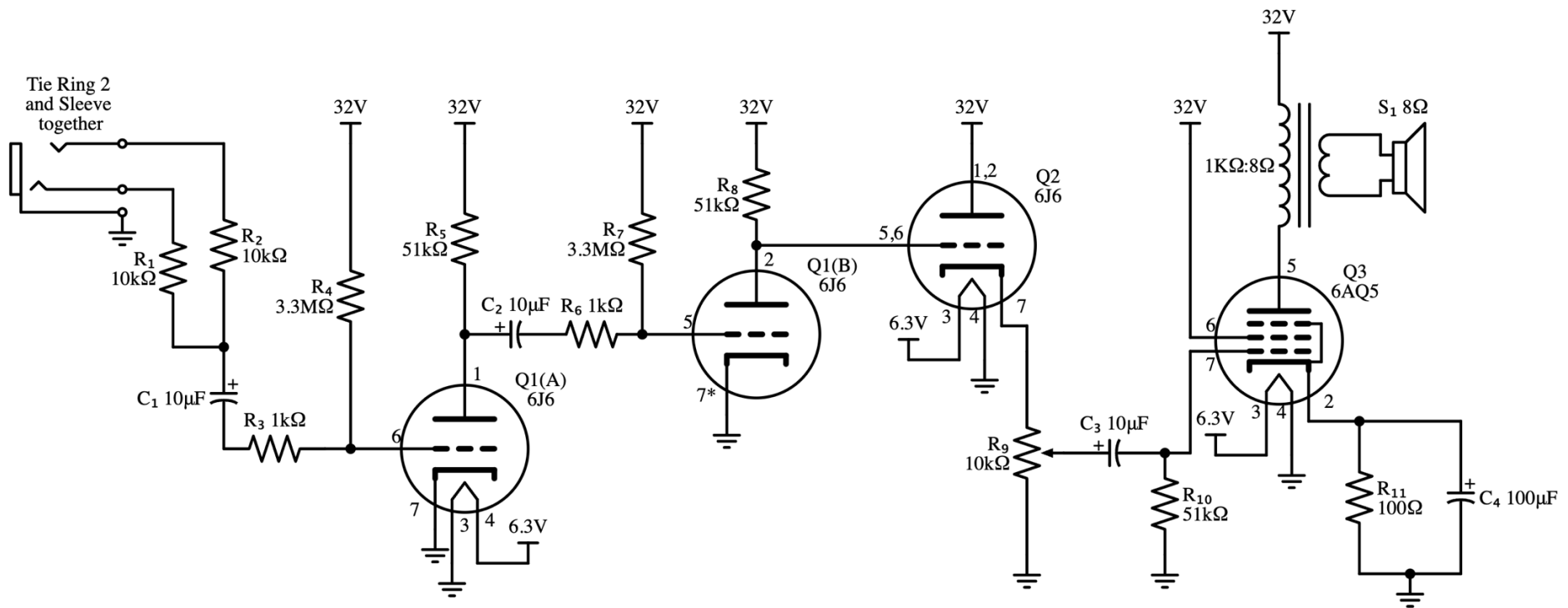
# 2025 Lab 5 is a bit different

- The circuit uses different tubes, but covers a lot of the same topologies just discussed




# 2024/5 Tube


- 6J6. Got a couple unopened trays of a hundred for chump change
- 6AQ5's got a bunch also for next to nothing




# Power Supplies!

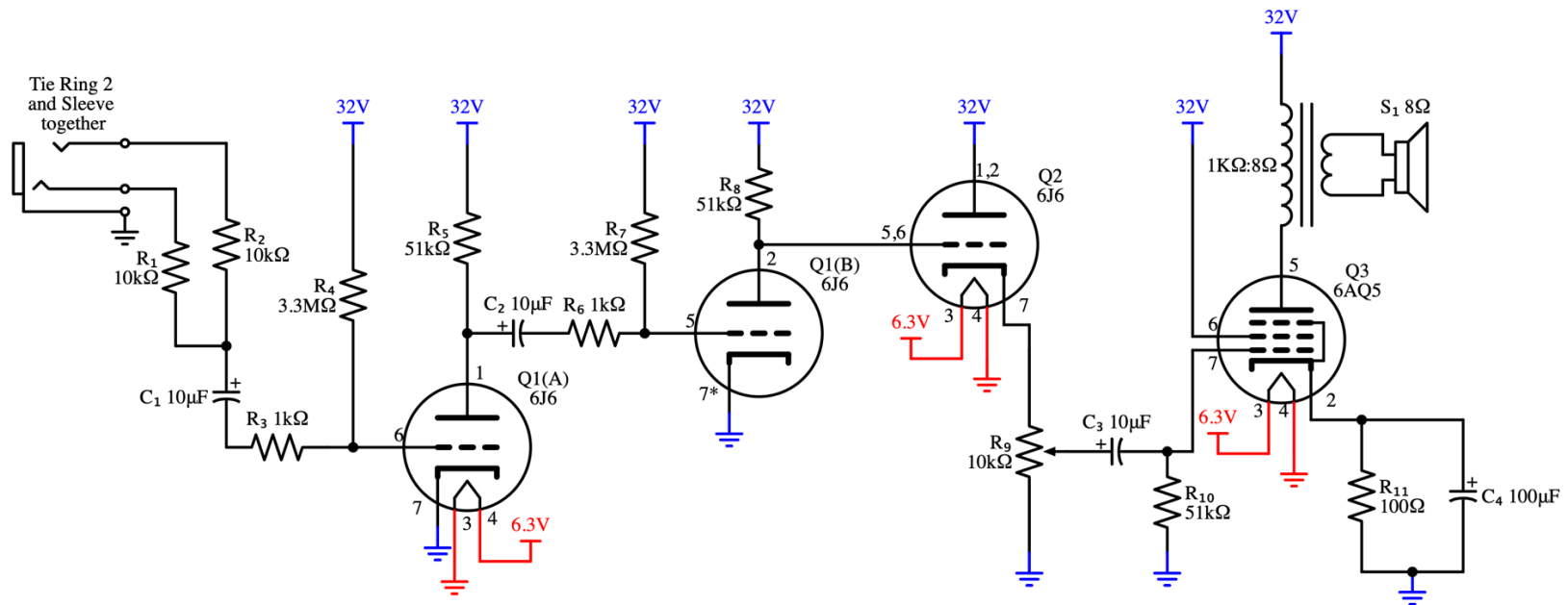


# Input

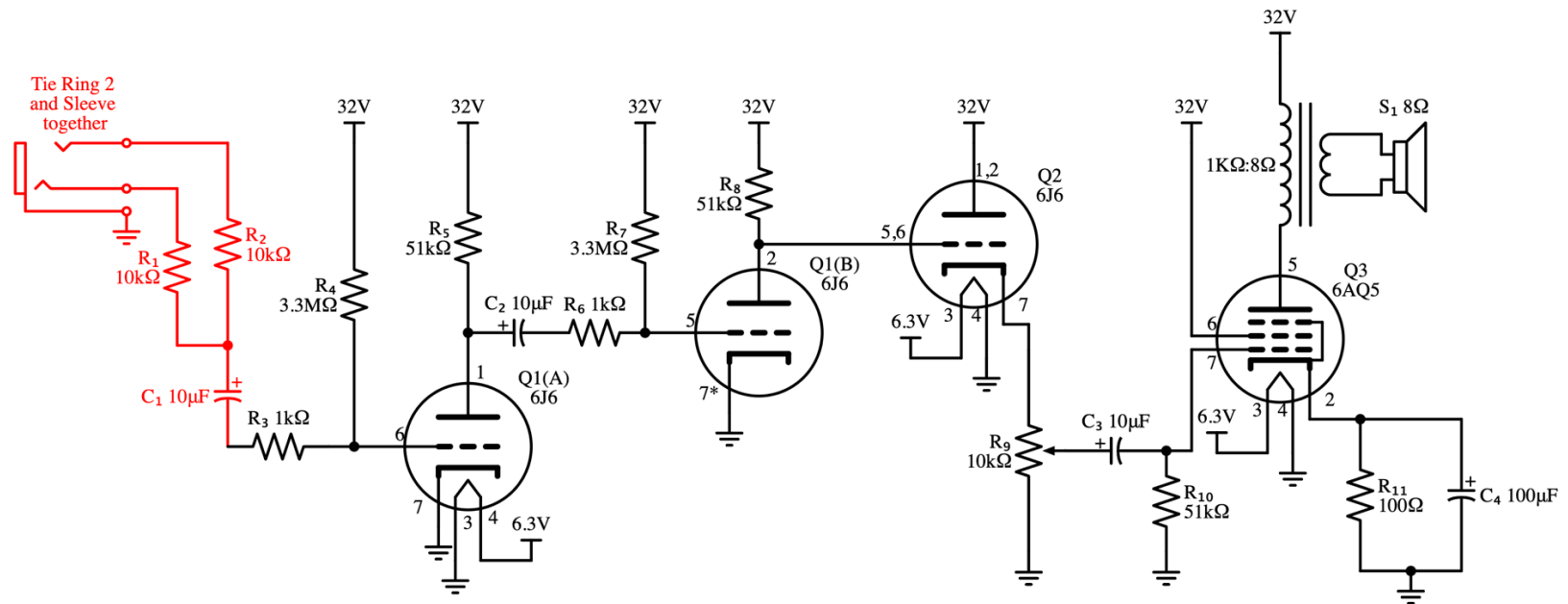


# Stage 1: Voltage Gain

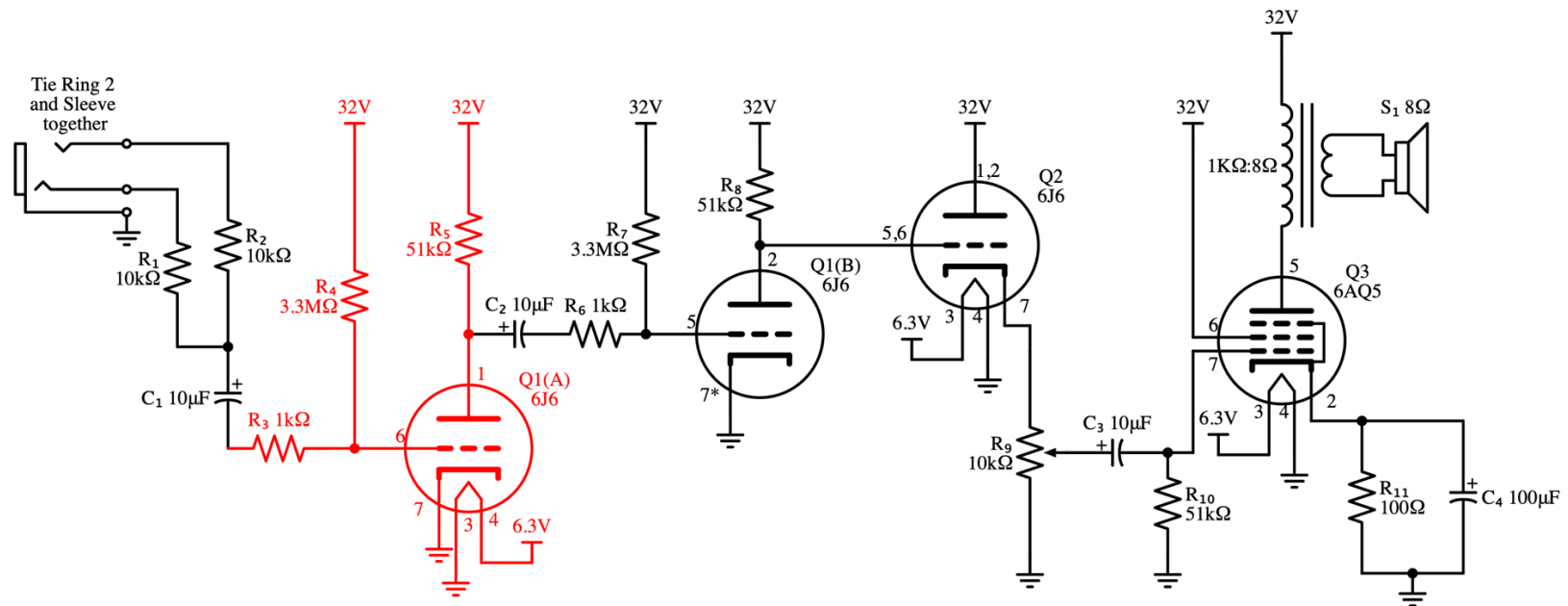


# Stage 2: Voltage Gain (More)

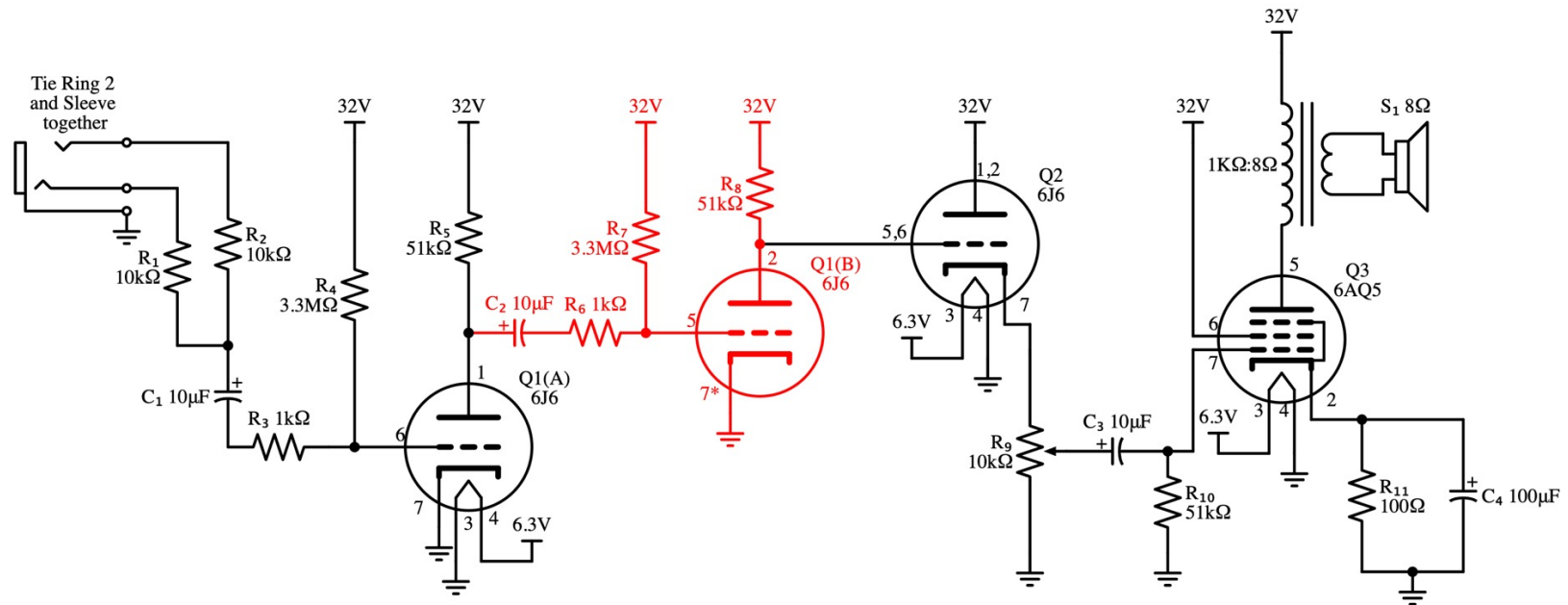

## Stage 3: Buffer (cathode follower)

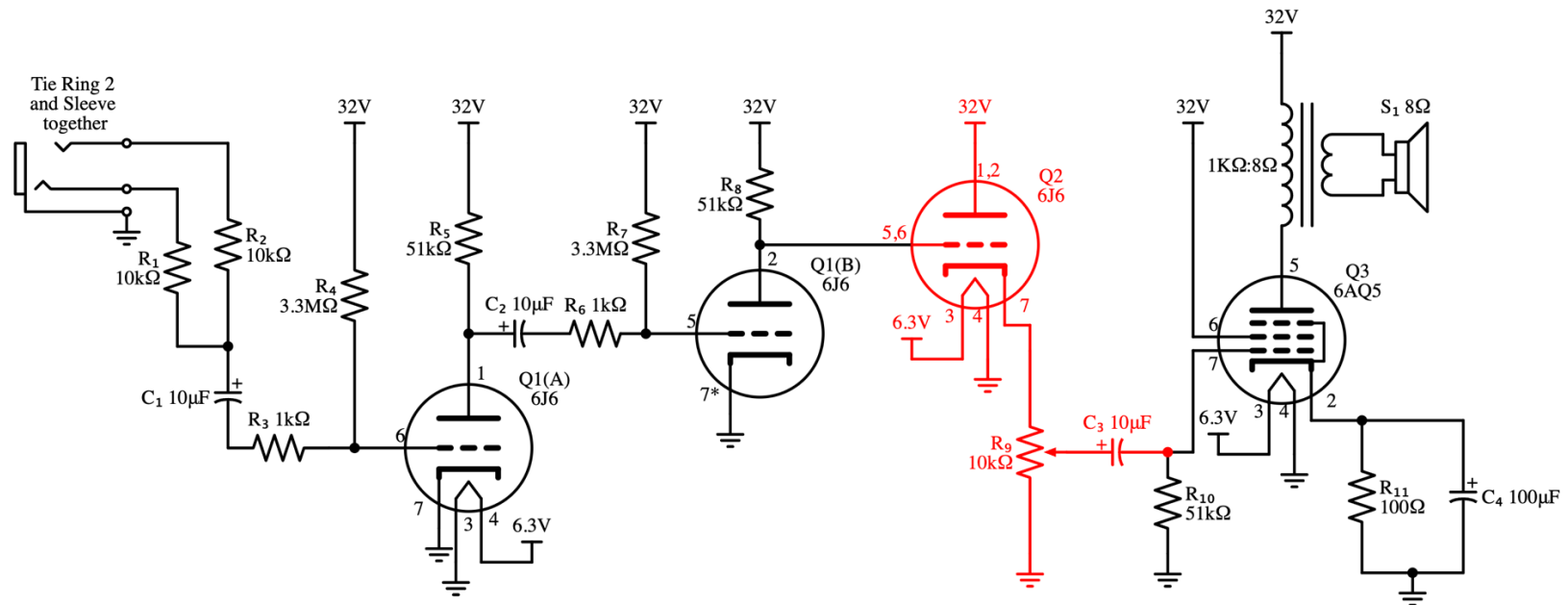

# Stage 4: Power Amplifier

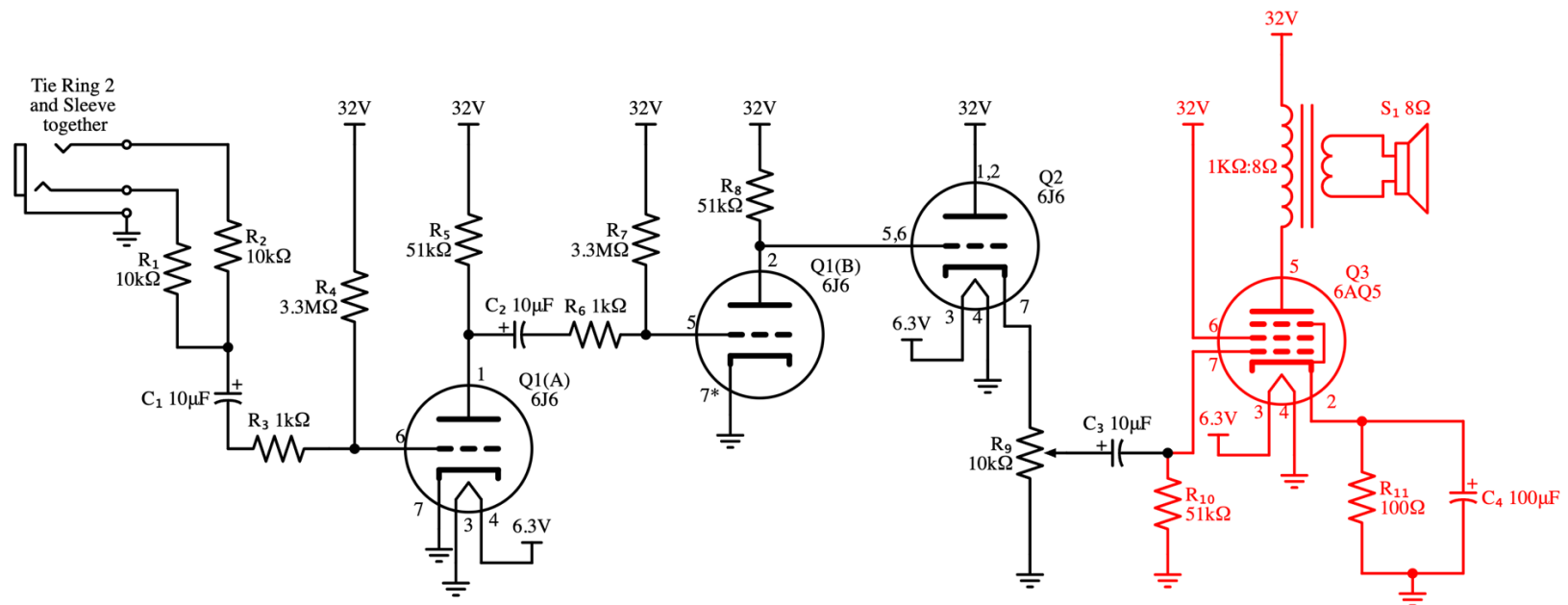



# Coming Up #2

- In next lecture:
  - Look at triode failings
  - Look at new tube types and what they brought to table
  - Revisit Tetrodes and tubes with the weird I-V curves
  - Continue to move through history