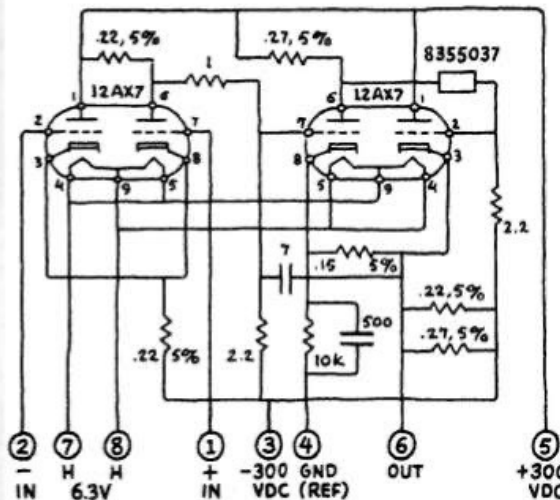


# Lecture 6


## Tube and Early Transistor Electronics
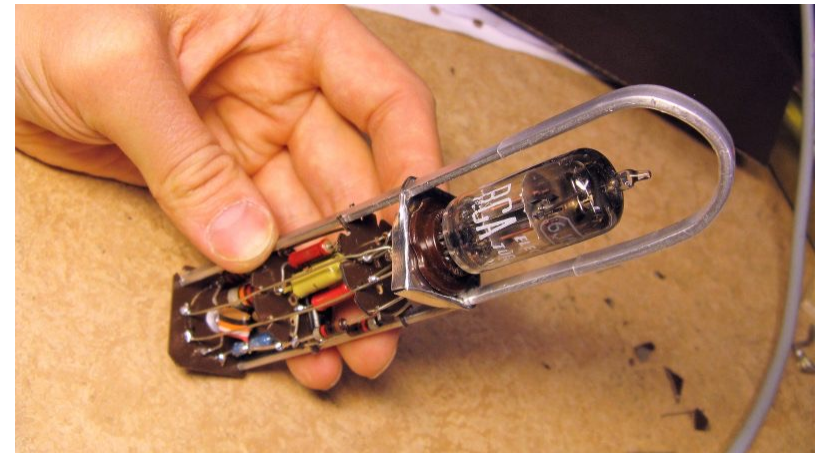
# We Did A Lot With Tubes

- Most modern designs started with tubes.



The first commercial  
Operational Amplifier




Triode-based Flip-Flop  
From IBM 605



<https://www.talkbass.com/threads/tube-op-amps-experience-interests.1215611/>
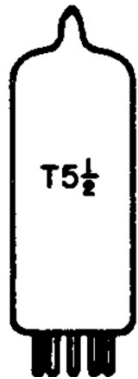
# 12CN5 12V Pentode Tube

- We'll use this in the end of lab 05 and 06 to make an oscillator (Abraham Bloch circuit) and then an early op amp
- It acts pentodic at low voltages!



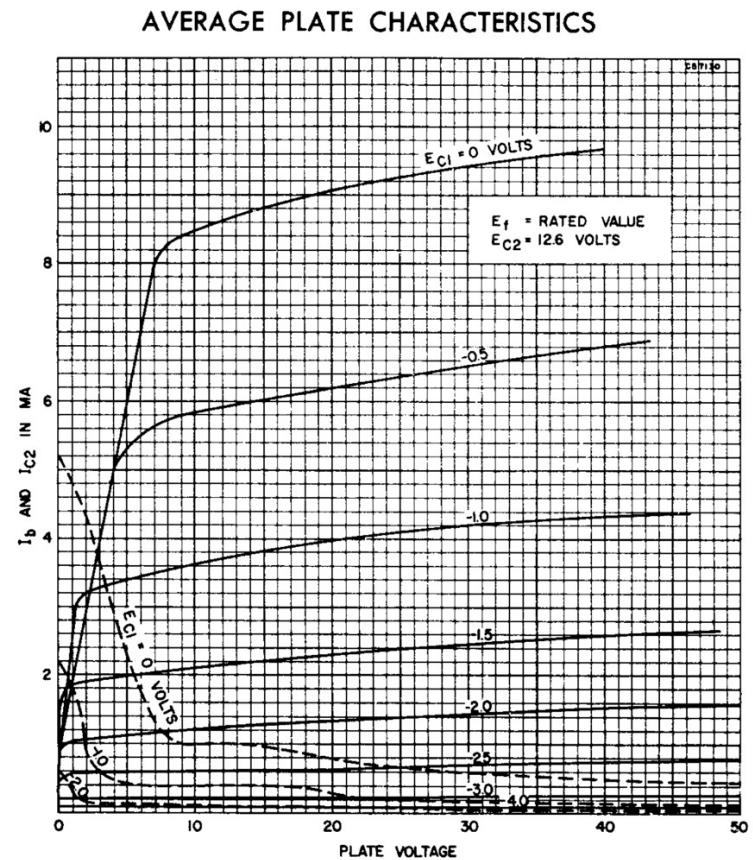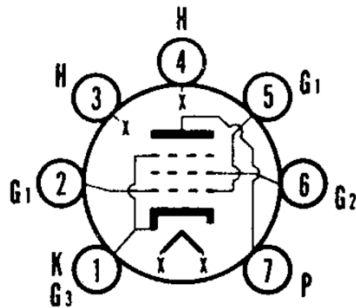SYLVANIA TYPE **12CN5**  
SHARP CUTOFF PENTODE



# The “soft-clipping”

- The fact that triodes **don't** transition very abruptly is one reason why people really like assign “good” sound effects to triodes.
- They tend to not “clip” as hard because they very gradually turn on and off at the extremes of their operating range whereas pentodes (And later transistors) have very clearly defined ON/OFF regions





# Conclusion

- Triodes Make Lousy Switches *especially when we are running them in low voltage starvation mode*
  - You can get that behavior out of them with the right conditions, but they are not very good “switching”-style amplifiers because of their I-V relationships
- Pentodes, on the other hand can be pretty good switches if you can position your bias point operation so that you’re jumping between the two regions of operation

# The Bistable Multivibrator

- This was also discovered/developed right around 1919 by Eccles and Jordan
- Originally termed “trigger circuits” but they eventually became known as flipflops



Essentially just two NOT gates

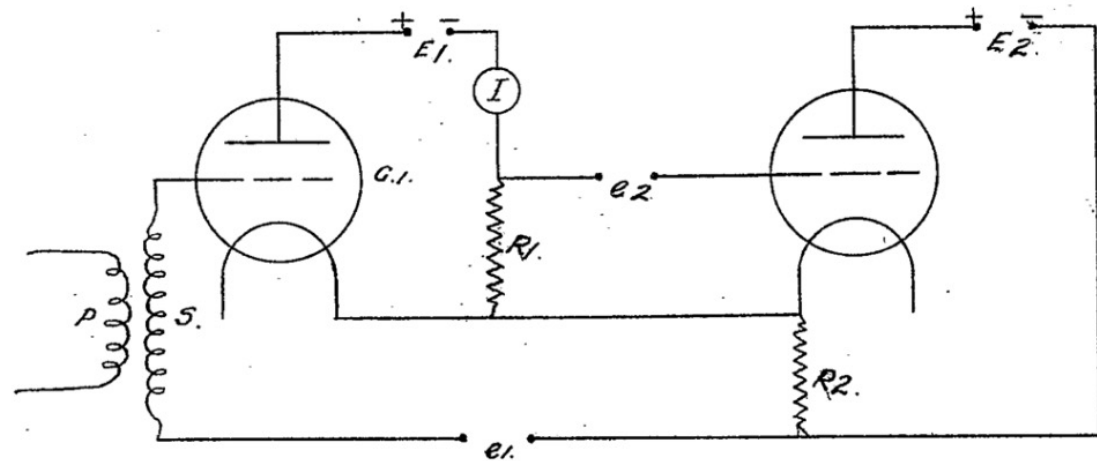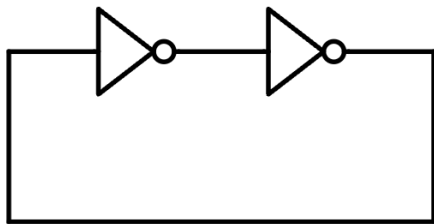

*The original Eccles Jordan*

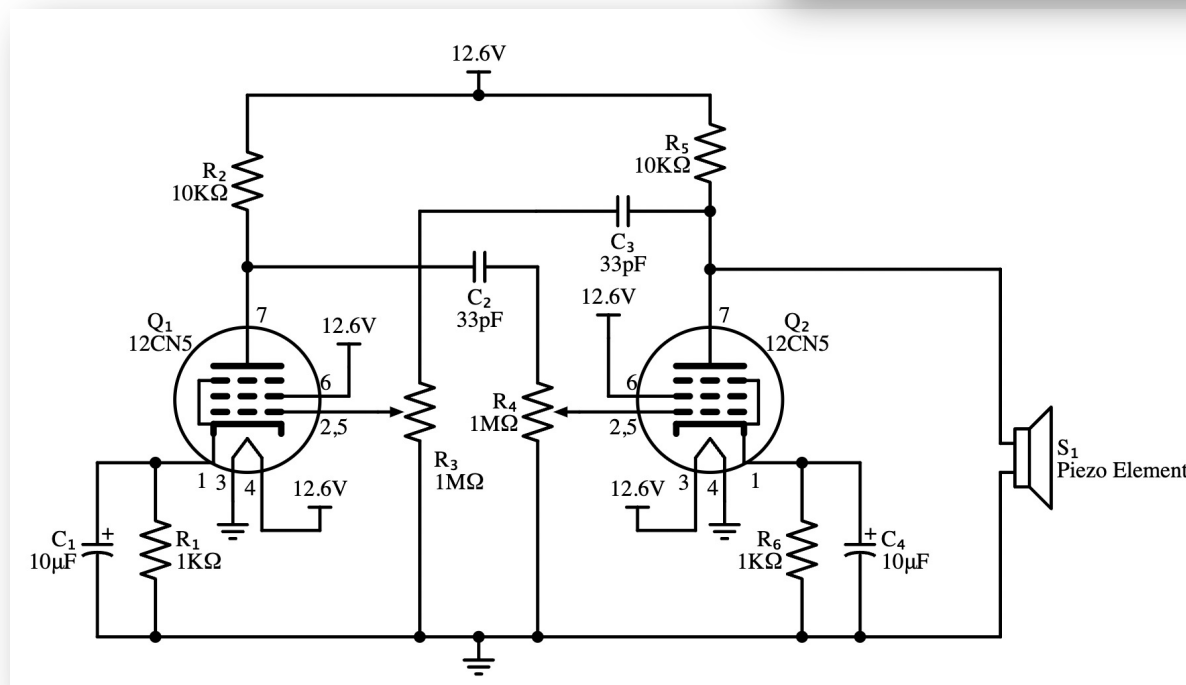
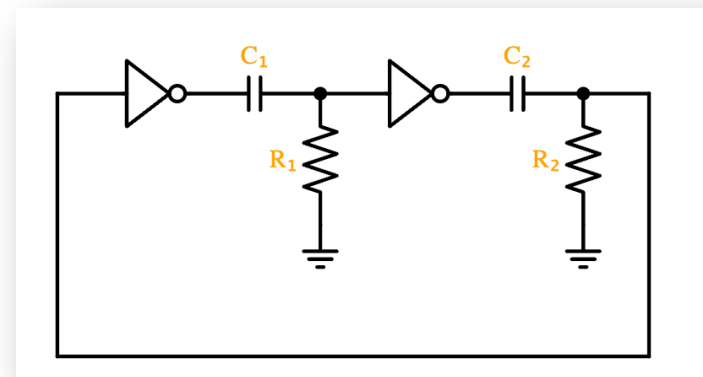
# Abraham Bloch Circuit (Lab 05)

- Two inverters connected with high-pass filters...inherently unstable
- Will oscillate



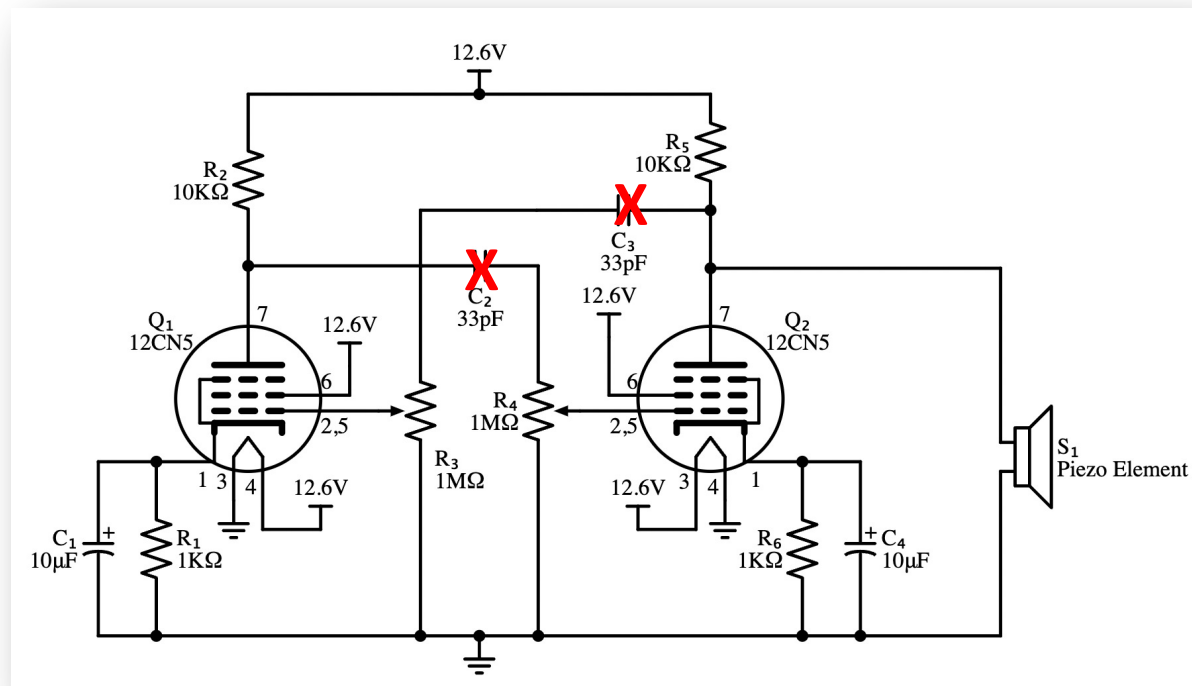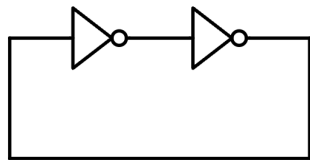
# The Eccles Jordan Circuit

- Almost the same as the Abraham Bloch circuit just replace the capacitors with wires which introduce the high-pass-filter behavior...that allows the circuit to have two long-term stable positions instead of none (which causes the oscillation)


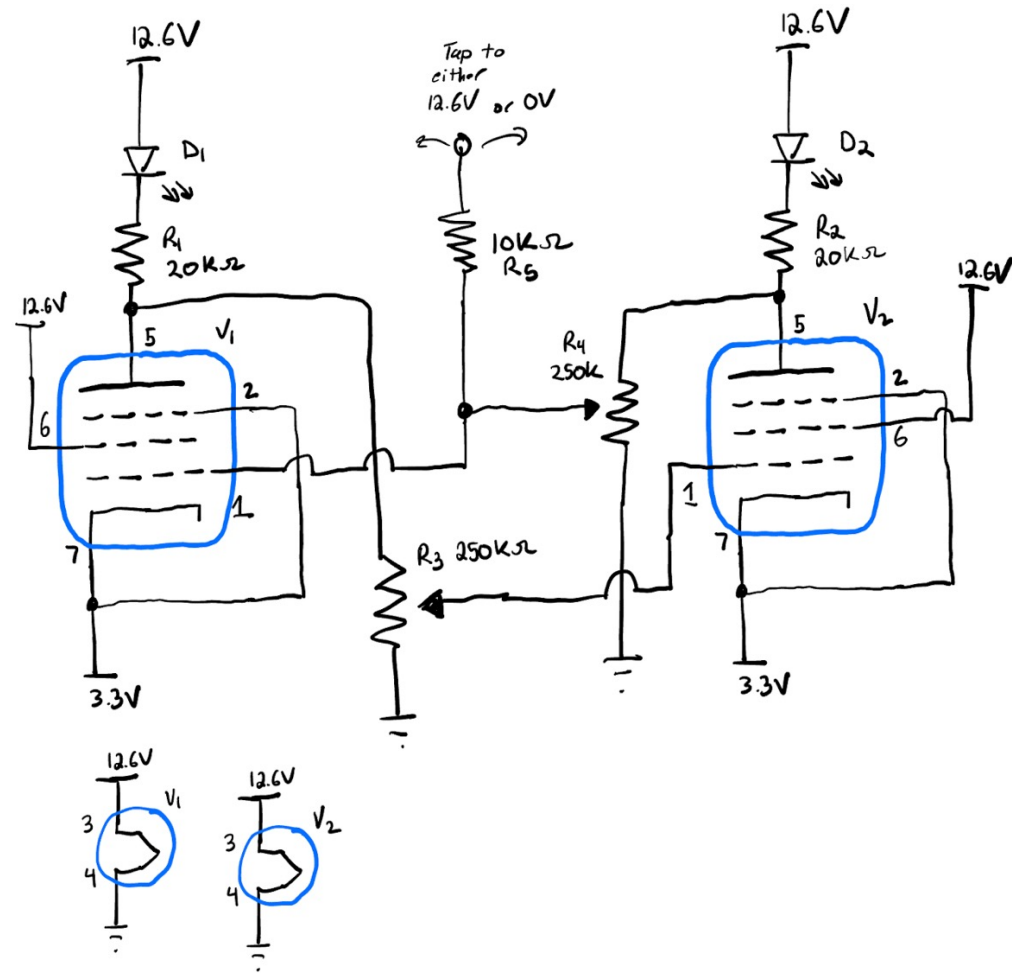
# Instead we'll Build the Flipflop with Pentodes


- Using the 12CN5 tubes you can in fact make a 12V stable flip flop



Sorry didn't lay this out in my pretty schematic drawing software

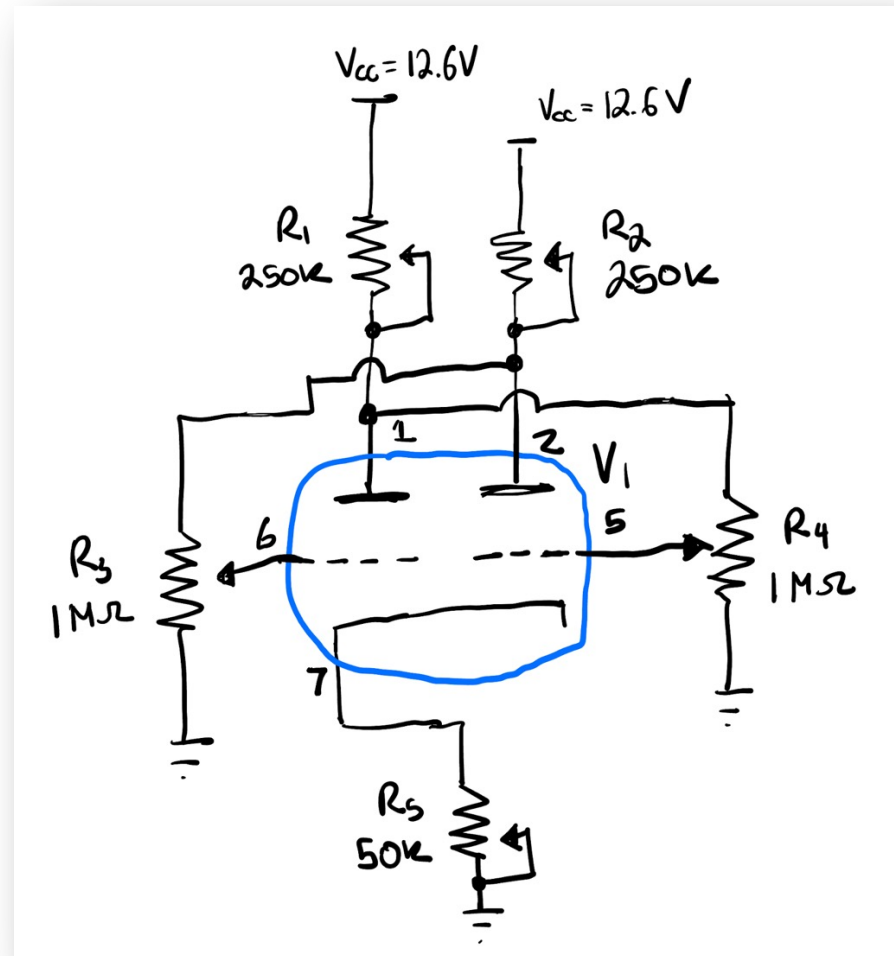
# Can we do this with our Triodes?

- Could we make a bistable flip-flop circuit using just a triode?




In theory should be relatively easy to implement something like this:

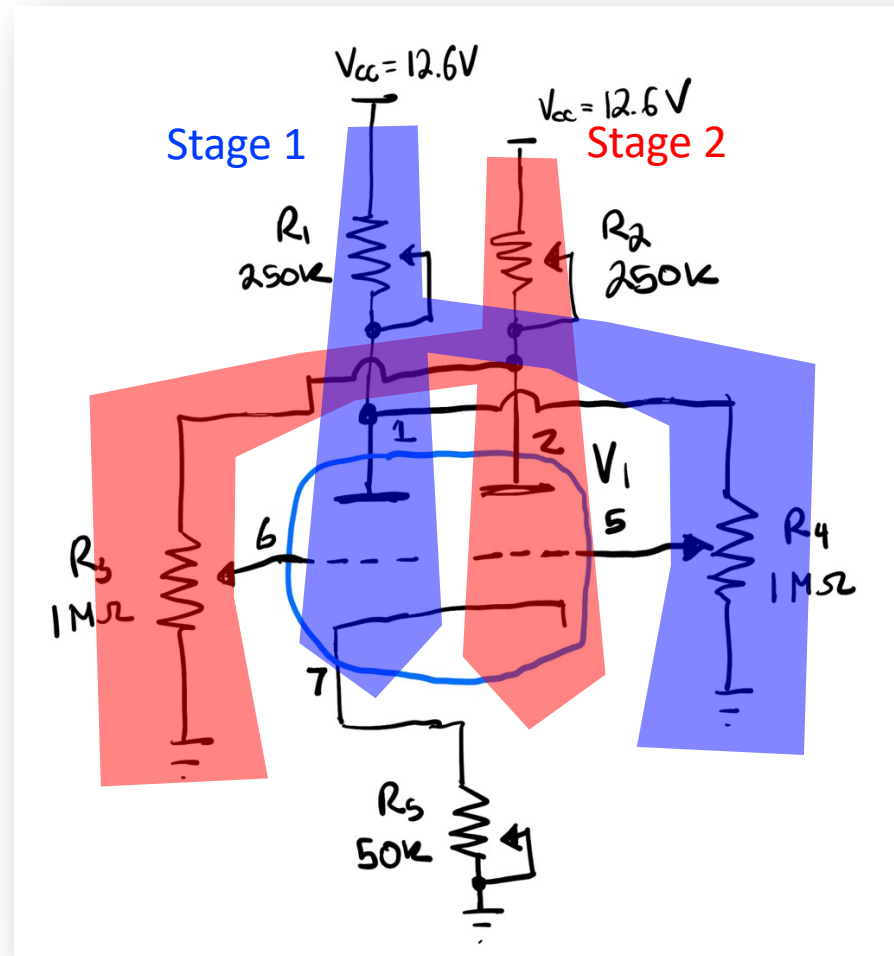*The "high" output of this stage 1 provides a "high" output to stage 2 which causes stage 2 to have a "low" output which is a "low" input to stage 1...which...*


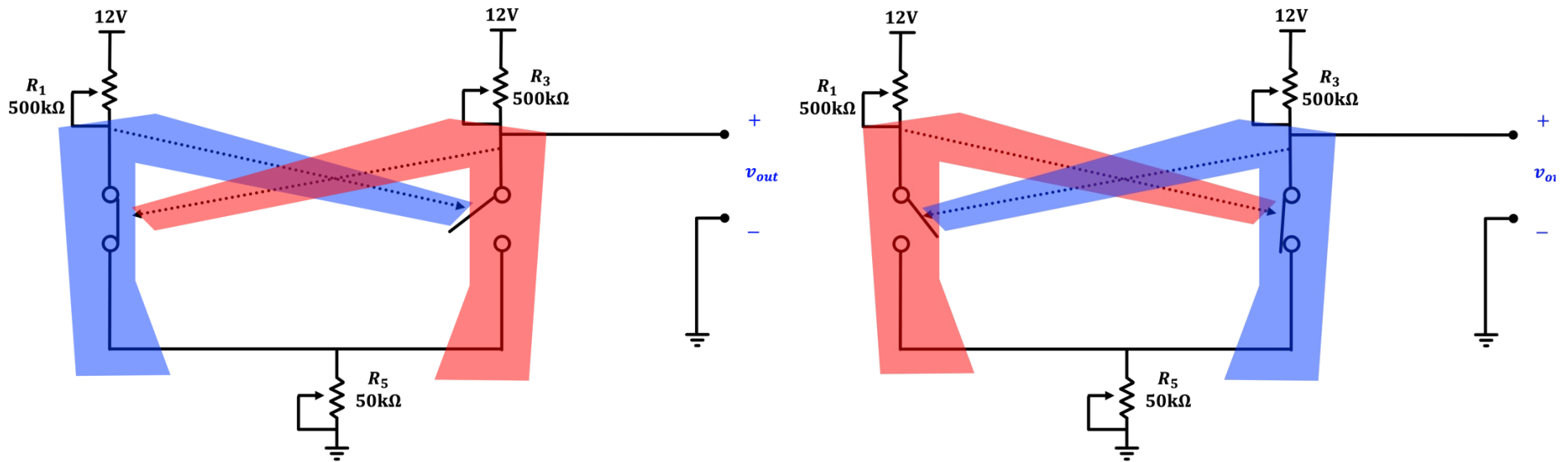
# A Bistable Circuit


- In order for a Bistable circuit to work reliably the active devices need to act more “switch-like” than “amplifier-like”.
- Doing so will give a much cleaner behavior that’s also more digital:





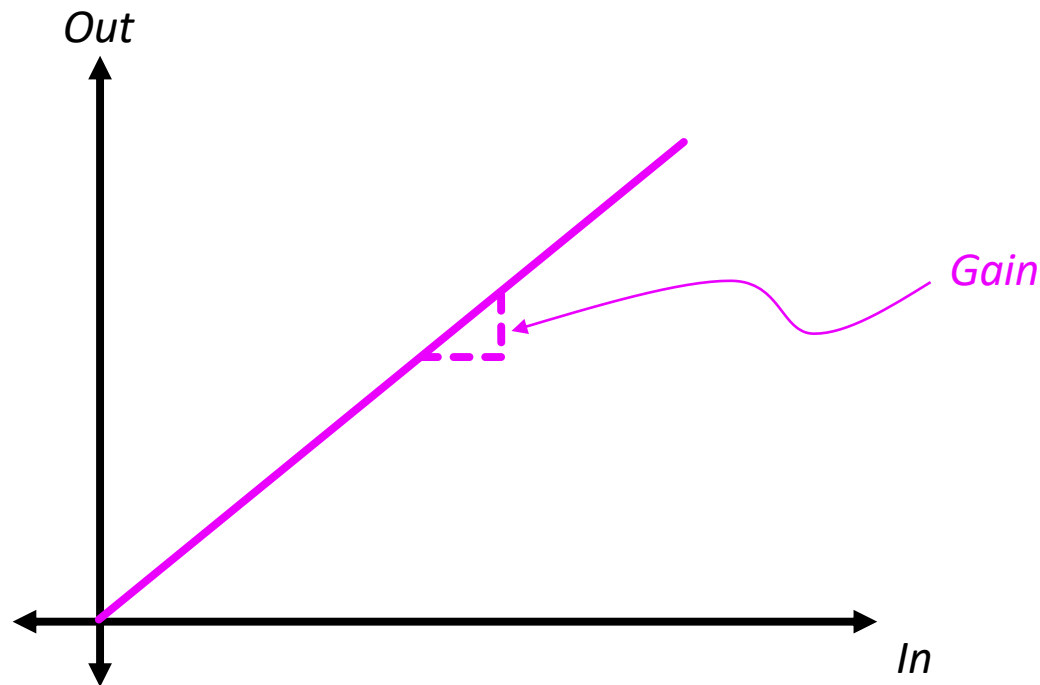
# For a Analog Amplifier...

- We generally want a nice, linear in/out relationship
- Ideally the In/Out relationship is predominantly linear


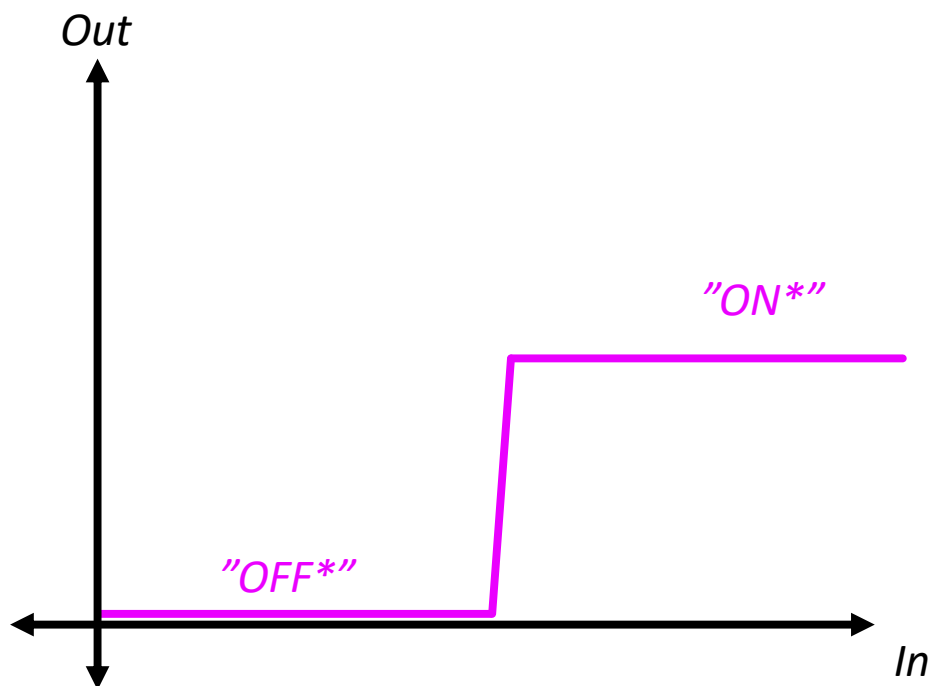
# For a Digital Amplifier...


- We want an amplifier that is over-driven and/or saturated
- Something that clips ideally at both ends of its extremes
- Something that is best described by an if/else or piecewise function




- In the case of a flip-flop we really want something to work that way
- The more non-linear, the better and more stable it will be
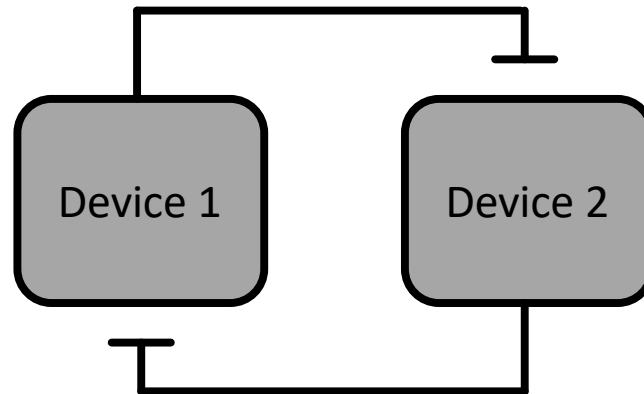
# A Jordan-Eccles Circuit (Bistable Flip-flop)

- Built around the idea of two active (amplifying) devices mutually suppressing one another.




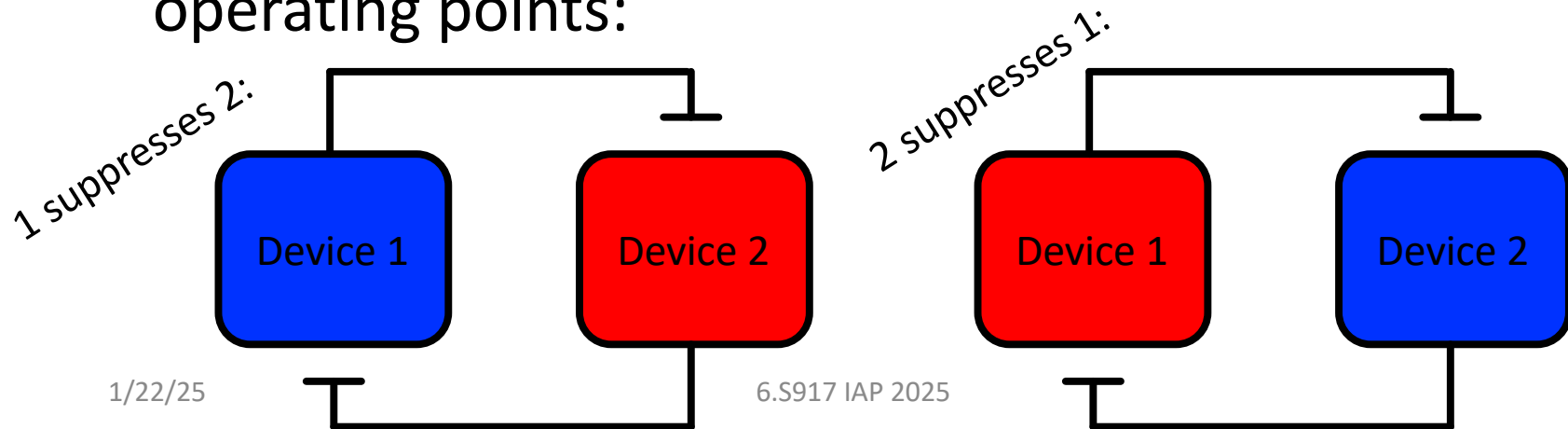- When tuned, the circuit will stabilize to one of two operating points:




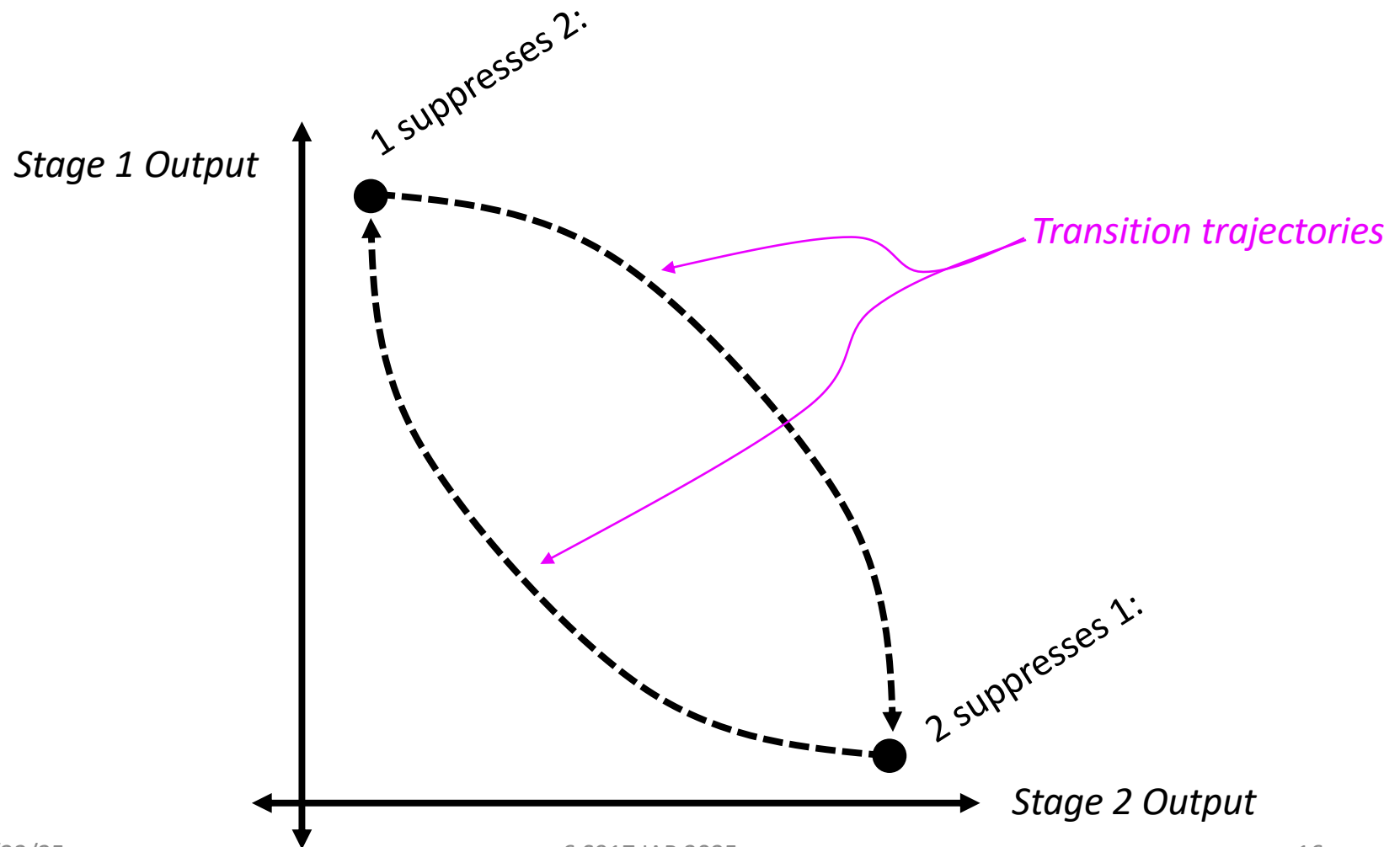
# Map of Stability



- If the two sides can turn on/off very sharply, you can get a very clear map of two stable points



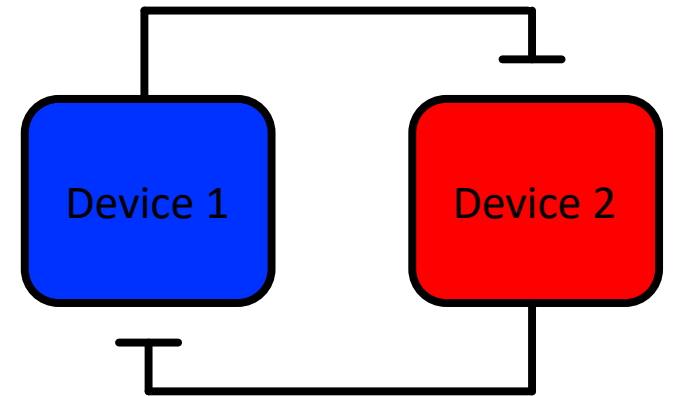
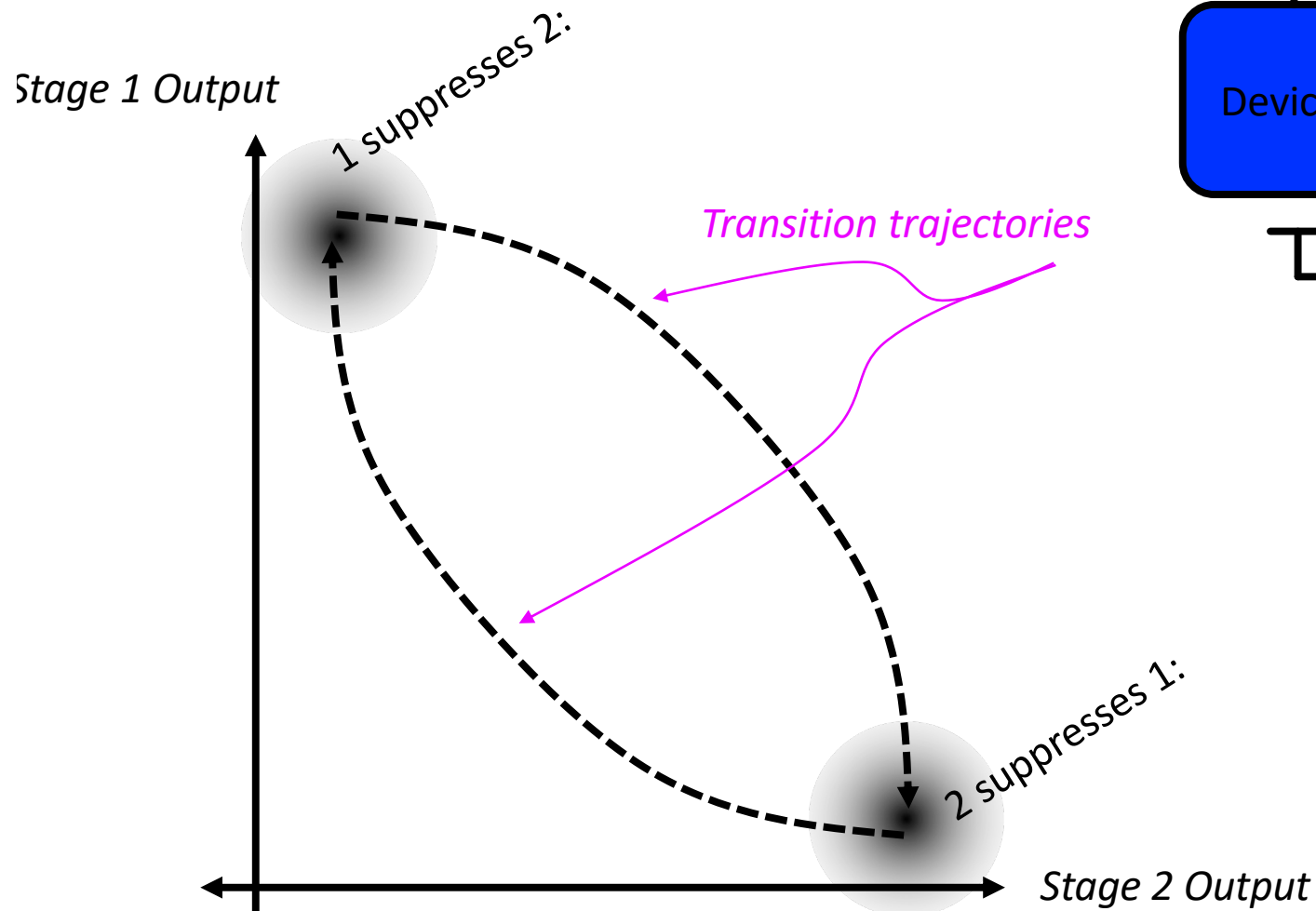
# The Less Switch-Like Our Amplifiers Look, the Less Ideal Our Stability Map Will Become...



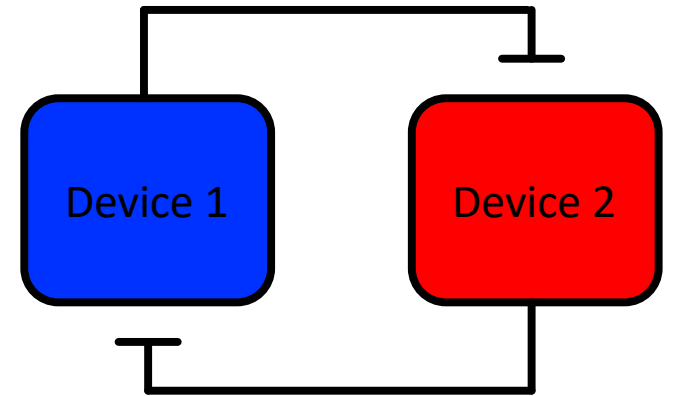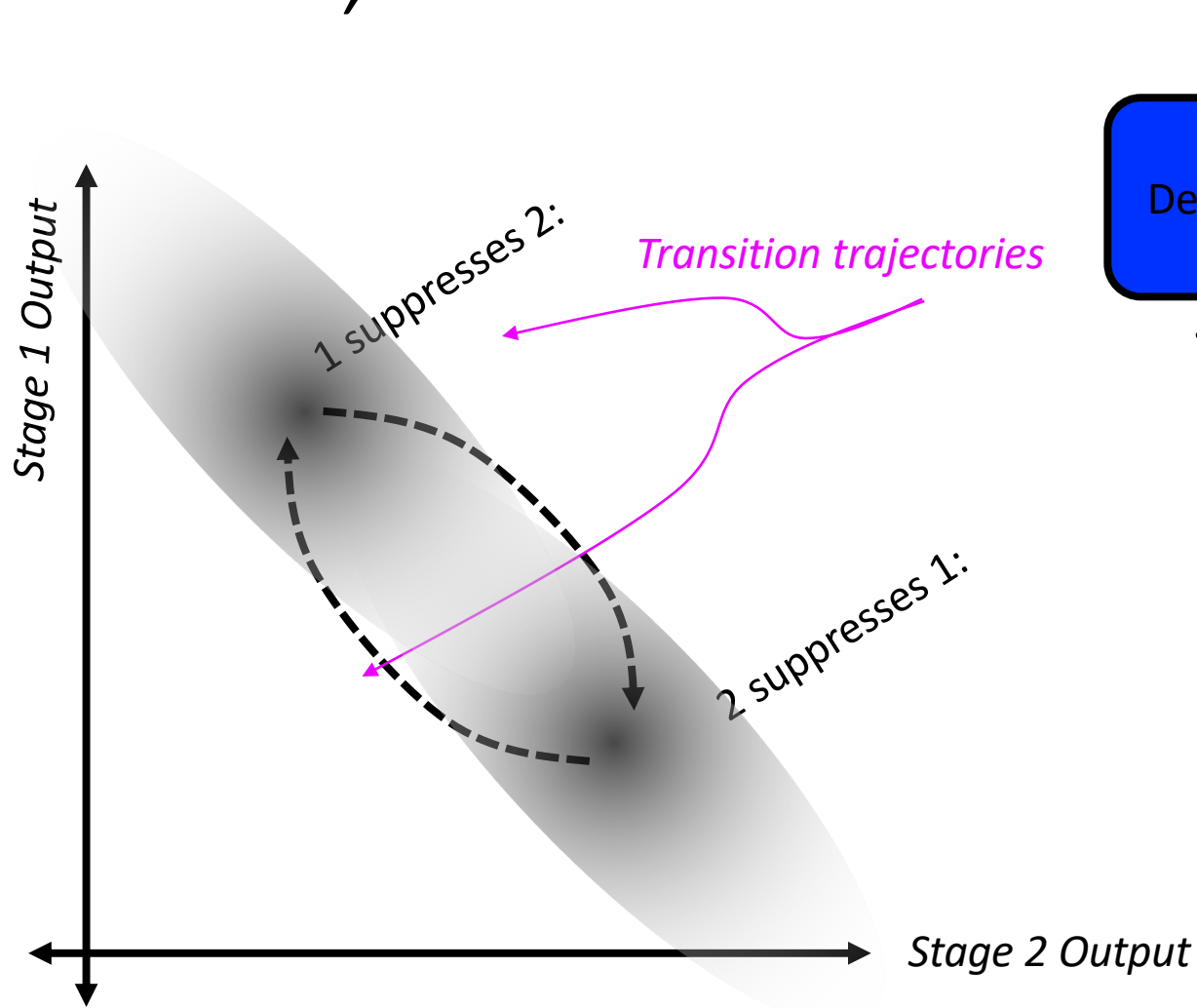If Our amplifiers *really* can't act like switches, then...





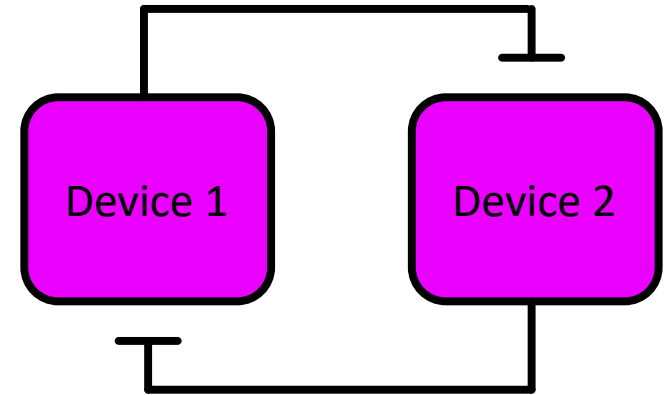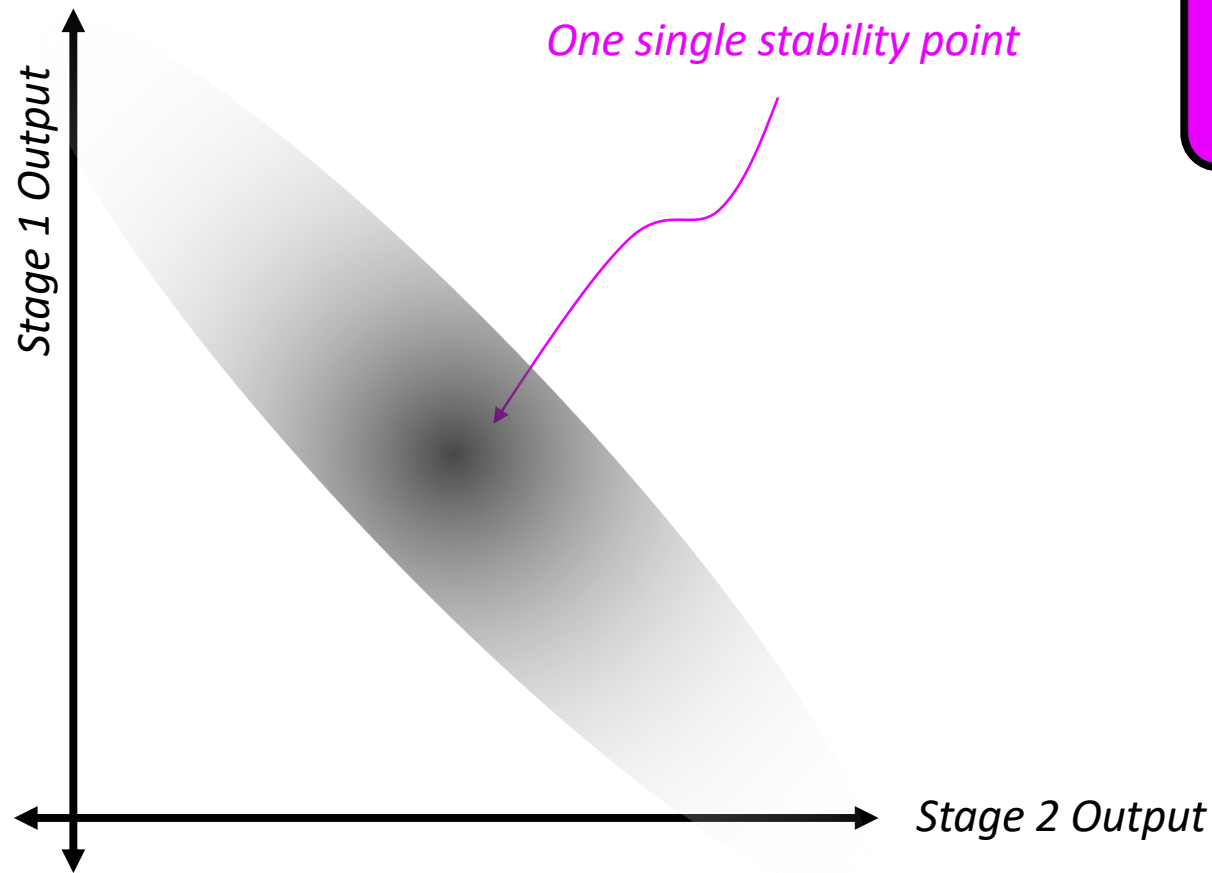
# If they really really can't act as switches, then...



# Can Our Amplifiers Act as Switches?




- Consider the Triode:

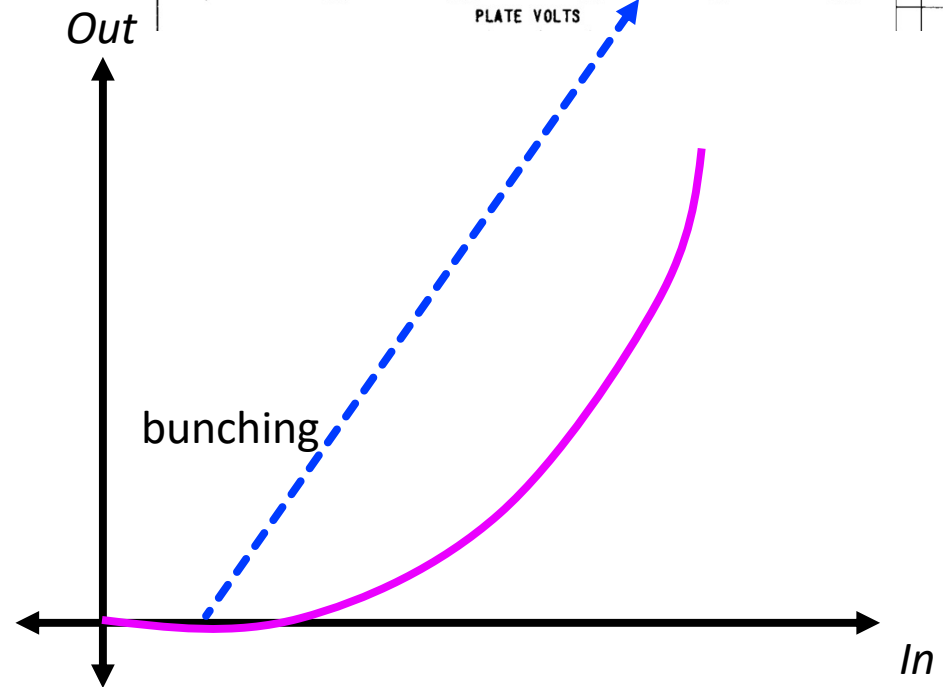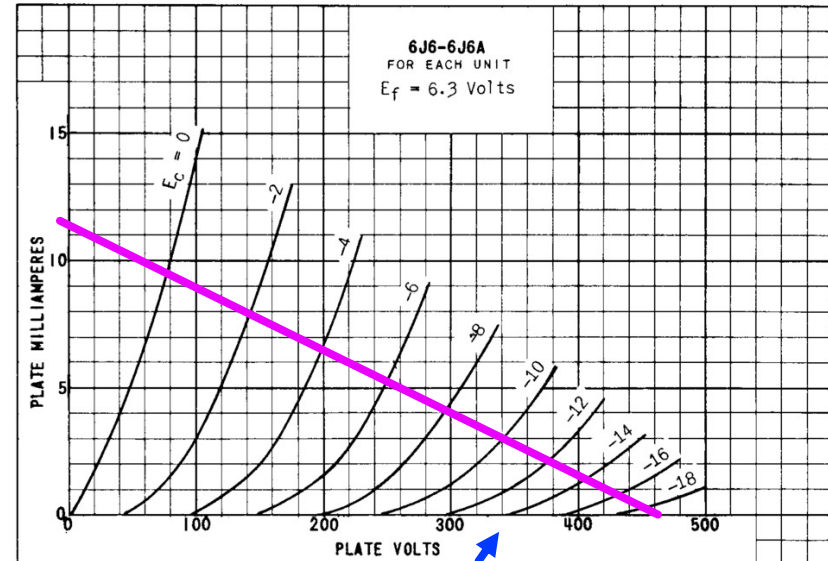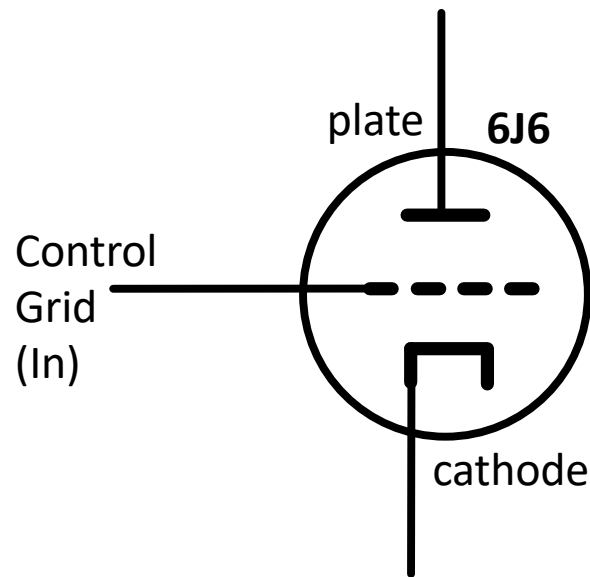


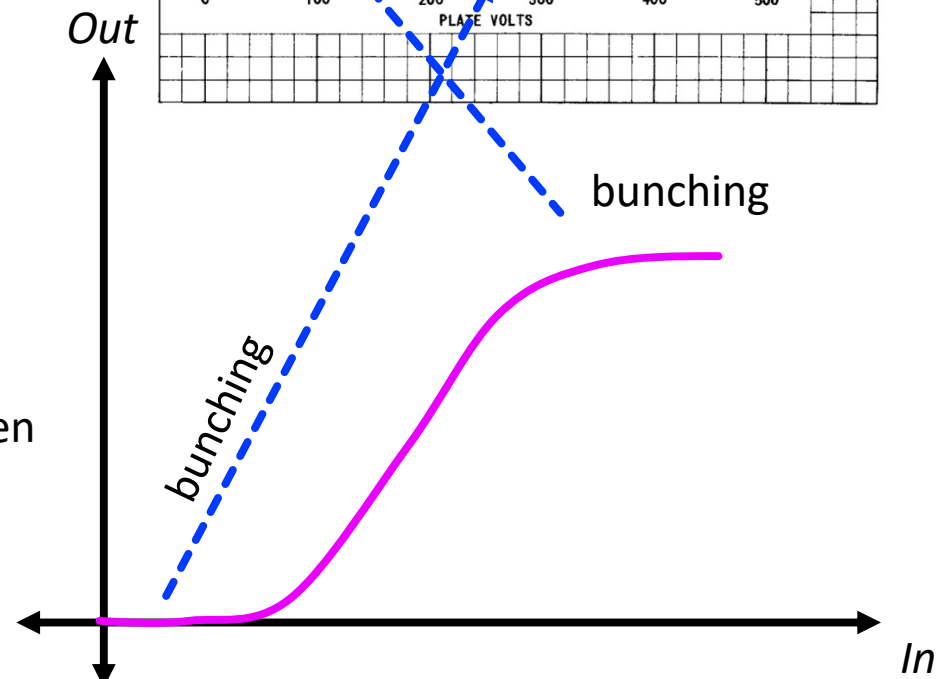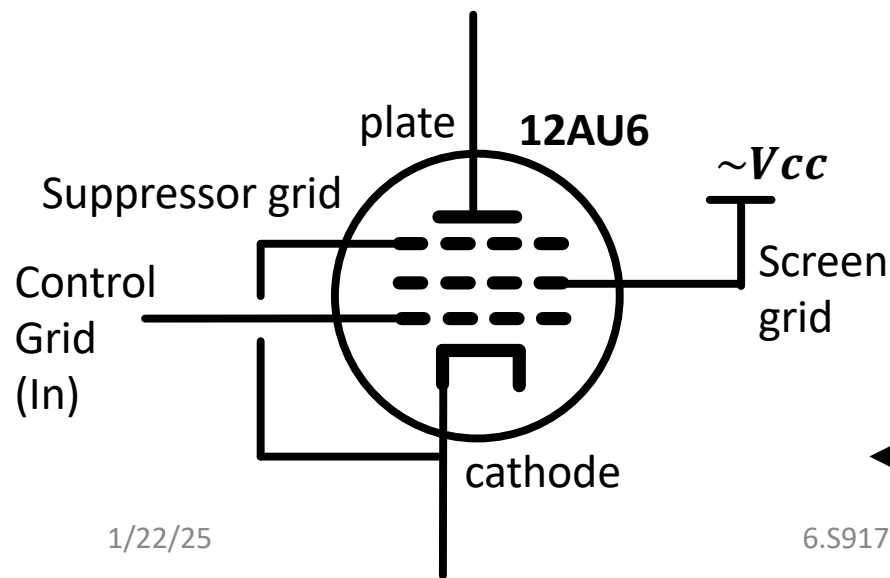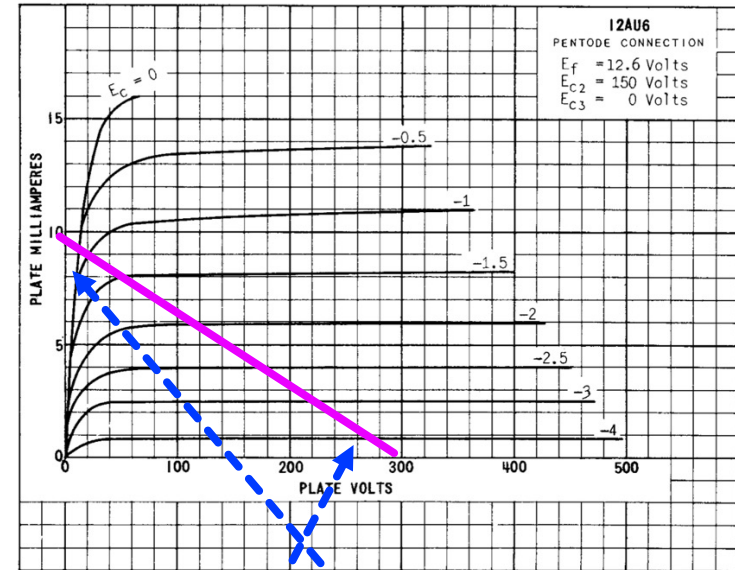
# Can Our Amplifiers Act as Switches?


- Consider the Pentode
- Originally developed to fix Miller Capacitance.
- In the Process we got new I-V relationships for our output terminals


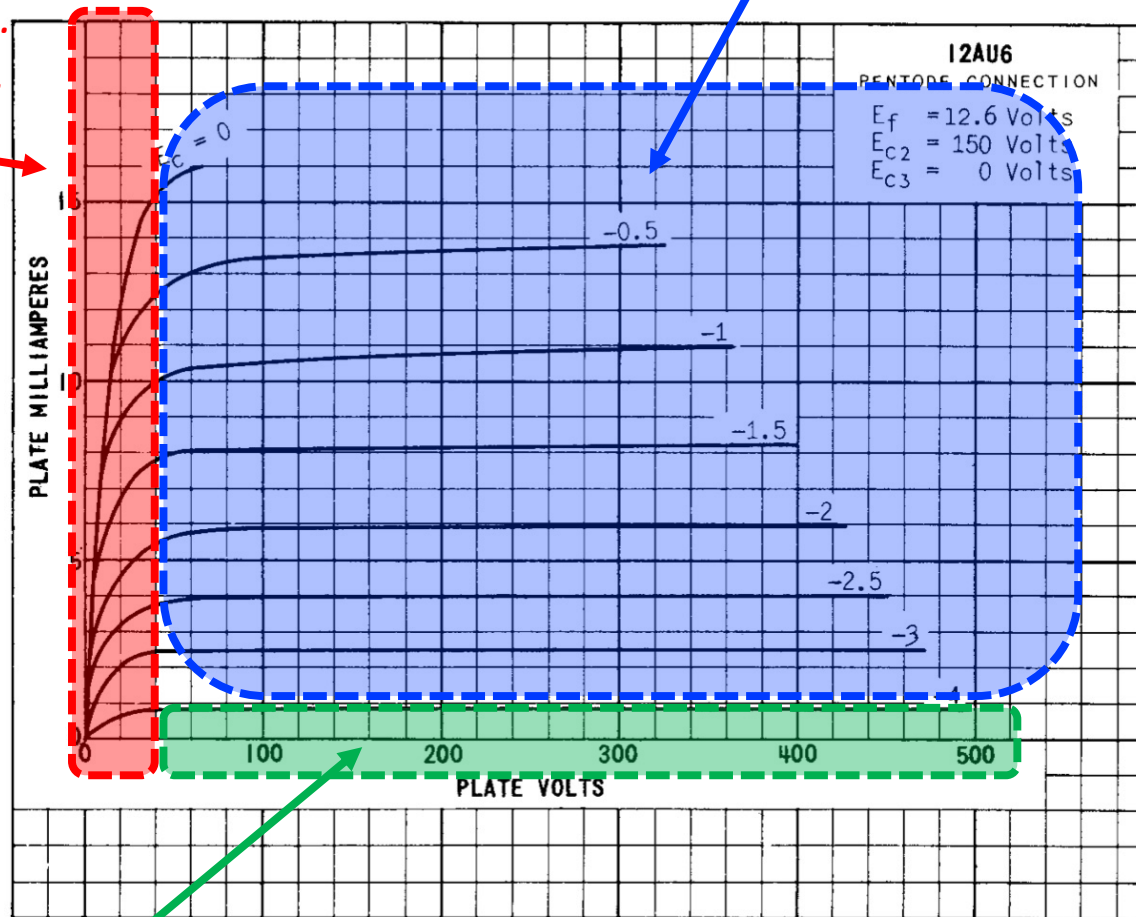
# Pentode Curves

*Current varies with voltage quite cleanly  
Good for regular amplifiers*

*Very steep I/V relations...  
like a low-Ohm resistor...  
or a wire...  
Or a closed Switch!*




*Almost no I for any V  
like a high-Ohm resistor...  
or an open...  
Or a open Switch!*

1/22/25
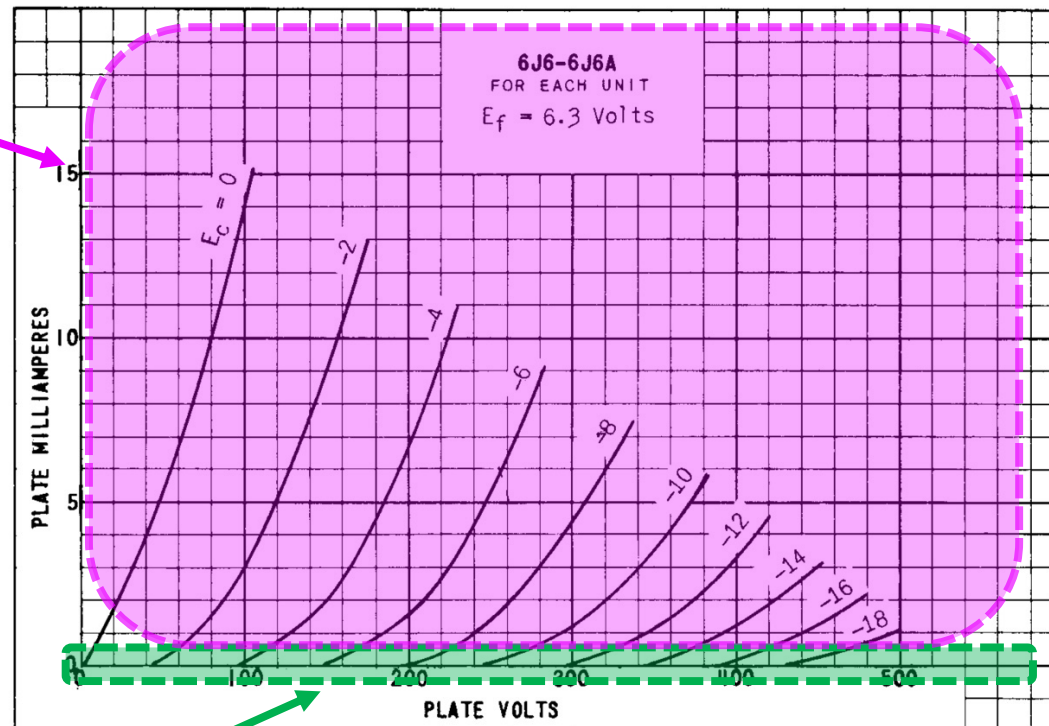
# Triodes Don't Give Us Much in the Way of Abrupt Changes in their behavior


Beyond that we get these sort of diagonal lines which gradually evolve from infinite ohms to less and less ohms. Fine for regular linear amplifiers maybe. Not really a switch, though




Almost no  $I$  for any  $V$  like a high-Ohm resistor... or an open...  
Or a open Switch!  
1/22/25

Triodes **do** have a cutoff range where if grid voltage below threshold, no current flows

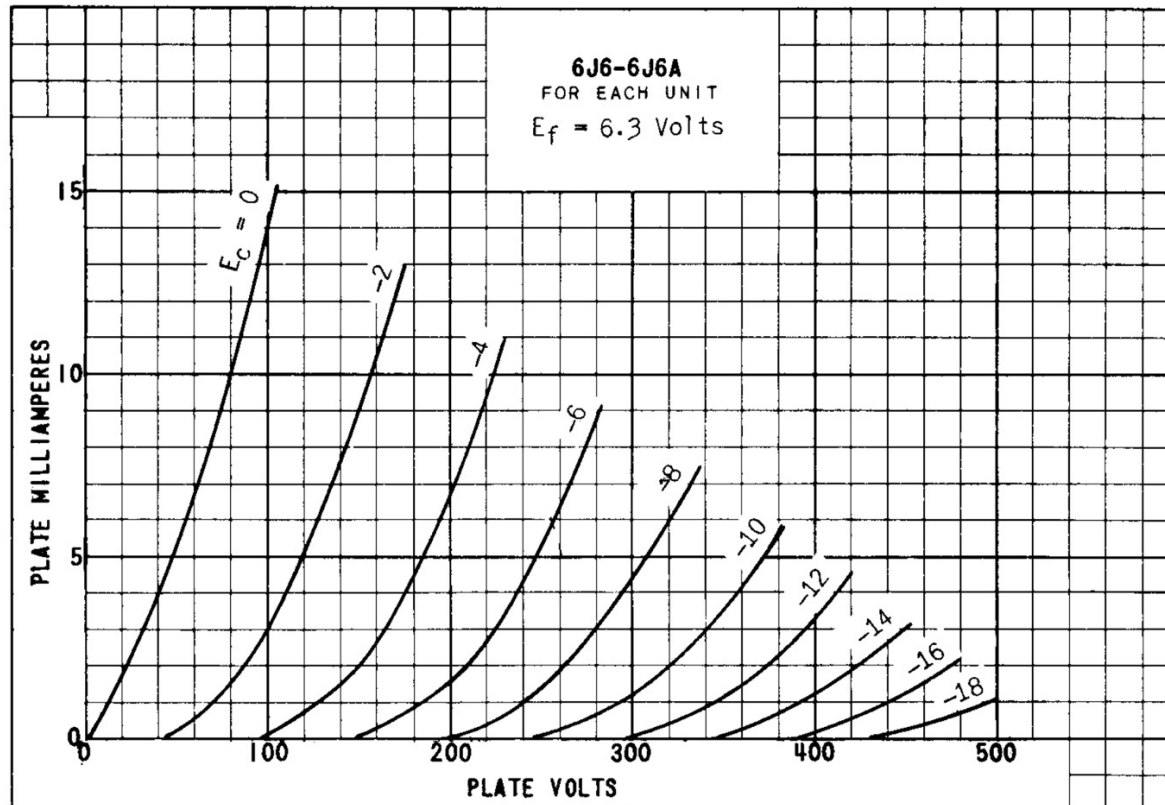In addition to the  $<0$  grid voltages...



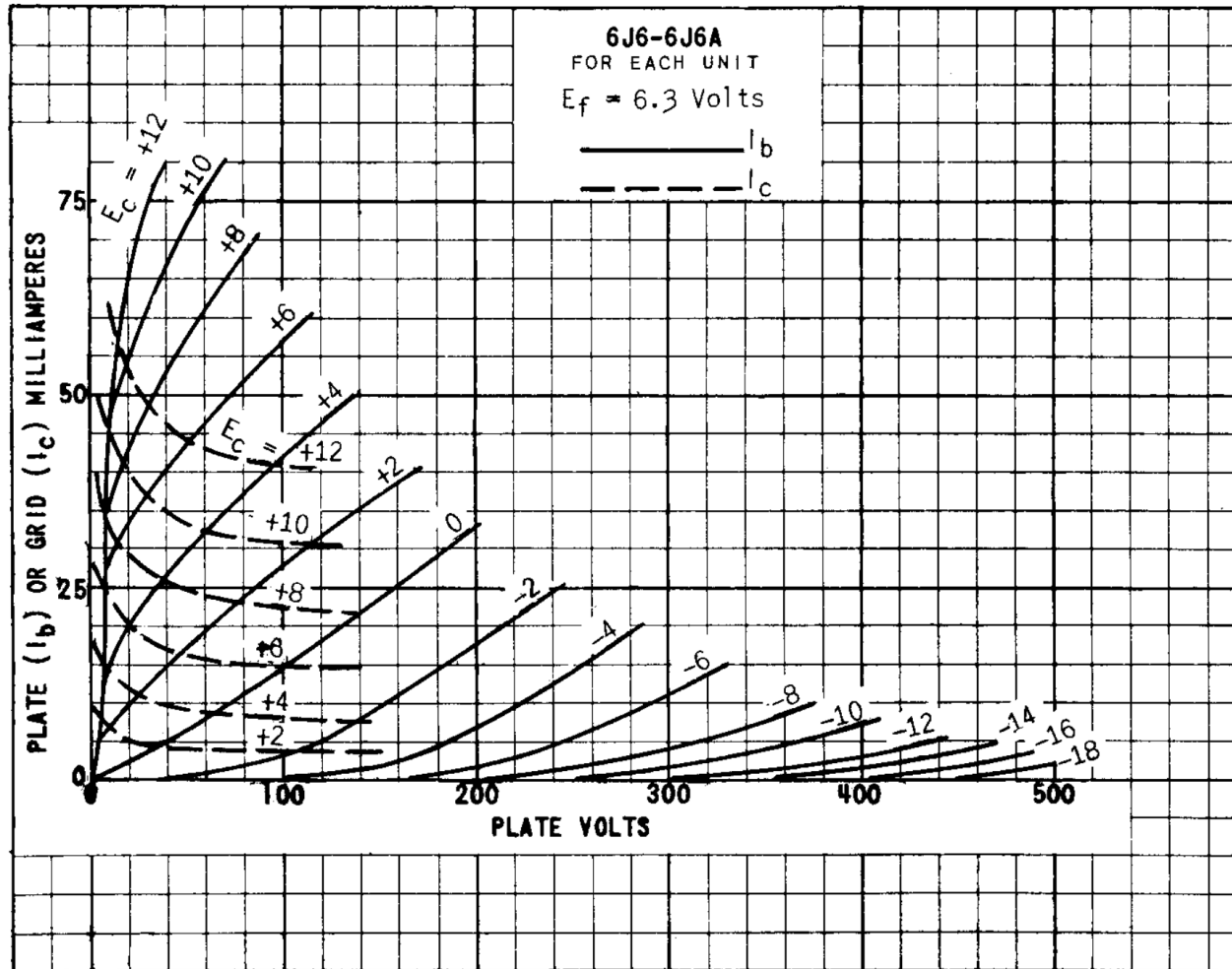
# Some triodes could work at grid voltages $>0$


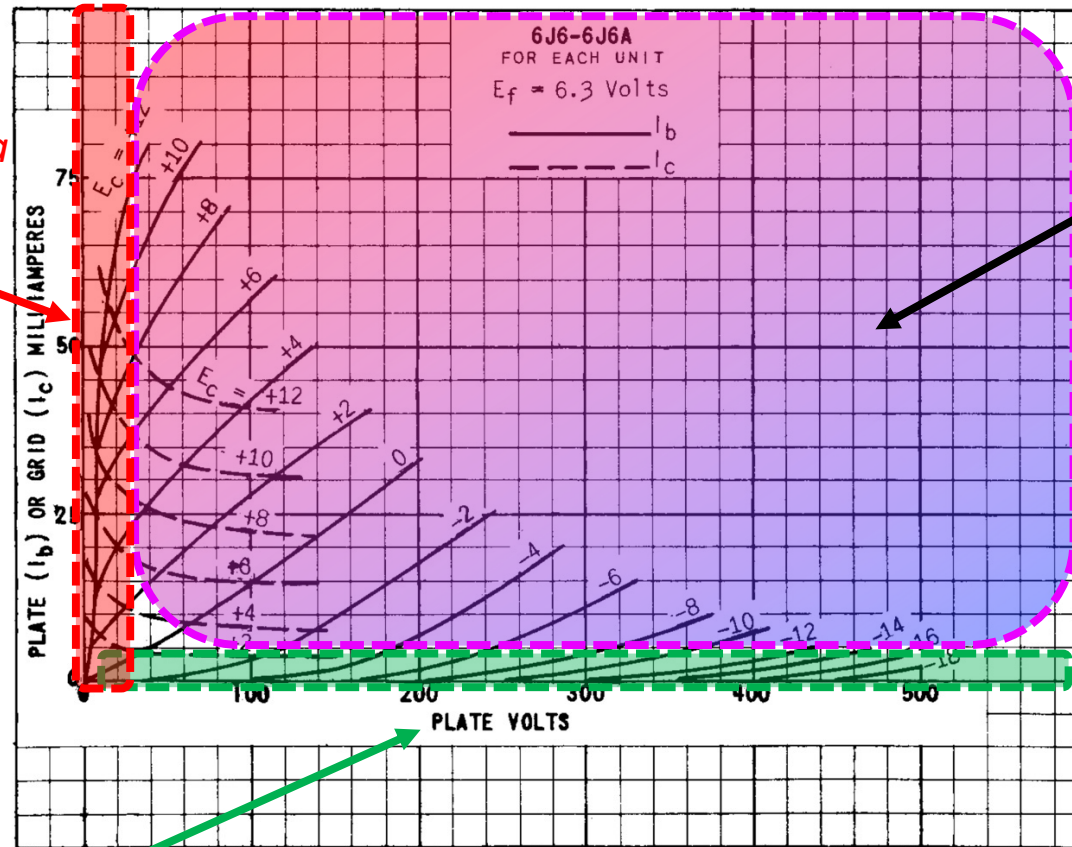
# With positive Grid Voltages, Triodes can actually give ok behavior!

Can get near vertical lines here....so basically a nice closed switch



Not useful region

Triodes have a cutoff range where if grid voltage below threshold, not current flows

Almost no  $I$  for any  $V$  like a high-Ohm resistor... or an open...  
Or a open Switch!


1/23/25

# Unfortunately...


- At positive grid voltages the input impedance of triodes drops drastically
- The grid can now take milliAmps of current (normally grid current is  $\sim 0$ )
- Not possible in our low-voltage circuits since this loads them down.
- So it is basically impossible to get decent switch-like-behavior out of a triode at low voltages (the 6J6 tubes from our labs, for example need to be running with about 100V to even start to approach this)
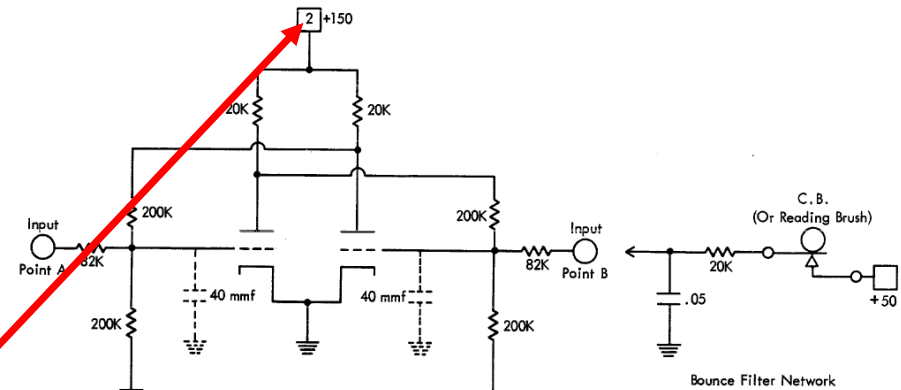
# IBM

- Early Flip-Flop circuit
- Notice the voltages (we don't got those :/ so tube is working a lot less ideally)
- They used about 1500 of these modules for the FFs in an early IBM computer



*1950s tube flip flop*

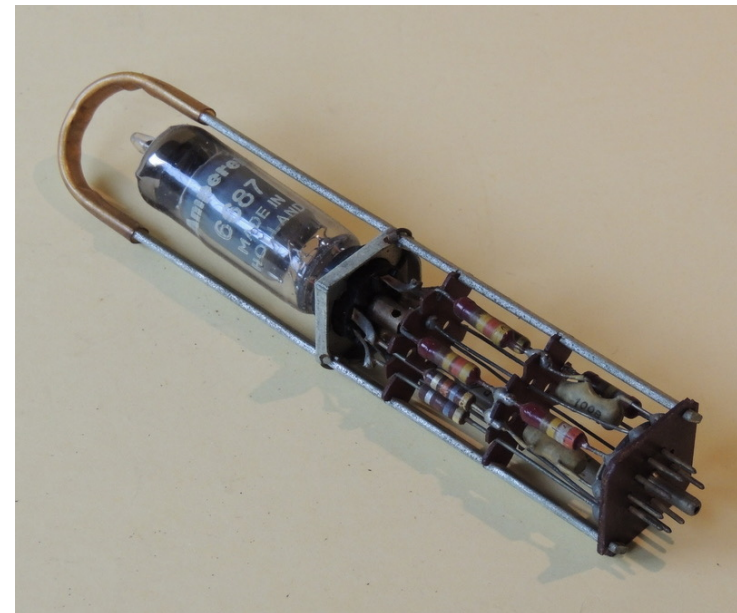

[http://www.calculatormuseum.nl/calculators/computers\\_IBM701.html](http://www.calculatormuseum.nl/calculators/computers_IBM701.html)



# So interesting...

- The two-tube multivibrator can either:
  - oscillate for us (very nice)
  - Sit in one of two states for us (also very nice)
- Why is that second one very nice?
- Because it can remember!
- You pull one grid low and then remove it, the circuit sits in one position
- You pull the other grid low and then remove, the circuit sits at the other position
- We can use these positions to store 1 bit

# So interesting...


- Of course the first computers weren't until the 1940s so we're jumping ahead a bit, but all throughout the 1920s and 1930s, tube circuits like this were used to gradually build up Computer Theory.
- Even a very insightful line in Claude Shannon's Masters Thesis where it finally got linked together formally (I feel shivers when I read this):

*“A device with two stable positions, such as a relay or a **flip-flop circuit**, can store one bit of information.  $N$  such devices can store  $N$  bits, since the total number of possible states is  $2^N$  and  $\log_2 2^N = N$ .”*


*-Claude Shannon, 1948*
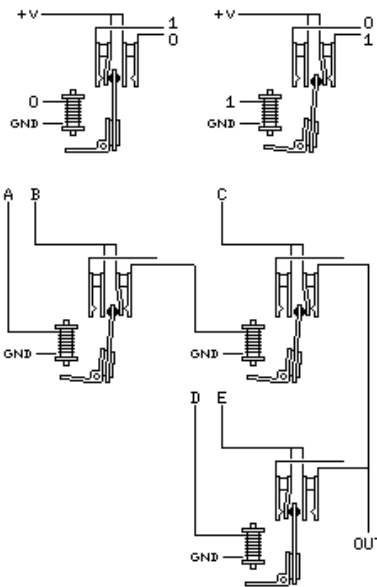
# Combine those FlipFlops with the ability perform Boolean logic operations


- Using either relays or vacuum tubes make some logic:



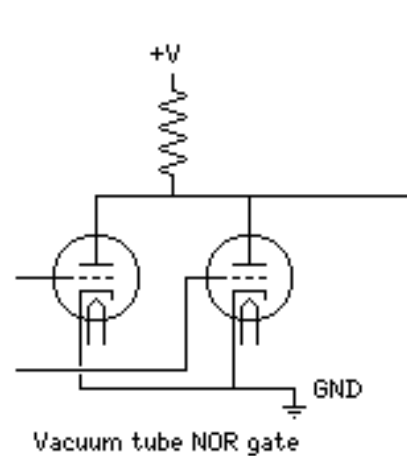Relay Logic Gates like you built in Lab 01



Vacuum tube NOR gate

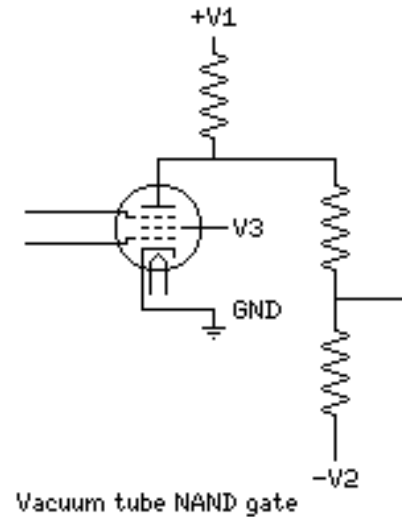

Vacuum tube NAND gate

Vacuum Tube Logic Gates  
(Can be done with triodes at high voltage...or low voltage pentodes if their "shoulder" is low enough)


<http://www.quadibloc.com/comp/cp01.htm>

# If you can make NAND (or NOR)


- **Any** Boolean logic expression can be reduced to either the following shape:
  - $Y = \overline{A|B|C| \dots}$  (which is a NOR)
  - OR
  - $Y = \overline{A\&B\&C\& \dots}$  (which is a NAND)
- With the ability to remember bits and the ability to perform logic operations of any type you can now start building **finite state machines**.
- With access to sufficient memory/instructions, this is easily expanded to full-fledged computers
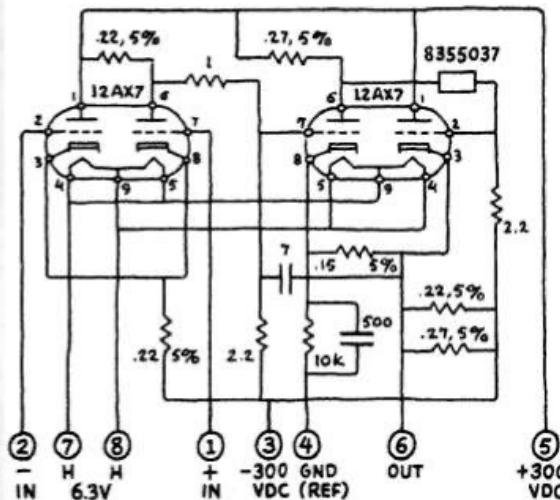
# We Did A Lot With Tubes

- Most modern designs started with tubes.



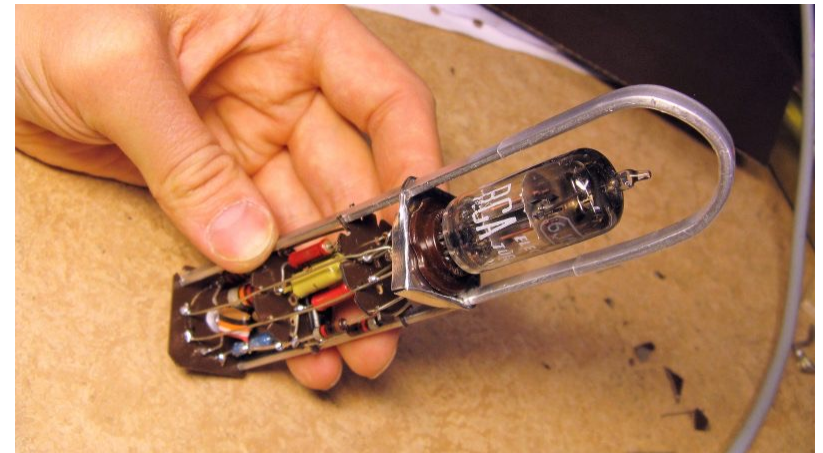
The first commercial  
Operational Amplifier



Triode-based Flip-Flop  
From IBM 605

<https://www.talkbass.com/threads/tube-op-amps-experience-interests.1215611/>

# Op Amps

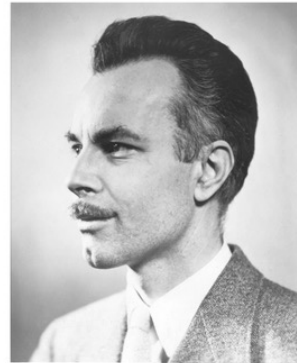


ELECTRONIC ANALOG COMPUTING INSTRUMENTS

GAP/R  
MODEL  
K2-W
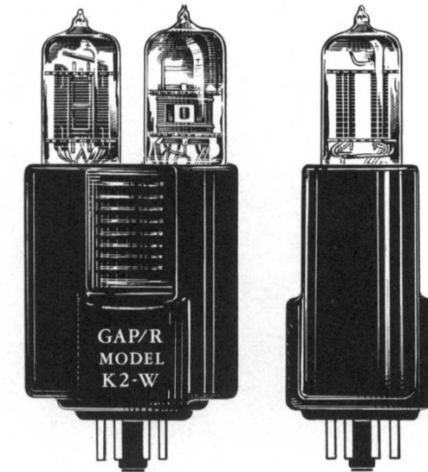
## Model K2-W Operational Amplifier

- The idea of op amps was formalized right towards end of WW2 (1945-1950)
- George Philbrick developed op amps and sold tube-based ones right out of Cambridge/Boston in mid 1950s
- Building block of much modern analog circuitry



Model K2-W is the same operational amplifier, engineered and designed into this compact form, that has proved so successful in the Philbrick Analog Components. Using these plug-in units as basic subassemblies, feedback computing devices of all speeds may be assembled with only the simplest of wiring. The versatile K2-W is already serving in widespread applications. It features balanced differential inputs for minimum drift and maximum utility, and embodies both high performance and economy of operation in one unit.


This type of high gain amplifier, with appropriate feedback connections, maintains the two inputs at a nearly equal potential. Such properties give rise to a large number of operational applications.

Among the many feedback operations which the K2-W will readily perform are: addition, subtraction, integration, differentiation, multiplication, division, inversion, impedance-conversion, and the injection of current.

GENERAL SPECIFICATIONS			
<b>GAIN:</b> 15,000 DC, open-loop	<b>INPUT IMPEDANCE:</b> Above 100 Megohms	<b>VOLTAGE RANGE:</b> -50 VDC to +50 VDC, at output and both inputs	<b>INPUT BIAS:</b> Positive input should be made to operate about 1.5 V <i>big</i> at balance, normally re- quiring adjustable external bias
<b>POWER REQUIREMENTS:</b> 4.5 Milliamps. at +300 VDC 4.5 Milliamps. at -300 VDC 0.6 Amperes at 6.3V	<b>OUTPUT IMPEDANCE:</b> Less than 1 K open-loop; below 1 ohm fully fed back	<b>INPUT CURRENT:</b> Less than 0.1 Microamp., for either input	<b>RESPONSE:</b> 2-Microsecond rise time, with band width over 100 KC when used as inverter
<b>TUBE COMPLEMENT:</b> 2 12AX7	<b>DRIFT RATE:</b> 5 Millivolts per day, re- ferred to the input	<b>OUTPUT CURRENT:</b> -1 Milliamp. to +1 Milli- amp., driving 50 K load over full voltage range	
<b>BASING:</b> Octal plug	<b>HEIGHT:</b> 4½ Inches overall		
<b>CASE:</b> Black plastic, molded	<b>WEIGHT:</b> 2.8 ounces		

[http://www.philbrickarchive.org/k2-w\\_refurbished.pdf](http://www.philbrickarchive.org/k2-w_refurbished.pdf)


### OPERATIONAL SYMBOL

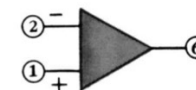

### BASE PIN CONNECTIONS

1: Pos. Input	4: Ground	7 & 8:
2: Neg. Input	5: Plus 300VDC	Heaters,
3: Minus 300VDC	6: Output	6.3V AC or DC
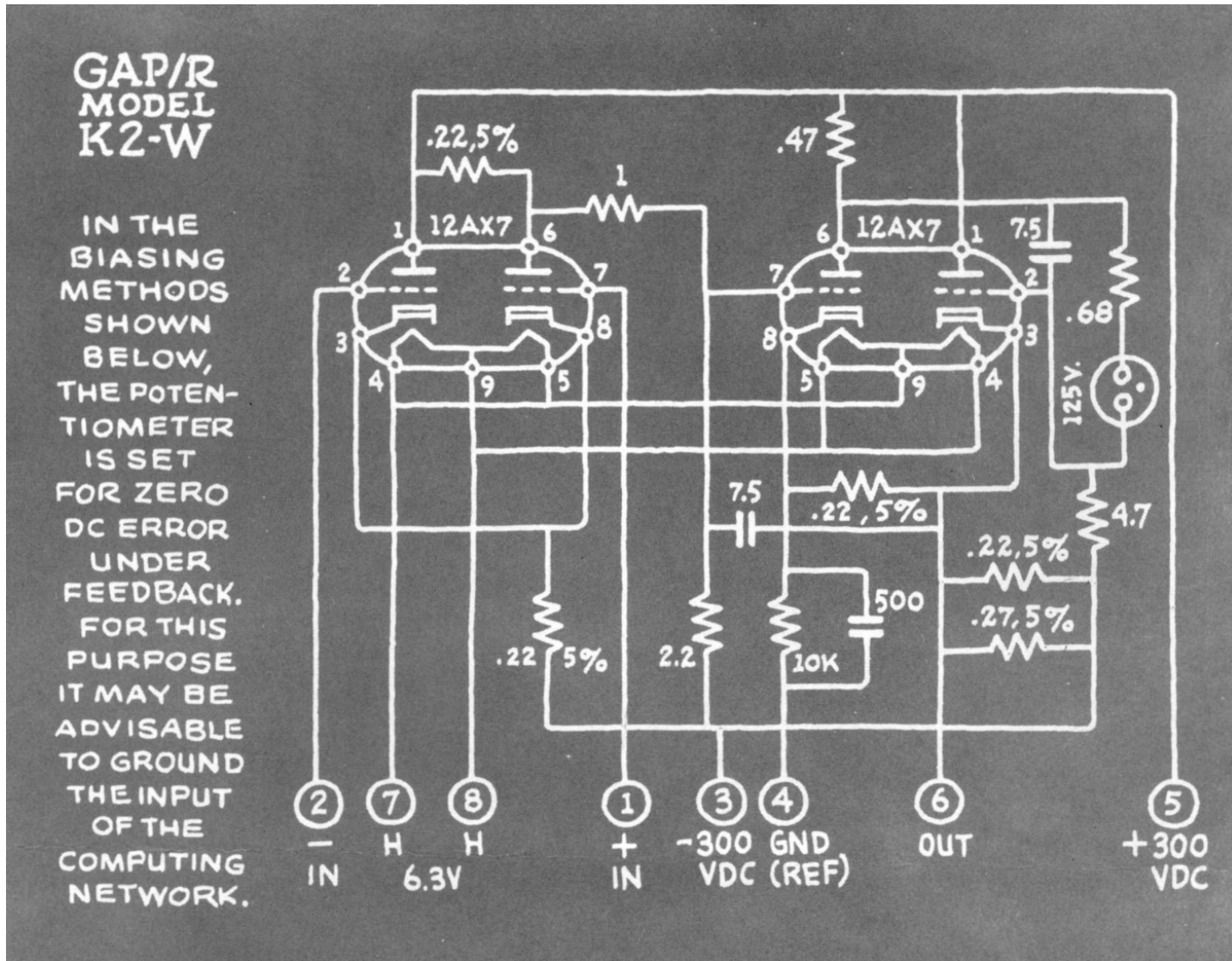
# The first Commercially Available Op Amp






# Example Applications

- Literature use to sell the op amps showed all the useful circuits you could do with them.
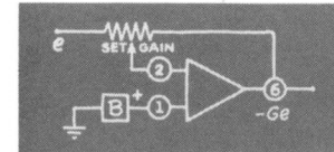
## APPLICATIONS


In general terms, the field of application of the K2-W Amplifier is in measurements and active transformations, in the range from DC to above 100 KC. It is primarily intended for feedback operations, where fidelity is made to depend almost entirely on the external circuit arrangements employed.

There are already more such applications than may readily be presented, and new computing connections are being conjured up every day. The following group of applications is merely typical. The circuits shown have been selected since they are fundamental as well as useful; they should suggest a variety of other forms.



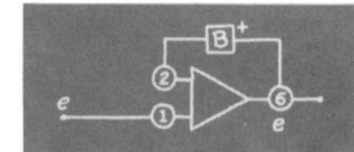
**WIDE-RANGE AMPLIFIER**

The usual feedback and feed-forward resistors are here embodied in a single potentiometer. A voltage gain of minus one is given by the central setting.



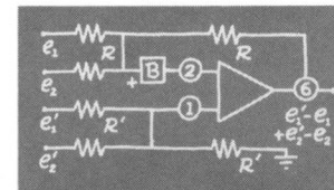
**VOLTAGE REPRODUCER**

This exceedingly simple arrangement supplies the need for a "follower" without attenuation or distortion, and with an output impedance well below one ohm.



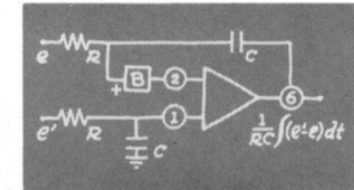
**ADDER-SUBTRACTOR**

A number of simpler and possibly more familiar circuits are special cases of this one. By using unequal resistors, a more general form of linear combination is made possible.



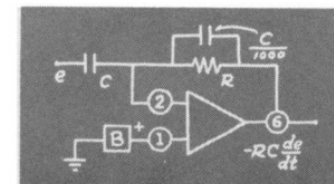
**SUBTRACTING INTEGRATOR**

A positive or negative integral may be obtained by grounding one input. Unless an integrator is in a stable loop it must be subjected to some sort of "clamping" process.



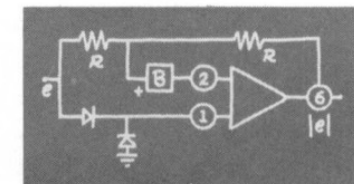**STABLE DIFFERENTIATOR**

The smaller shunt capacitor will prevent ringing or singing, and introduces very little error. In certain difficult cases one might also add a small resistor in series with the input capacitor.




**ABSOLUTE-VALUE CIRCUIT**

Reversing both diodes will reverse the sign of the output. To the AC Power engineer this is simply a "full wave rectifier", but as a computing device it is useful in a much wider sense.


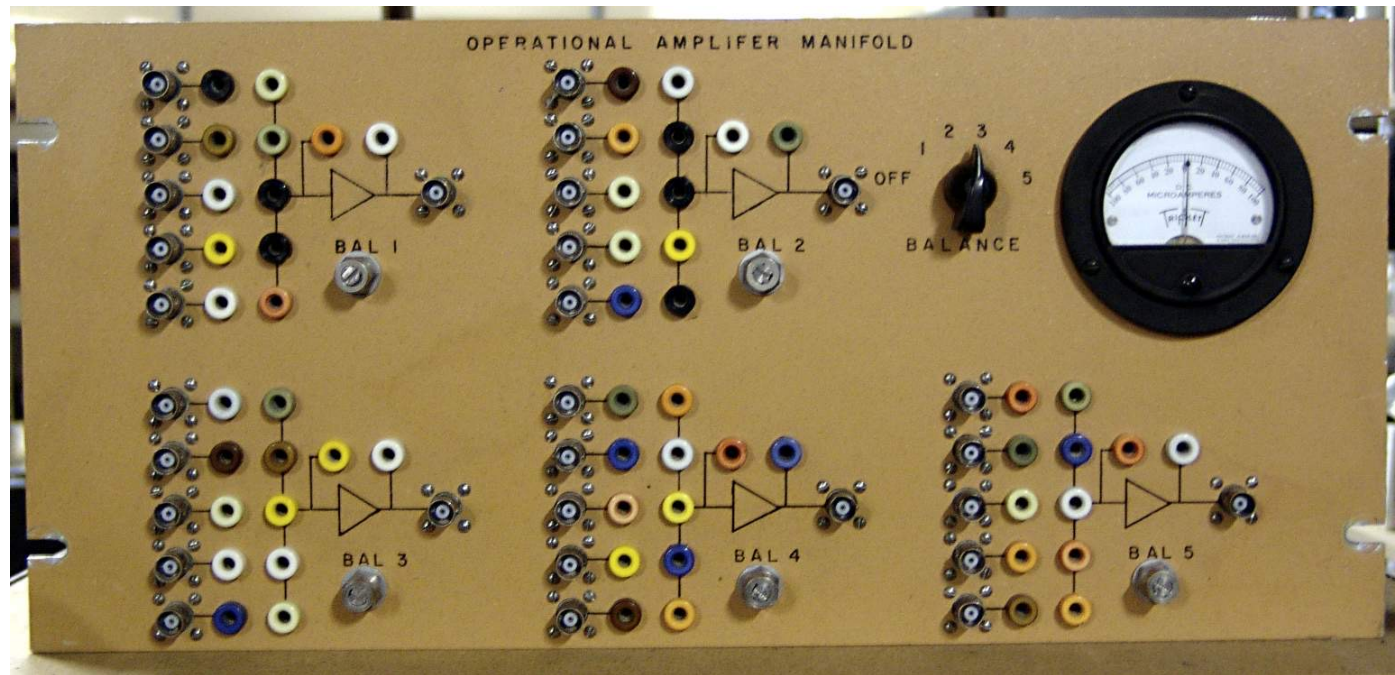
# Early Analog Computer

- In competition with early digital computers were analog computers.
- The idea with these was you'd use operational amplifiers as programmable math blocks to solve differential equations/perform simulations
- The voltage and current levels would “model” the phenomena of interest and you'd measure the output



- Use jumpers, R's, C's, L's in between to perform differential equation calculations and other things




<http://www.dvq.com/oldcomp/analog/philbrick.htm>

# Why Analog vs. Digital?

- Digital computers start with an inherently less-dense usage of electricity to represent information (represent one-of-two) whereas analog could represent 1000's or more.
- Digital computers essentially rely on speed to overcome this initial down-side and early digital computers were not that fast.
- So analog computers were valuable up until the early 1960s in certain numerical simulation situations....

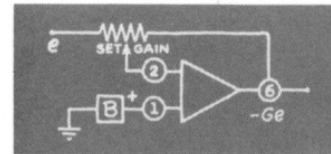
# Op Amp Usage

- When we use op amps we do something weird... we...
- Connect the output back to the input...but do so in a destructive way!



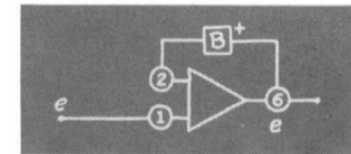
**WIDE-RANGE AMPLIFIER**

The usual feedback and feed-forward resistors are here embodied in a single potentiometer. A voltage gain of minus one is given by the central setting.



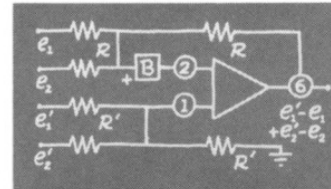
**VOLTAGE REPRODUCER**

This exceedingly simple arrangement supplies the need for a "follower" without attenuation or distortion, and with an output impedance well below one ohm.



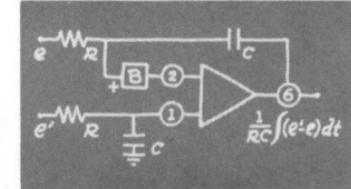
**ADDER-SUBTRACTOR**

A number of simpler and possibly more familiar circuits are special cases of this one. By using unequal resistors, a more general form of linear combination is made possible.



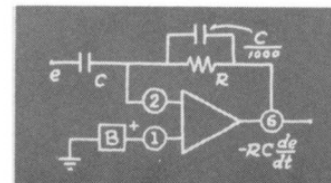
**SUBTRACTING INTEGRATOR**

A positive or negative integral may be obtained by grounding one input. Unless an integrator is in a stable loop it must be subjected to some sort of "clamping" process.



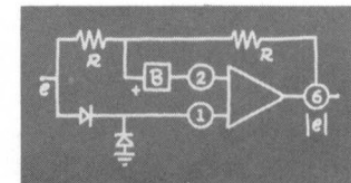**STABLE DIFFERENTIATOR**

The smaller shunt capacitor will prevent ringing or singing, and introduces very little error. In certain difficult cases one might also add a small resistor in series with the input capacitor.



**ABSOLUTE-VALUE CIRCUIT**


Reversing both diodes will reverse the sign of the output. To the AC Power engineer this is simply a "full wave rectifier", but as a computing device it is useful in a much wider sense.

# Not Exactly Linear

- You may have noticed, that our triode is not exactly a linear amplifier

$$I_B = P \left( V_C + \frac{V_B}{\mu} \right)^{3/2}$$

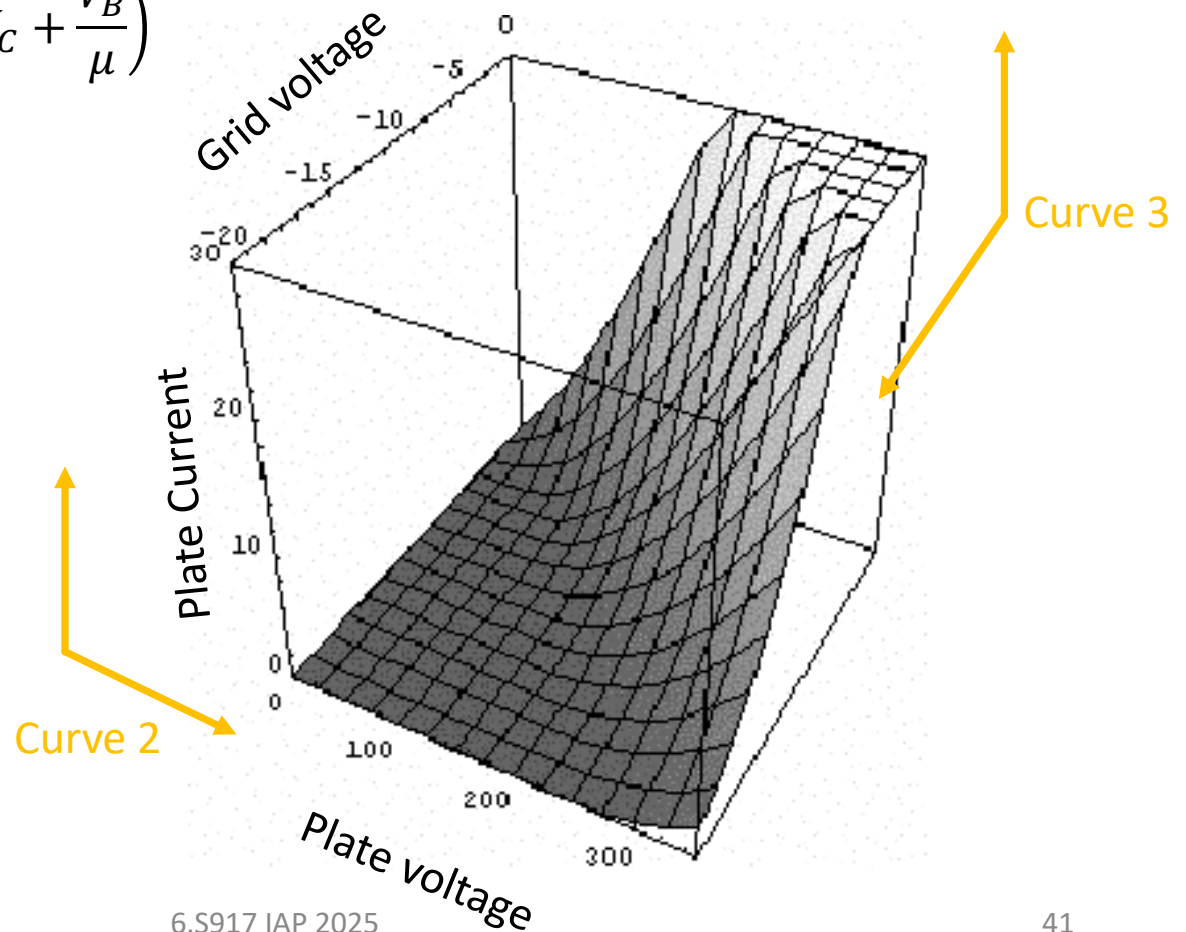- Being linear is desired for amplification
- How did they make good amplifiers?



<https://www.john-a-harper.com/tubes201/>

# Not Exactly Linear But Pretty Close

- As non-linear as a thing to the  $3/2$  power is, it is actually much closer to linear by “raw” device standards (especially when compared with what was to come historically (pentodes and transistors))
- This ability to be more linear-ish while in a simple vanilla circuit is one reason why modern “Hi-Fidelity” audio amplifiers still use tubes (though the cool aspect of it is probably really the reason since excellent linear-behavior can be achieved with more modern devices/circuit topologies).

# Still...

- Even early in the triode's life in the 1910's people wanted a more linear amplifier capability since *any* non-linearity was always going to be causing all those weird extra frequency components that could get annoying/impossible to filter
- So people set out searching how to linearize an amplifier!
- There were lots of problems...in particular as you made triodes with larger gains, they seemed to become *less and less linear*\*
- So the field kinda got jammed between the more-gain and more linearity directions with no way to go.

\*lots of non-idealities started to come into play

# The Solution

- Harold Black approached the problem
- During a ferry ride into work in 1927 he came up with the idea of negative feedback
- It turned out that you could trade gain for linearity and other nice features
- The problem was that at first it was just a few years too early for it to be useful.




[https://en.wikipedia.org/wiki/Harold\\_Stephen\\_Black](https://en.wikipedia.org/wiki/Harold_Stephen_Black)


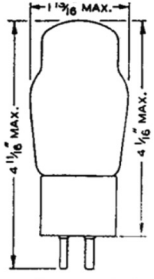
# Feedback

Originally


- Early Triodes didn't have much gain so the value proposition of throwing away gain to achieve linearity wasn't exactly a good one...



## RCA-26
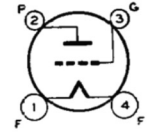
### AMPLIFIER

The 26 is an amplifier tube containing a filament designed for operation on alternating current. This tube is for use as an r-f or a-f amplifier in equipment designed for its characteristics. The 26 is not ordinarily suitable for use as a detector or power output tube.




CHARACTERISTICS			
FILAMENT VOLTAGE (A. C. or D. C.)	1.5		Volts
FILAMENT CURRENT	1.05		Amperes
PLATE VOLTAGE	90	135	180 max. Volts
GRID VOLTAGE*	-7	-10	-14.5 Volts
PLATE CURRENT	2.9	5.5	6.2 Milliamperes
PLATE RESISTANCE	8900	7600	7300 Ohms
AMPLIFICATION FACTOR	8.3	8.3	8.3
TRANSCONDUCTANCE	935	1100	1150 Micromhos
GRID-PLATE CAPACITANCE			8.1 μμf
GRID-FILAMENT CAPACITANCE			2.8 μμf
PLATE-FILAMENT CAPACITANCE			2.5 μμf
BULB			ST-14
BASE			Medium 4-Pin

\* Grid voltage measured from mid-point of a-c operated filament.

In 1927:

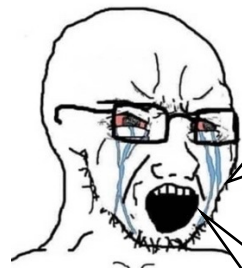*“Currently I have a voltage amplifier with a gain of 2.3 that is slightly non-linear and awful levels of input and output impedance”*




Some loser engineer

*“No. Are you crazy? Get away from me with your theories”*

1/22/25

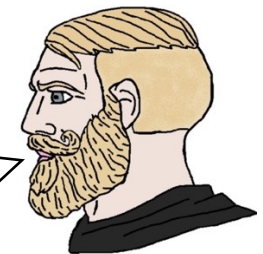*“Yes but imagine if you could make a voltage amplifier with a gain of 1.2 and potentially worse in/out impedances that is linear! Doesn't that sound enticing????”*



Harold Stephen Black

6.S917 IAP 2025

45

# Feedback


A few years later...

- Tubes got better...better gain, cheaper, better I/O char

**High-Mu Twin Triode**  
 9-PIN MINIATURE TYPE  
 For High-Fidelity Audio-Amplifier Appli-

Characteristics, Class A<sub>1</sub> Amplifier (Each Unit):


Plate Voltage . . . . .	100	250	volts
Grid Voltage . . . . .	-1	-2	volts
Amplification Factor . . . . .	100	100	
Plate Resistance (Approx.) . . . . .	80000	62500	ohms
Transconductance . . . . .	1250	1600	μmhos
Plate Current . . . . .	0.5	1.2	ma

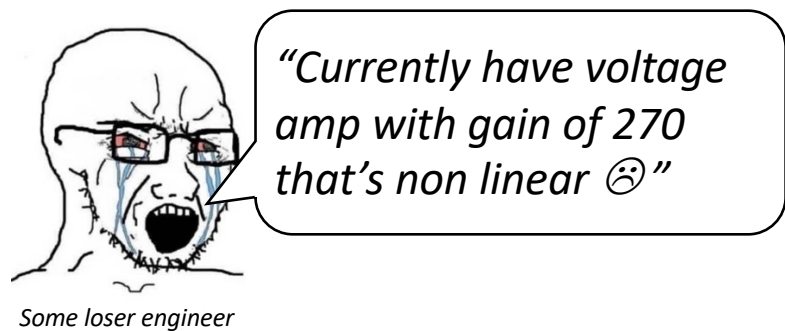

"Currently have voltage amp with gain of 270 that's non linear ☹"

In 1930s:

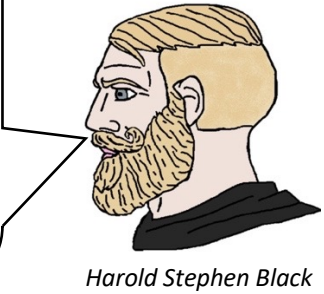"Yes but imagine if you could make a voltage amplifier with a gain of 100 with negligibly worse in/out impedance that is linear! Doesn't that sound enticing????"



Transforms into



"Your ideas intrigue me, and I would like to subscribe to your newsletter."




# Basic Triode Setup

- Our Basic Triode setup in open loop:

$$v_{OUT} = A_o \cdot v_{IN}$$

What is  $A_o$ ? It was the value we eyeballed from looking at our load-line plots last week. It will be non-linear and will also be affected by source and load impedances.
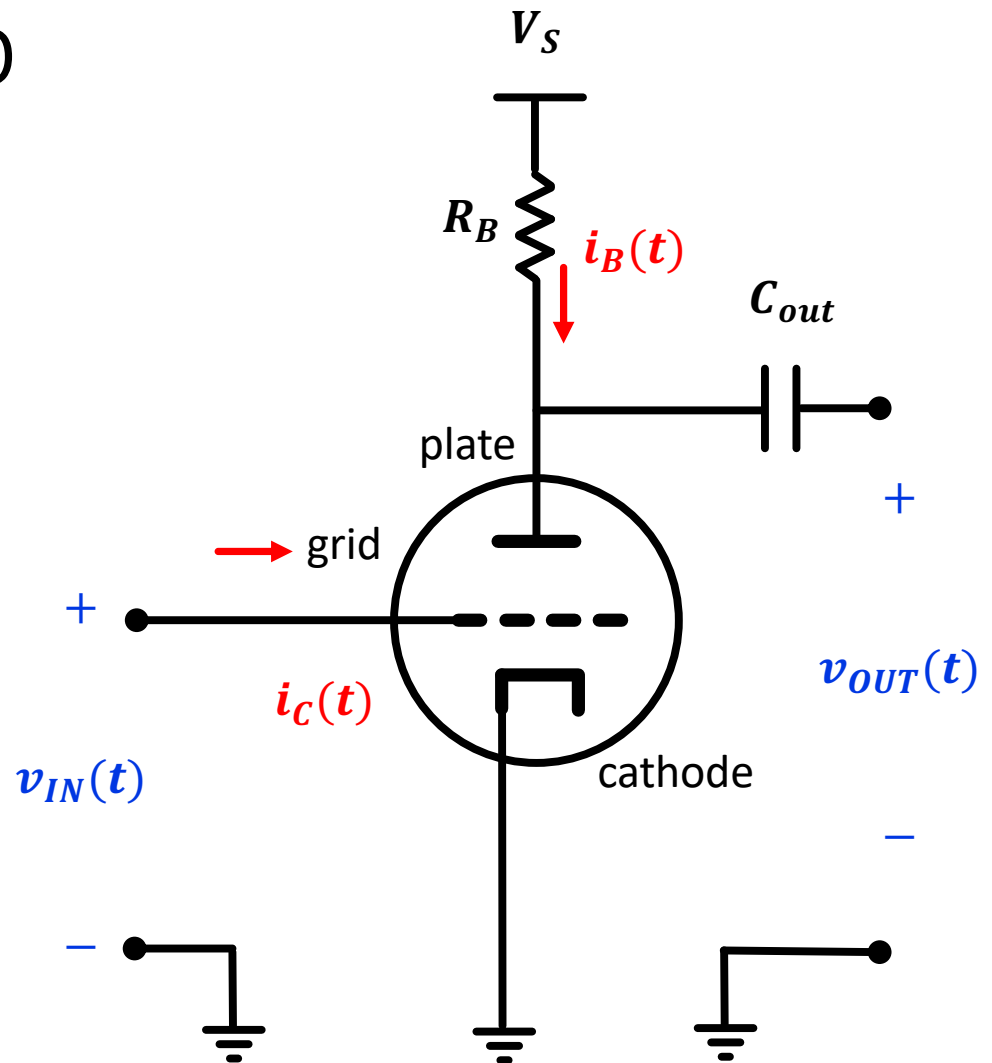
$$\text{Nominally: } A_o = -\frac{R_B \cdot \mu}{R_B + R_p}$$



*\*ignore grid bias and things for these examples to keep things simple!*

# Critical Coefficients

- Three important values characterize a Triode and are related by this equation:

$$R_p = \frac{\mu}{G_m}$$

**Voltage amplification factor:** The factor by which the grid voltage changes the voltage at the plate. (unitless)



**Plate Resistance:** The output resistance of the tube at the plate (in Ohms)

**Mutual Conductance (Transconductance):** The factor by which a change in grid voltage causes a change in plate current (units of conductance...so Mhos or Siemens)

- These numbers are extracted from the values and slopes of the transfer function plots
- They are NOT Constants!


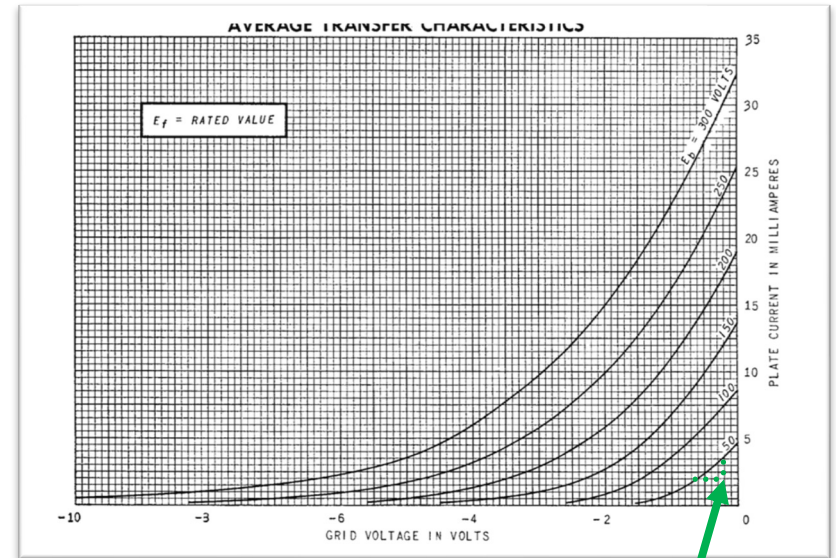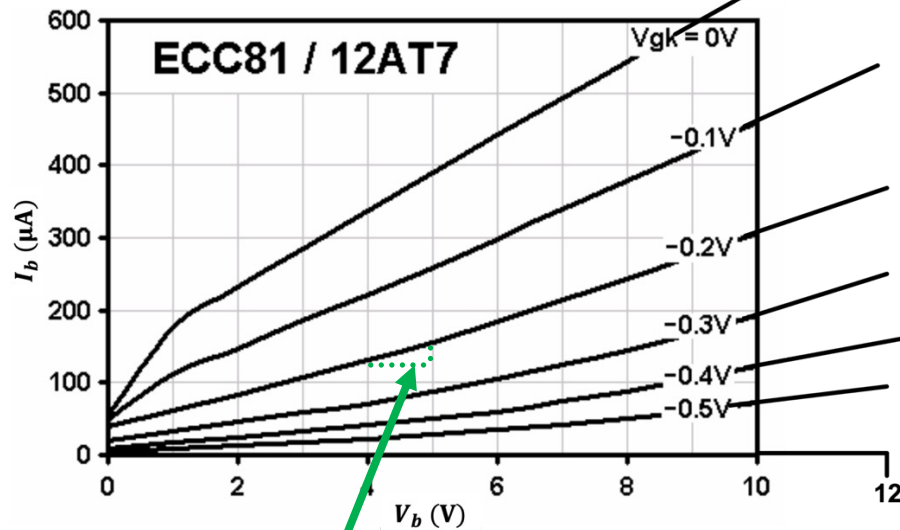
# Extract parameters from Plots and then use actual formula



$$\frac{\Delta I_b}{\Delta V_b} = \frac{1}{R_p}$$

$$\frac{\Delta I_b}{\Delta V_c} = G_m$$

$$\mu = R_p G_m$$


$$A_o = -\frac{R_B \cdot \mu}{R_B + R_p}$$

# Basic Triode Setup

- Regardless of How we get the open loop gain, the important thing is that it is a varying, non-linear quantity!

$$v_{OUT} = A_o(*) \cdot v_{IN}$$

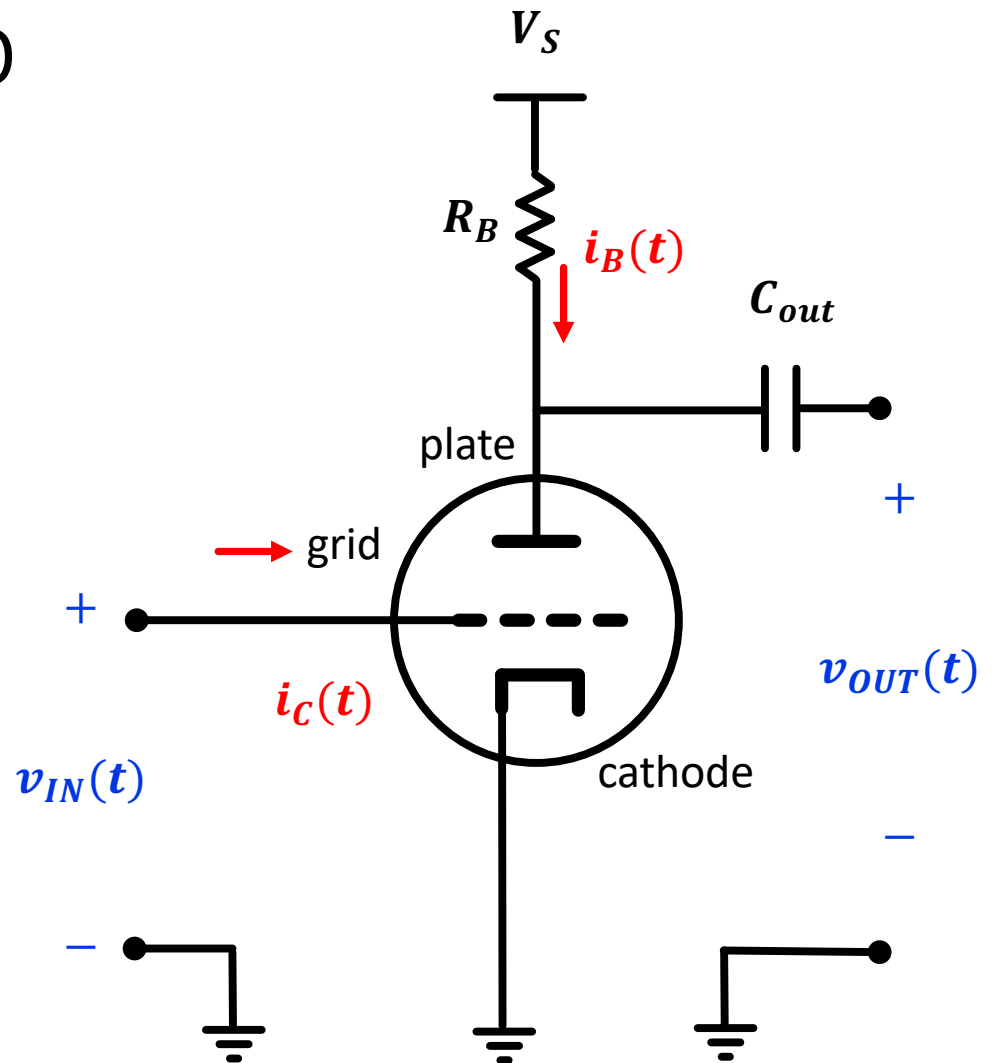
So let's just say that  $A_o$  is a function of everything (\* is wildcard) to indicate it is a nonlinear thing...and as a result, the entire equation is going to be nonlinear! Our job isn't to know exactly the nonlinearity, just recognize the shape



*\*ignore grid bias and things for these examples to keep things simple!*
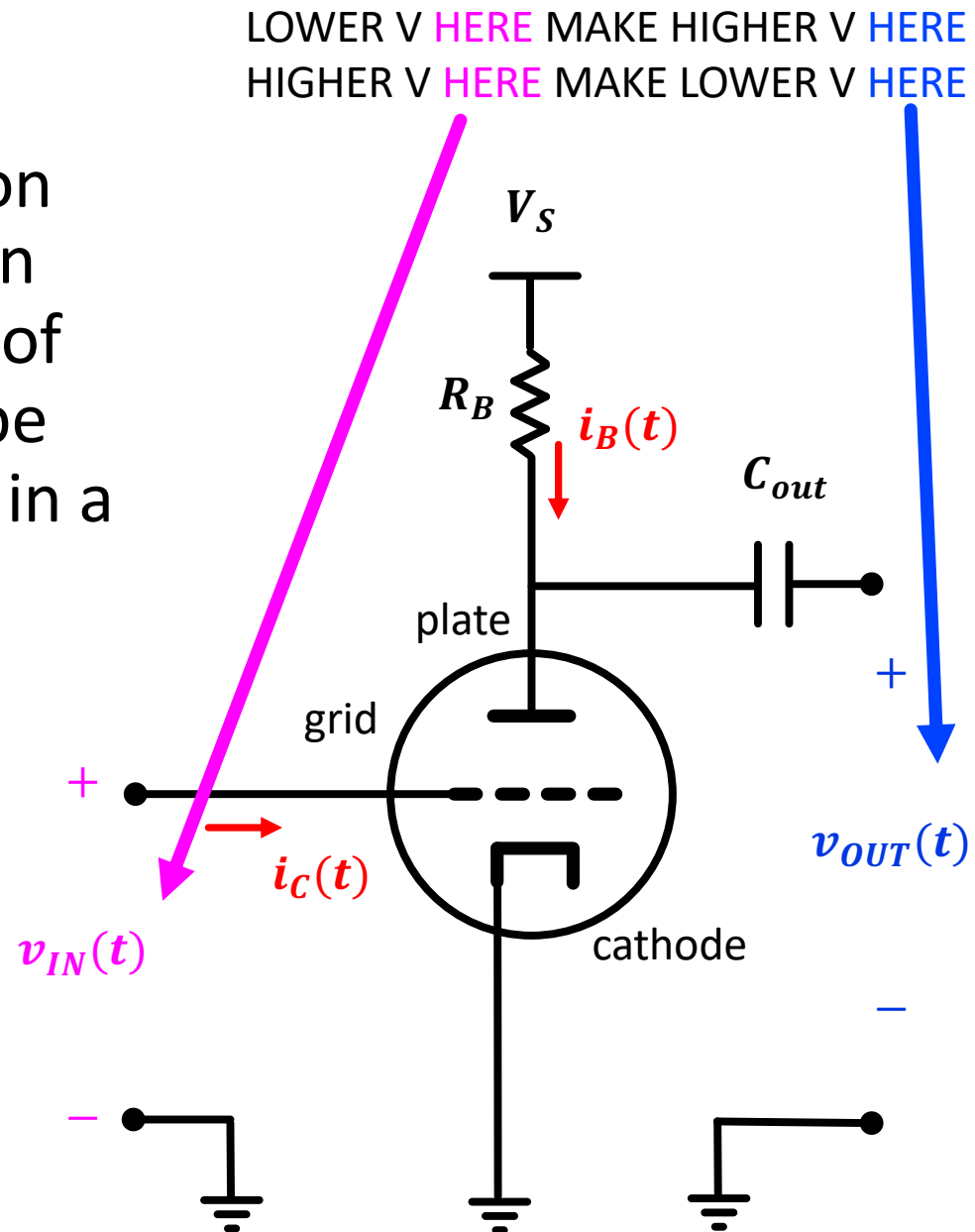
# Sign of Gain

- Regardless of how non linear or not our open loop gain is, the sign of our gain will always be **negative** since we're in an inverting amplifier topology!





# Add a Feedback Path

- Take some of our output...and using a voltage divider, feed it back to the input...
- Assuming  $i_c$  is  $\sim 0$ :

The voltage at the grid is:


$$v_c = v_{in} + (v_{out} - v_{in}) \frac{R_g}{R_g + R_f}$$

Like before the output is a function of voltage at input (grid):

$$v_{out} = A_o(*) \cdot v_c$$

Or put another way:

$$v_c = \frac{v_{out}}{A_o(*)}$$

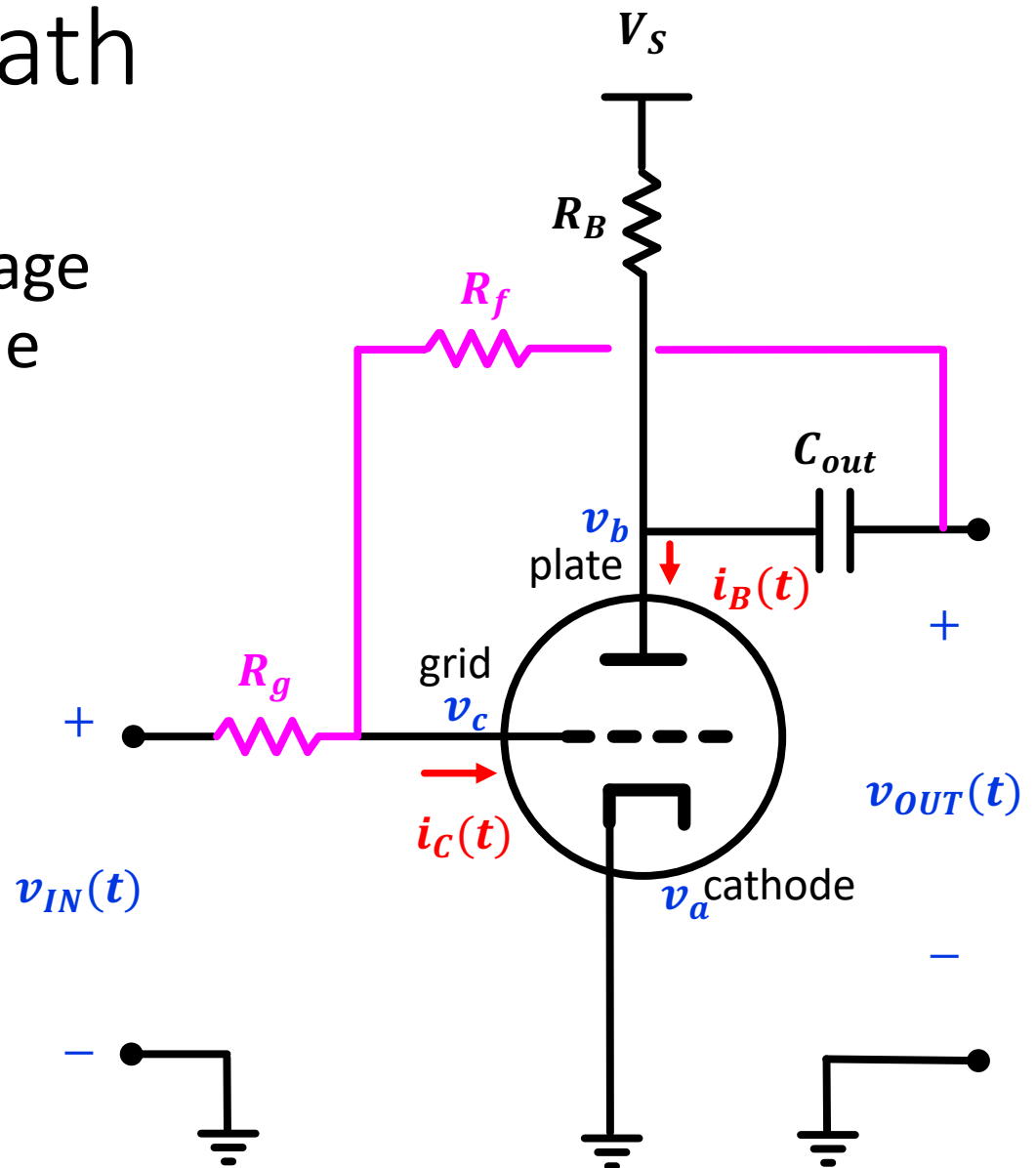

# So Putting This Together:

$$v_c = v_{in} + (v_{out} - v_{in}) \frac{R_g}{R_g + R_f}$$

$$v_c = \frac{v_{out}}{A_o(*)}$$

Therefore:

$$\frac{v_{out}}{A_o(*)} = v_{in} + (v_{out} - v_{in}) \frac{R_g}{R_g + R_f}$$

Therefore:

$$v_{out} \left( \frac{1}{A_o(*)} - \frac{R_g}{R_g + R_f} \right) = v_{in} \left( 1 - \frac{R_g}{R_g + R_f} \right)$$

Therefore:

$$\frac{v_{out}}{v_{in}} = \frac{\left( 1 - \frac{R_g}{R_g + R_f} \right)}{\left( \frac{1}{A_o(*)} - \frac{R_g}{R_g + R_f} \right)}$$

Therefore:

$$\frac{v_{out}}{v_{in}} = \frac{A_o(*)R_f}{(R_g + R_f - A_o(*)R_g)}$$

Therefore:

$$v_{out} = \frac{A_o(*)R_f}{(R_g + R_f - A_o(*)R_g)} v_{in}$$

# Conclusions I

- The result of this feedback had some interesting properties...
- Let's say we had a non-linear amp system where the *gain was a simple function* of  $v_{in}$  such that:  $A_o(*) = -10v_{in}$
- If we just applied this to our known I/O equation:
  - $v_{out} = (-10 \cdot v_{in}) \cdot v_{in} = -10 \cdot v_{in}^2$ ...in other words,  $v_{out}$  is highly non-linear with  $v_{in}$
- In the context of feedback therefore:
  - $$v_{out} = \frac{-10v_{in}R_f}{(R_g + R_f - 10v_{in}R_g)} v_{in}$$
- For reasonable values for those resistors, this equation is actually more “linear” than the original


# Conclusions I

$$v_{out} = -10 \cdot v_{in}^2$$

vs.

$$v_{out} = \frac{-10v_{in}R_f}{(R_g+R_f--10v_{in}R_g)} v_{in}$$
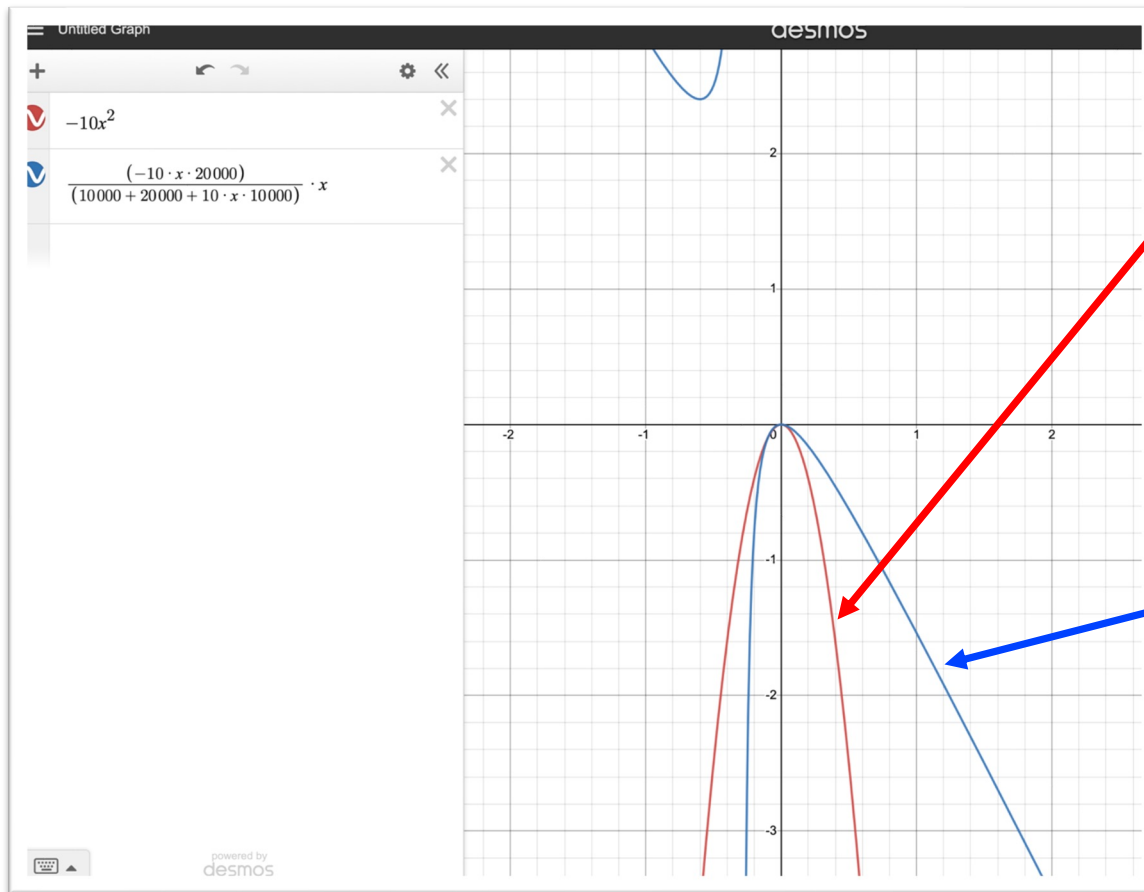
$$R_f = 20\text{k}\Omega \quad R_g = 10\text{k}\Omega$$



*The original open loop exhibits highly non-linear relation of input to output*

*The system with closed loop negative feedback exhibits a shape that looks more linear-ish, albeit at a lower gain aka shallower slope!*

# Conclusions II

- Further investigation reveals another interesting pattern. And this one is **critical**:

- For the equation  $v_{out} = \frac{A_o(*)R_f}{(R_g + R_f - A_o(*)R_g)} v_{in}$  as the overall magnitude of  $A_o(*)$  gets larger and larger, ( $A_o(*) \rightarrow \infty$ ) both top and bottom of the fraction become dominated by it and the overall equation will simplify to the following:

- $v_{out} \approx -\frac{R_f}{R_g} v_{in}$

# Conclusions I

- The result of this feedback had some interesting properties...
- Let's say we had a non-linear amp system where the gain was a simple function of  $v_{in}$  such that:  $A_o(*) = -1000v_{in}$
- If we just applied this to our known I/O equation:
  - $v_{out} = -1000 \cdot v_{in} \cdot v_{in} = -1000 \cdot v_{in}^2$ ...in other words,  $v_{out}$  is highly non-linear with  $v_{in}$
- In the context of feedback therefore:
  - $$v_{out} = \frac{-1000v_{in}R_f}{(R_g + R_f - 1000v_{in}R_g)} v_{in}$$
- For reasonable values for those resistors, this equation is far, far more "linear" than the original


# Conclusions II

$$v_{out} = -1000 \cdot v_{in}^2$$

vs.

$$v_{out} = \frac{-1000v_{in}R_f}{(R_g+R_f--1000v_{in}R_g)} v_{in}$$
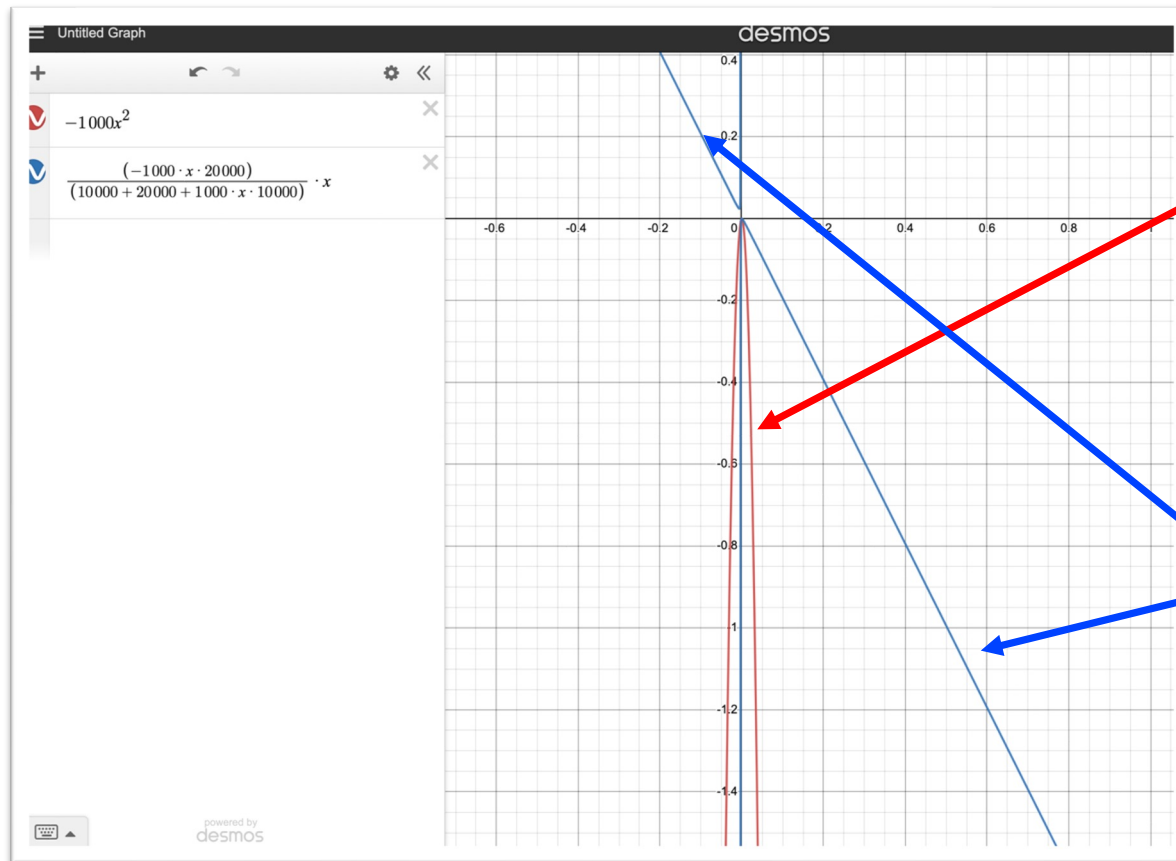
$$R_f = 20\text{k}\Omega \quad R_g = 10\text{k}\Omega$$



*The original open loop exhibits highly non-linear relation of input to output*

*The system with closed loop negative feedback exhibits a shape that is essentially linear!*

# Conclusions IIb

- Because of the invention and perfection of negative feedback the exact “shape” of a tube’s gain became less important
- What became important was that you have *a lot of gain*. If you can have a lot of gain, even if non-linear, you can trade it off for a more linear behavior of gain at a more moderate overall magnitude of gain
- This freed up engineers to push forward with making higher gain tubes and not obsess so much with the linearity of the tube itself! The circuit it lives in can fix that problem.



# Results are Shockingly Good

- The original Harold Black paper from 1934, arguably one of the greatest EECS papers of all time imo, is built around the study of this circuit:
- A multi-stage tube amplifier with the output negatively fed back to the input:


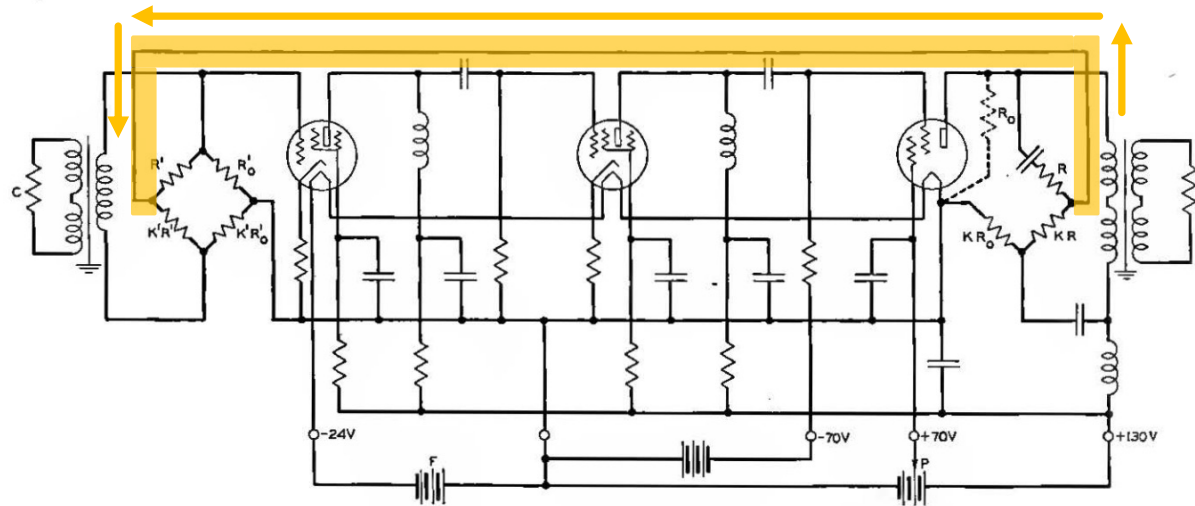


Fig. 2—Circuit of a negative feedback amplifier.
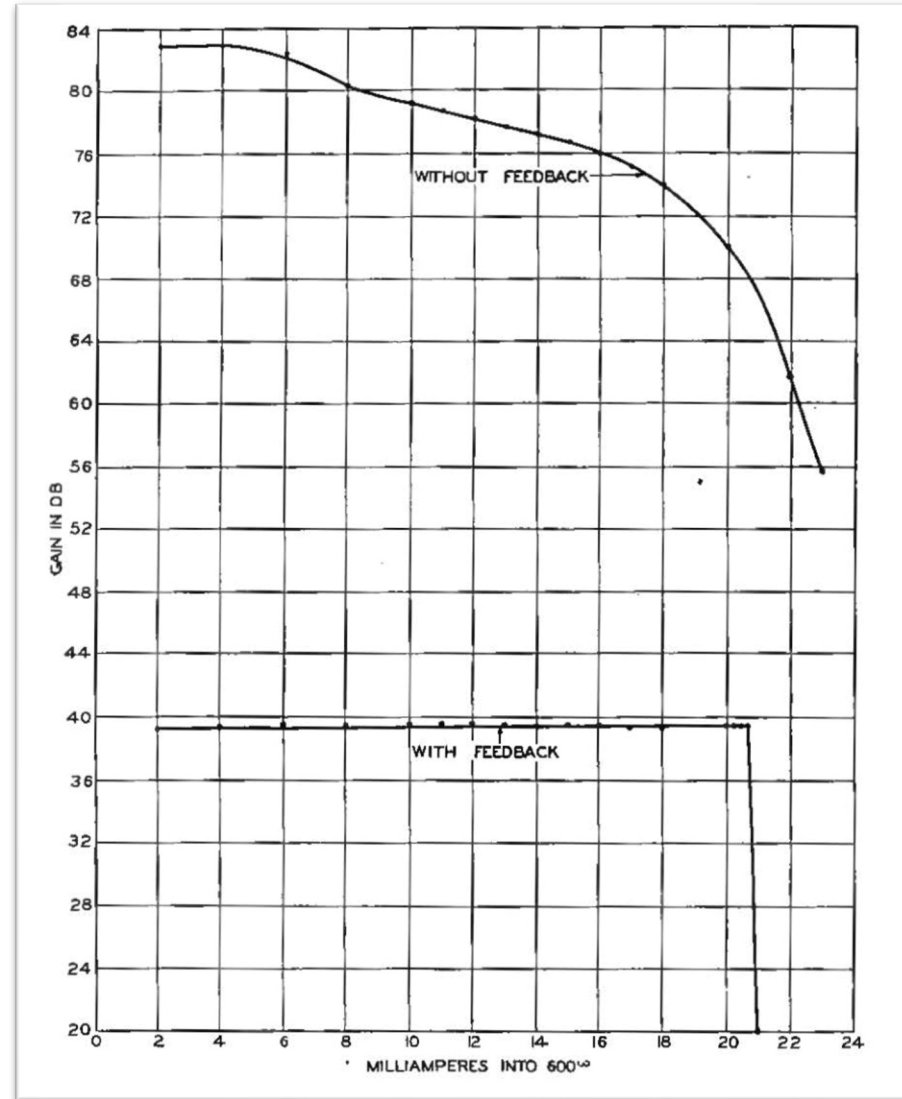
# Compare that circuit with/without feedback

- Gain now stays flat for a variety of output loads! (showing how as value of resulting output signal goes up/down, it stays proportional with input signal)
- Non-linearity suppressed at the expense of lower overall gain



H.S. Black, "Stabilized feed-back amplifiers", *Electrical Engineering*, vol. 53, pp. 114-120, Jan. 1934.


1/22/25

6.S917 IAP 2025

62

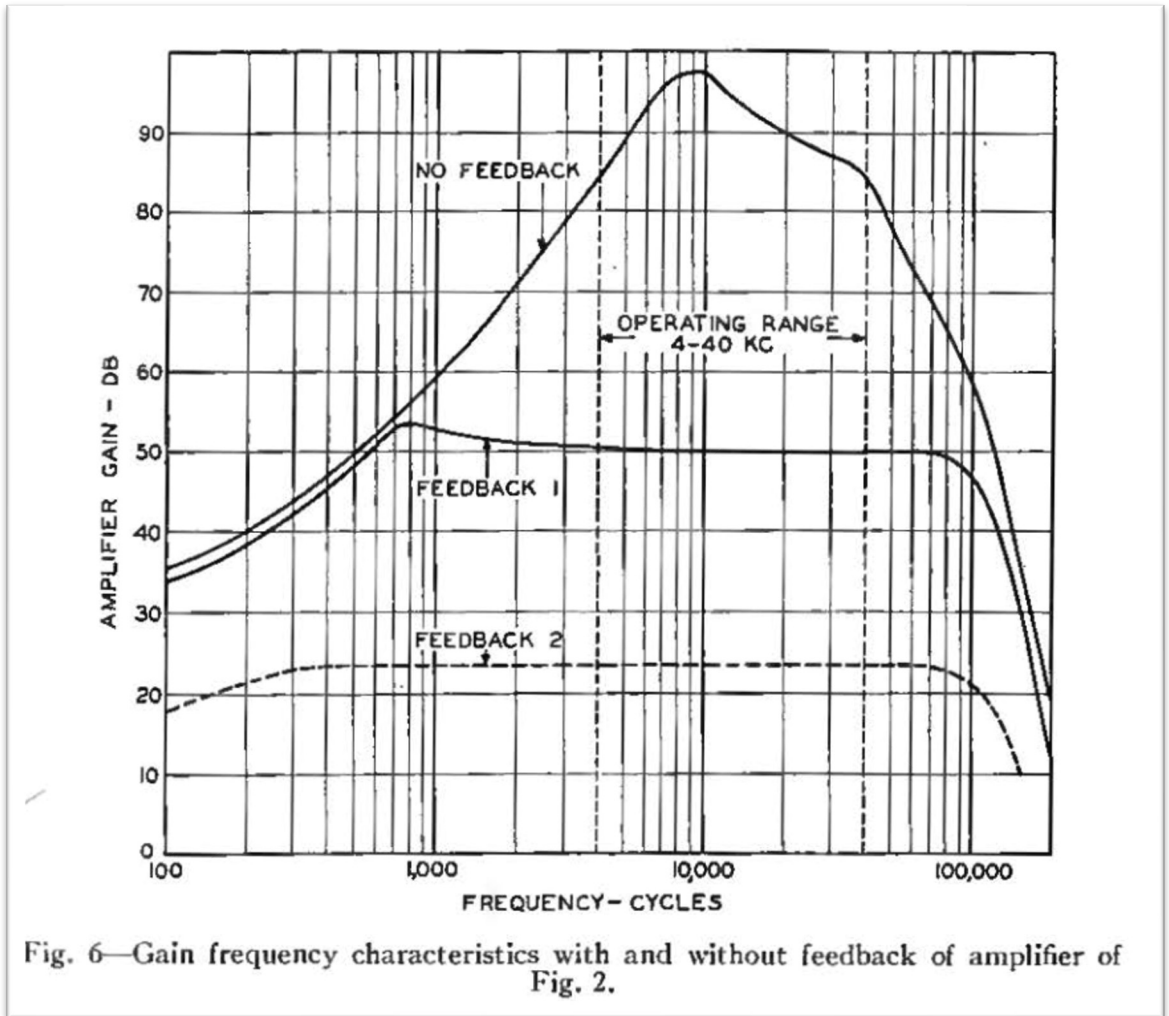
# Works in Frequency Space Too!

- Gain stays constant for a variety of frequencies!
- Yes it is lower overall in magnitude but it is consistent!


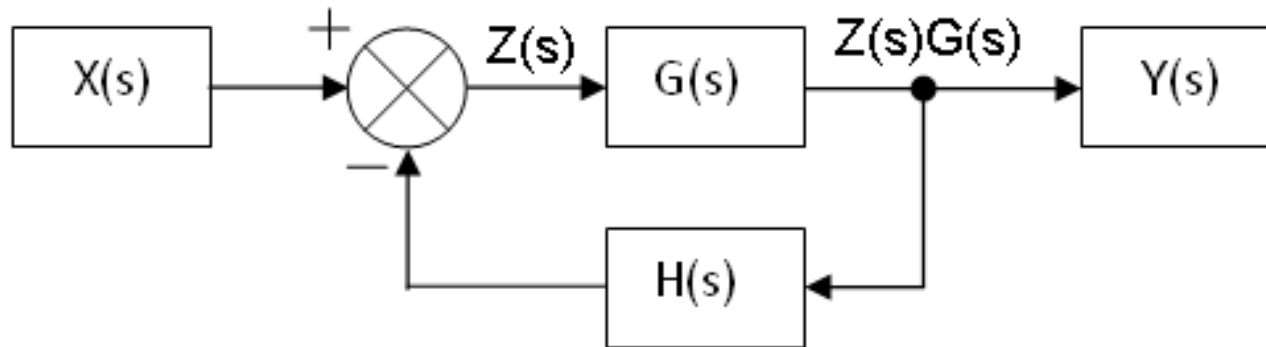
# This result

- All modern control theory is built around the work of Black:



- As an EE or EECS person or whatever, this is one of the most fundamental and important concepts/achievements in existence

[https://en.wikipedia.org/wiki/Closed-loop\\_transfer\\_function](https://en.wikipedia.org/wiki/Closed-loop_transfer_function)


# Now Let's Return to Armstrong and his circuits

- So...
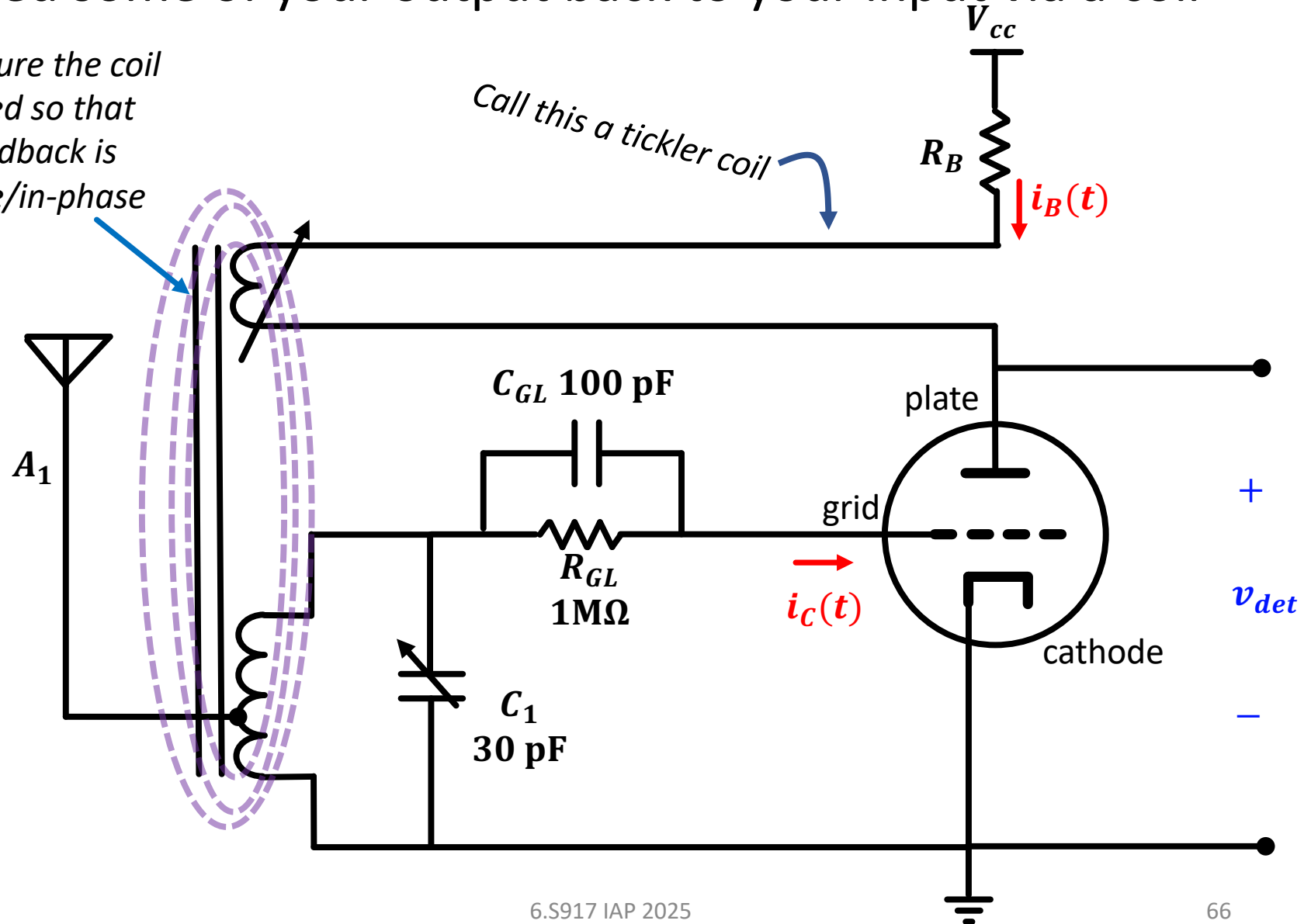
# Armstrong's Regeneration Receiver


- Feed some of your output back to your input via a coil

Make sure the coil is flipped so that this feedback is positive/in-phase



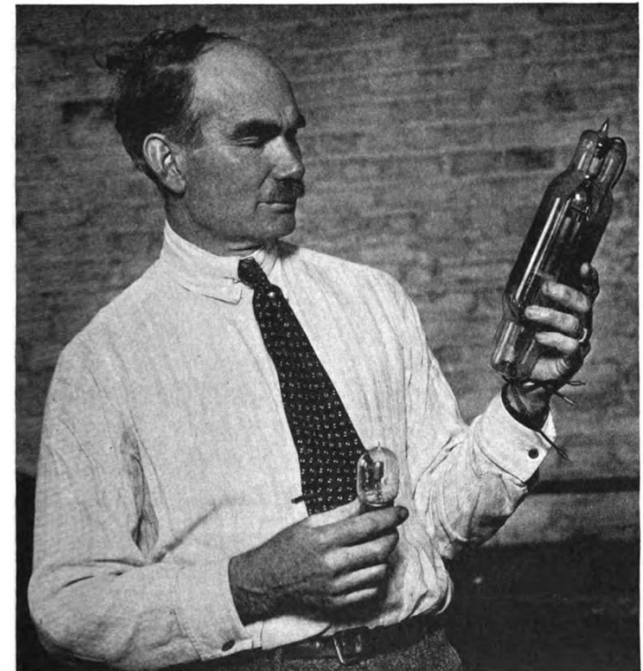
# ~1914/5...

- Remember Lee de Forest?
- First person to put a third wire into a thermionic tube
- He had like a dozen companies that failed and always seemed to become friends with shysters and conmen/conwomen
- Sued lots of people
- Declared himself to be “father of radio” later in life
- But it is largely established that he invented the “triode” which he called the “audion”
- Had no idea really how it worked


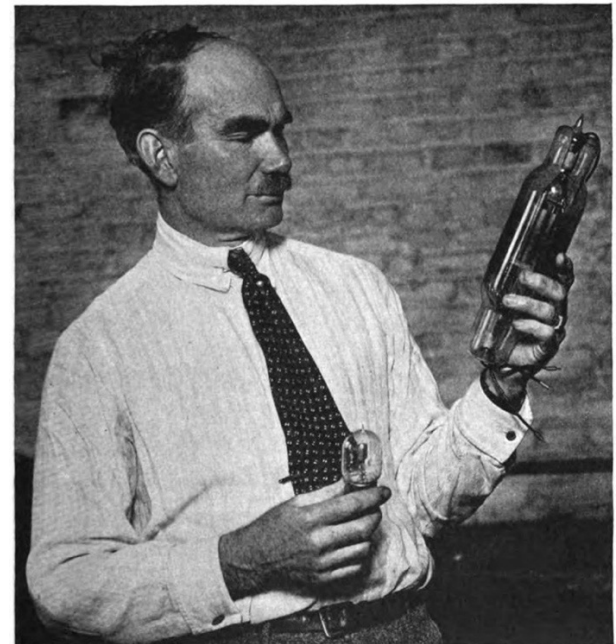
# Well de Forest Sued Armstrong


- He claimed he had invented regeneration based on some unclear doodlings from 1912, and he and Armstrong started fighting a very long drawn out legal battle that lasted ten years...well into the 1920s
- Went all the way to the Supreme Court and in 1924 it sided with De Forest much to the surprise of the entire engineering field.
- Armstrong was bummed out, but by this time all the patents had been inter-licensed so it wasn't a huge loss.
- And by then other things were being designed




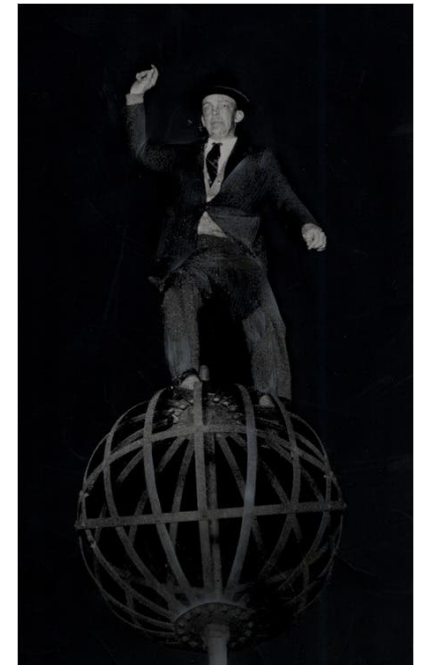
# A Better Regenerative Receiver

- Armstrong kept experimenting and developed a regenerative design that used a local oscillation to selectively filter and “quench” undesired feedback oscillations.
- As a result you could drive your receiver further into feedback and not “transmit” ...gains of over 1 million were possible but circuit was very finicky
- Called it...
- The superregenerative receiver and patented in 1922.
- Sold it, made more green




# Armstrong Kept Doing Stuff

- He was in the signal corps during WW1. Made some more inventions (come back to one in sec)
- Got married, made his wife the first known-portable radio (weighed 50 pounds) as a wedding present, lol
- Became very tight with RCA




*Radio Corporation of America*

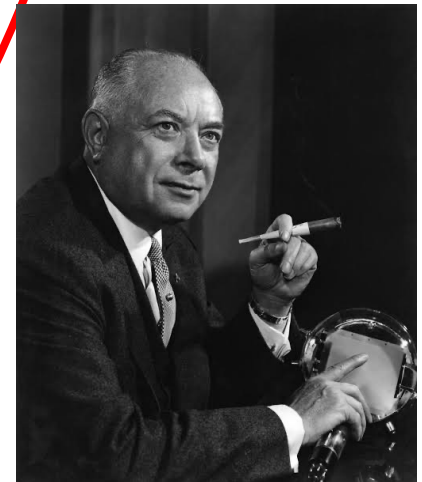


David Sarnoff, Leader of RCA
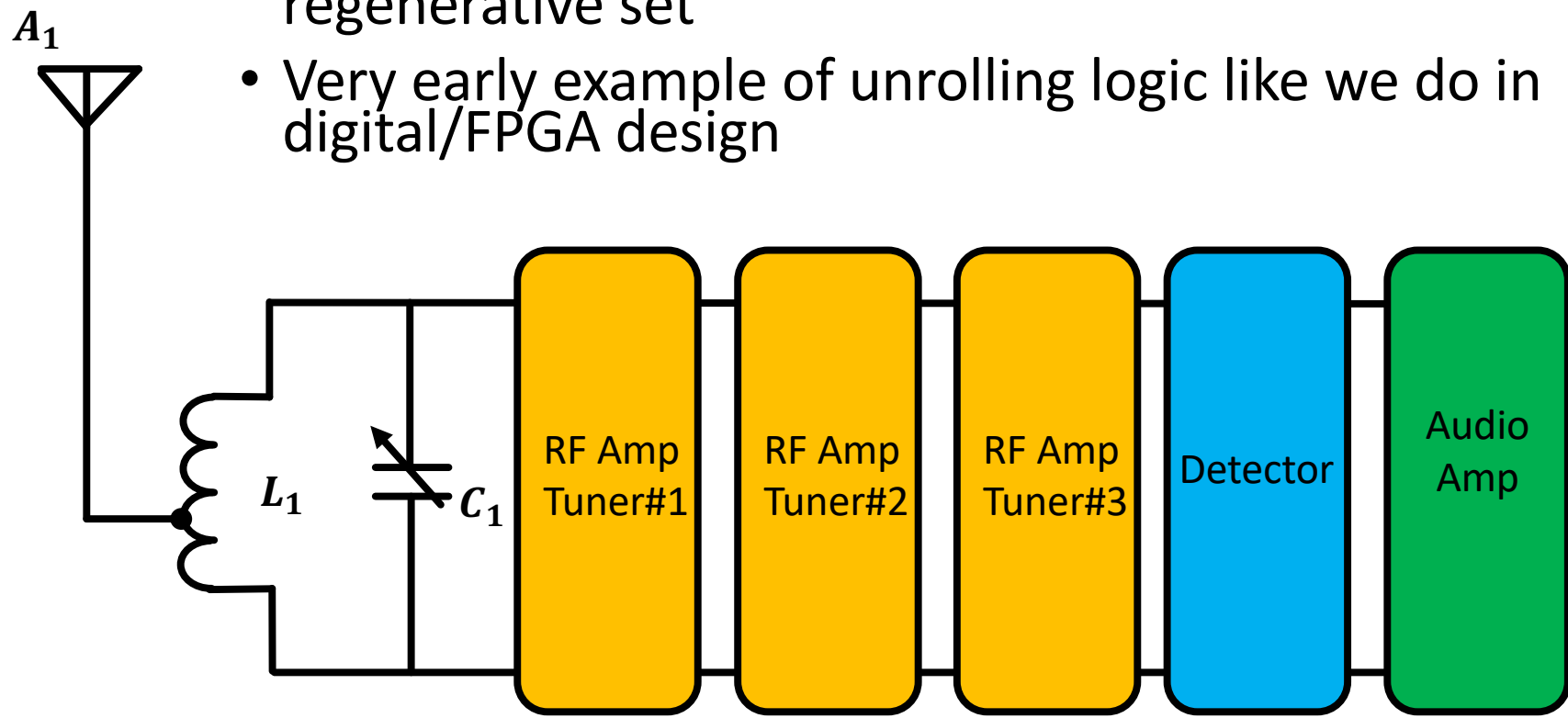
# The Tuned Radio Frequency Receiver

- Instead of reusing the same tube, use multiple tubes in series, other designs came out...
- Got around regeneration patents and as tubes got cheaper this wasn't as absurd
- It was also far less of a finicky design than a regenerative set
- Very early example of unrolling logic like we do in digital/FPGA design



# 1928 Bosch Radio Receiver Schematic

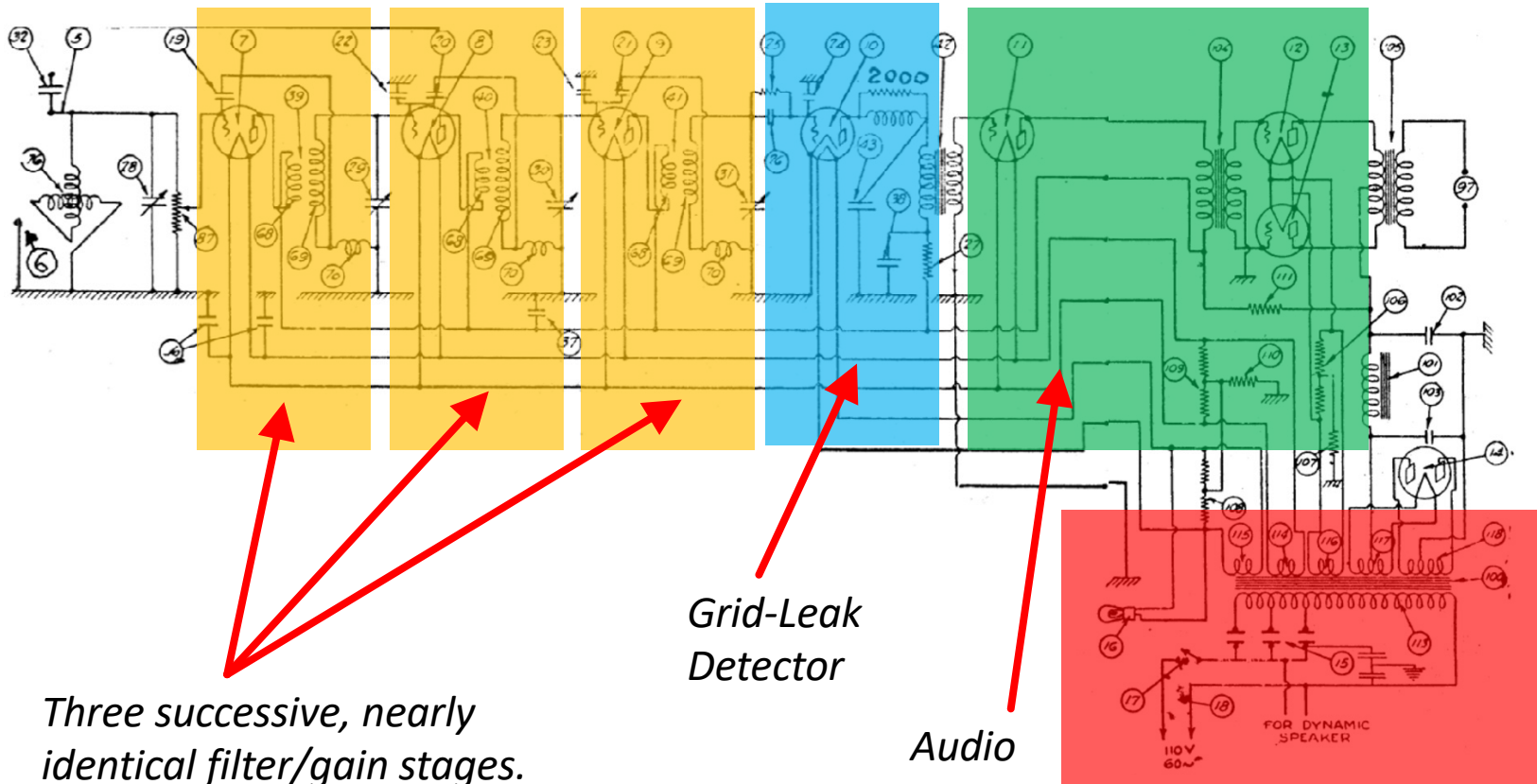

*Three successive, nearly identical filter/gain stages. Combined could have enough gain to compete with regenerative AND not have threat of oscillation!*

*Grid-Leak Detector*

*Audio Amps*

*Power Supply*

# More Tubes ==/!= Better?


- The appearance of the TRF designs motivated the notion that more tubes implied a better set.
- If done correctly, there was merit to this:
  - A four-stage TRF was better than a two-stage TRF
  - Also doing your audio amplification with several layers of tubes could result in more, cleaner signal
- However some radio manufacturers started just putting random tubes into sets to convey that they were better.
- “12-tube-6-tube sets” appeared: only used 6 tubes, even though there were 12 in the design doing nothing but consuming power.
- Wasn't always malicious, people were still figuring stuff out and there'd be weird trendy circuits that people thought were “better” but really did nothing...or did the same thing less efficiently.
- Weird times.

# Armstrong already coming up with even better solution



- Regenerative worked, but was finicky and dangerous
- The superregenerative worked but was even more complicated and finicky
- TRF worked pretty well, but needed a lot of tubes and wasn't very amazing with selectivity:
  - It is very hard to have a variable filter maintain the exact same relative shape as you vary its resonant frequency
  - Also working at raw radio frequencies is hard...it would be nice if you could do your pre-demodulation work/filtering at lower frequencies


# Having a Variable Tuner

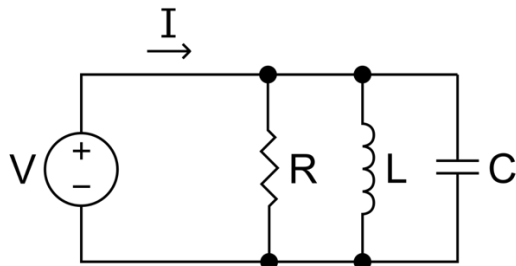

$\omega_o$  is always going to be  $= 1/\sqrt{LC}$

But the quality factor  $Q$  which relates to how selective a filter is is expressed with this:  $Q = R\sqrt{\frac{C}{L}}$

*Very good here*

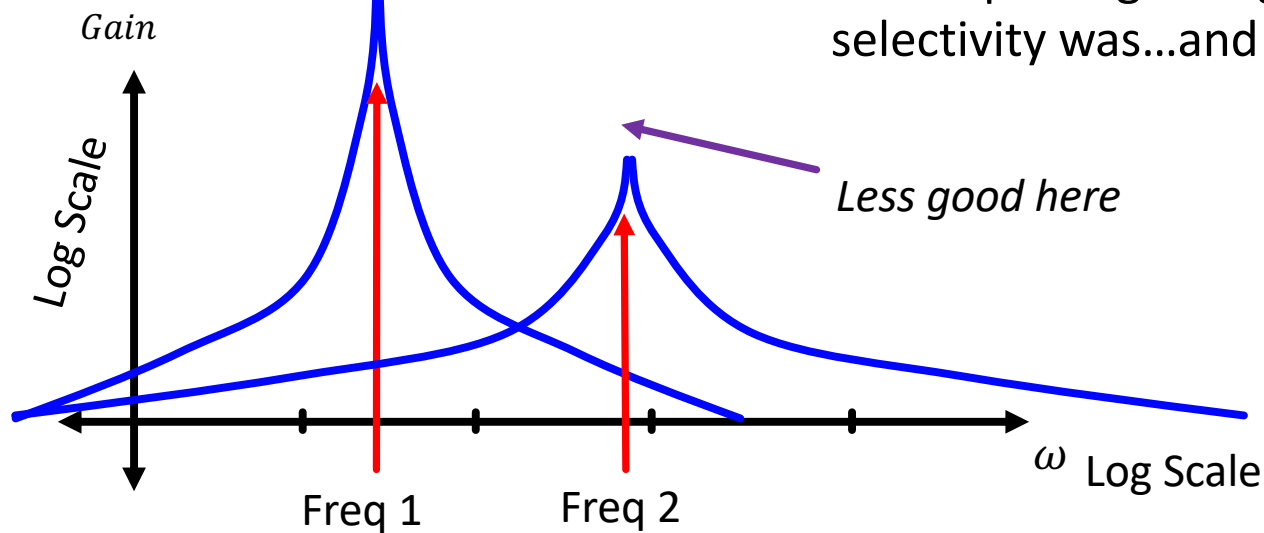

So as you tuned around with your radio varying the capacitance (or L), you were also impacting how good/bad your selectivity was...and that's not ideal

# Solution:

- Do all of the filtering at the same exact frequency regardless of what frequency your station is at.
- This way you could just have a bunch of unmovable filters targeting that fixed frequency that were perfectly calibrated.
- Seems simple, yes???

*Are you crazy?* “Do all of the filtering at the same exact frequency regardless of what frequency your station is at.” Do you realize how crazy that sounds? It sounds like communism or something....everyone will get paid the same amount of money regardless of the amount of money they earn.



# Mixing Signals (Down-Mixing)

- Based around multiplication of sine waves (remember from other week?)
- Let's say we have the following signal coming in:

$$v_c(t) = A_{s_1} \sin(2\pi f_{s_1} t)$$

- If we multiply that signal by a locally generated sine wave of frequency  $f_{s_1} - f_{IF}$  where  $f_{IF}$  is some low frequency value (for AM let's say 455 kHz), we'd get:

$$A_{s_1} \sin(2\pi f_{s_1} t) \cdot \sin(2\pi(f_{s_1} - f_{IF})t) =$$

$$A_{s_1} \cos(2\pi(2f_{s_1} - f_{IF})t) + \cos(2\pi(-f_{IF})t)$$

# Resulting frequencies

- We have two sinusoids as a result:

$$\cos(2\pi(2f_{s_1} - f_{IF})t) - \cos(2\pi(f_{IF})t)$$

This one is higher than starting radio signal. Ignore/filter it

This one is at lower frequency. Keep it.


- What if we want a different signal at frequency  $f_{s_2}$ ? Do same thing except this time multiply incoming signal of frequency  $f_{s_2} - f_{IF}$  The result will be:

$$\cos(2\pi(2f_{s_2} - f_{IF})t) - \cos(2\pi(f_{IF})t)$$

This one is higher than starting radio signal. Ignore/filter it

This one is at lower frequency. Keep it. Also it is the same frequency as first case!!!

# The Superheterodyne Receiver

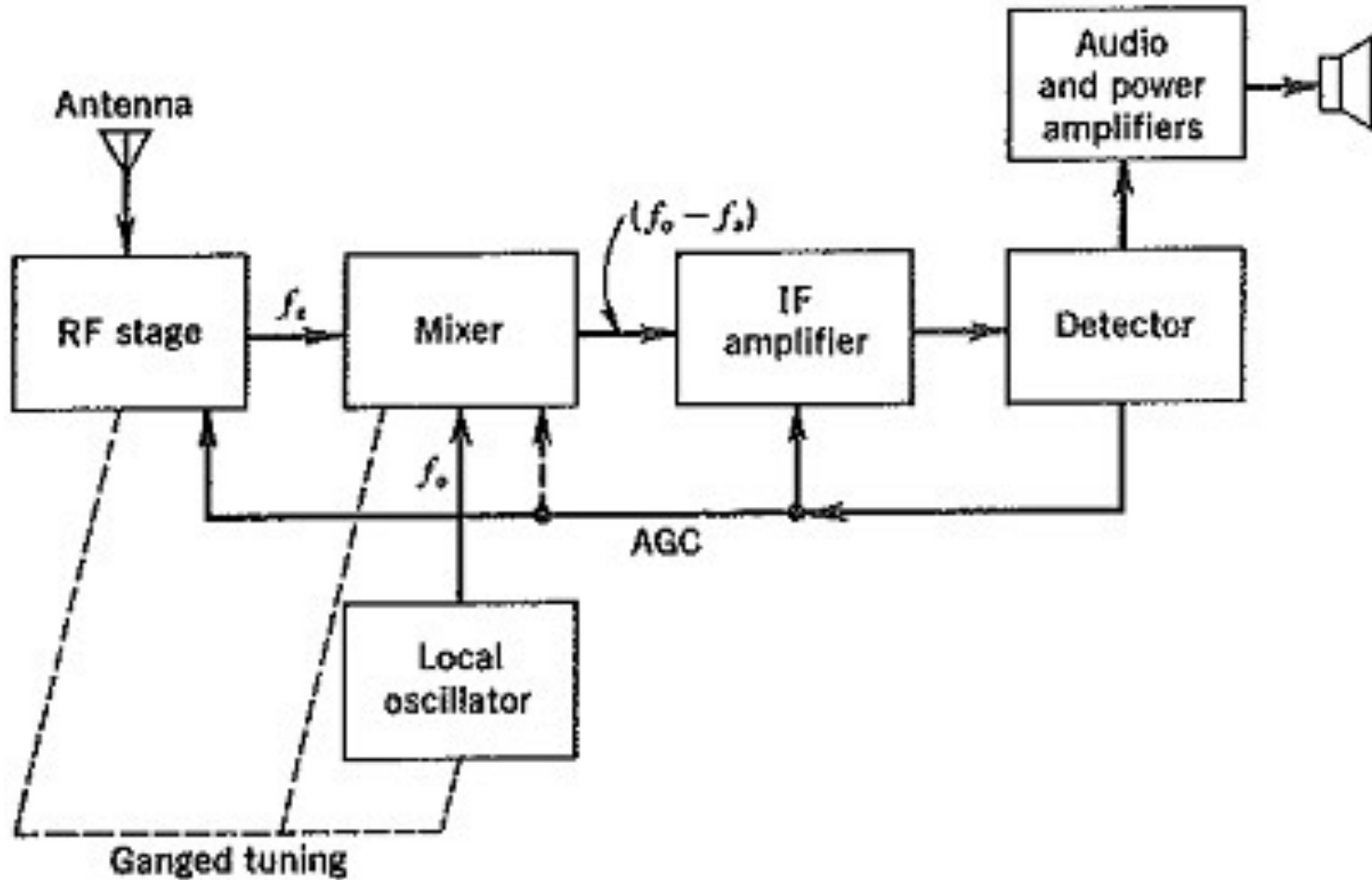

**FIGURE 6-2** The superheterodyne receiver.

# The RF Stage

- Up front have a pentode that can work at high frequencies perform some initial amplification.
- Also have a broad selection filter that is tunable that can remove some out-of-signal junk

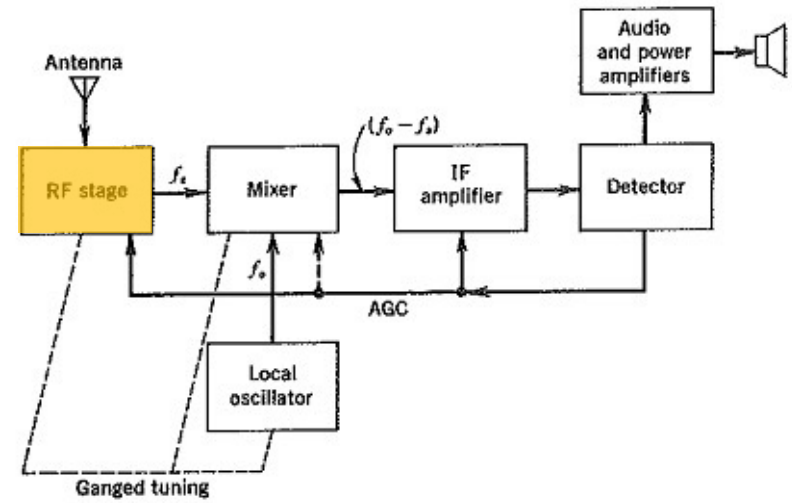


FIGURE 6-2 The superheterodyne receiver.

# The Local Oscillator (aka “LO”)

- Have a tube-driven local oscillator circuit that runs at a frequency  $f_{IF}$  below what we are trying to tune for

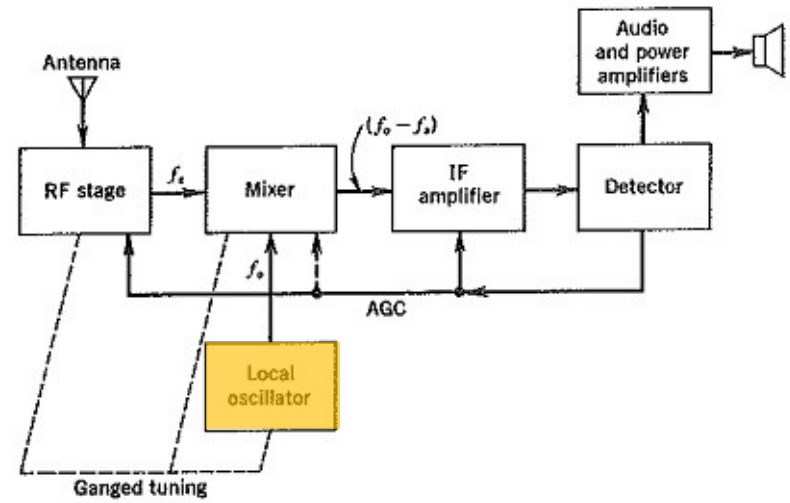


FIGURE 6-2 The superheterodyne receiver.

# Ganged Tuning

- Have the variable C's (or L's) "ganged" together so that when you vary the RF tuning filter, you also vary the LO so it remains at the correct frequency offset



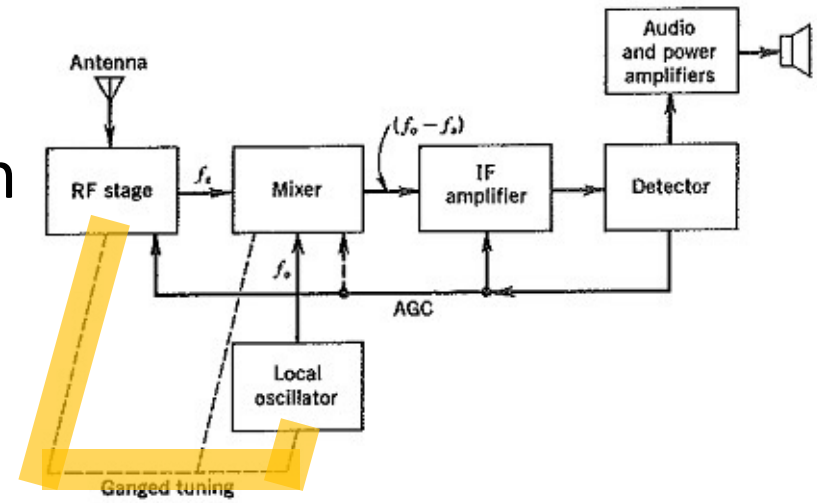


FIGURE 6-2 The superheterodyne receiver.

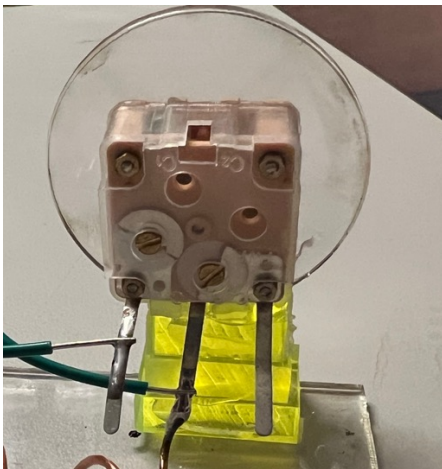

Schematic of lab 1 tuning cap

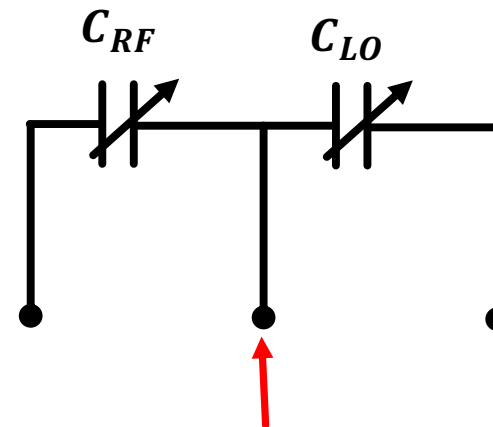

Ground me

<https://www.eeeguide.com/superheterodyne-principle/>

# The Mixer

- This is the stage that "mixes" (multiply in this context) the two signals to get the IF out.
- If the RF stage and the LO are properly synchronized the IF should always be the same
- IF stands for "Intermediate Frequency"

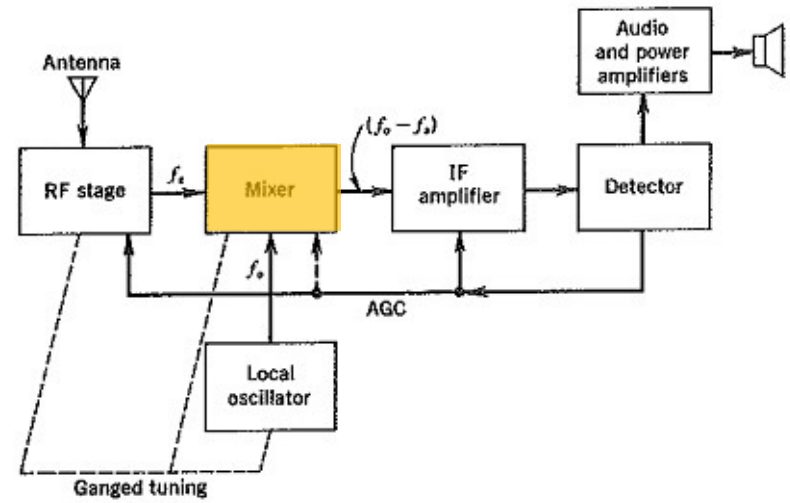


FIGURE 6-2 The superheterodyne receiver.

# How Do We Multiply?

- Silly question. We already went over this.
- We have amplifying devices that can be made to work in non-linear modes of operation. Add the signals you care about together, and run them through a tube in a particularly non-linear region and harvest the squaring signals (via F.O.I.L.) that come out and block with some filters!
- Profit
- Moving on...



# The RF/Mixer/LO

- For AM, sets usually targeted an IF of 455 kHz.
- So if you wanted 1080kHz in the AM band...
  - Your RF stage BPF set at 1080kHz
  - Your LO be set at: 625 kHz
  - Mixer/filter yields  $1080 - 625 = 455$  kHz
- If wanted 1500kHz in AM band...
  - Your RF stage BPF set to 1500 kHz
  - Your LO be set at 1.045MHz
  - Mixer/filter yields  $1500 - 1045 = 455$  kHz

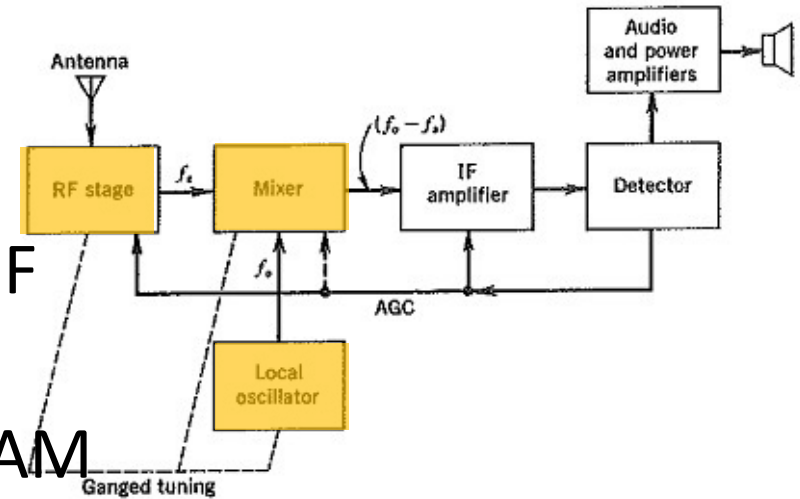


FIGURE 6-2 The superheterodyne receiver.

# The IF Amp

- This circuit can be special-made to work in and around the IF.
- This ability to not have to be flexible with center frequency can allow very nice tuning of the circuit overall (and very good filtering of signals outside our signal window)
- Note the signal is still modulated (AM...later FM or PM) in the IF

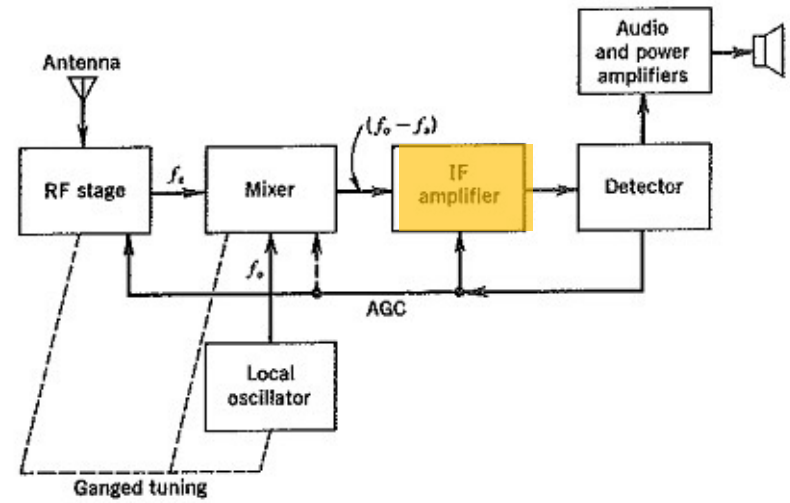


FIGURE 6-2 The superheterodyne receiver.

# The Detector

- Finally demodulate using the ways we've discussed.
- This stage isn't much different than other ways before
- But easier to build since it only had to demodulate at one specific frequency

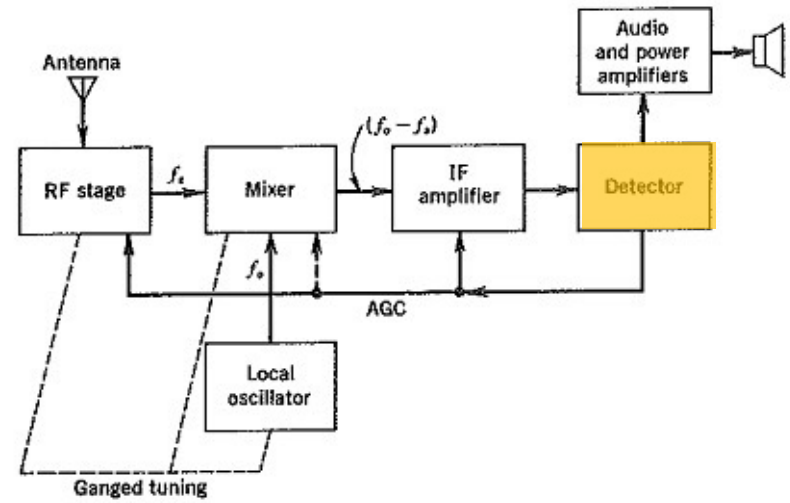


FIGURE 6-2 The superheterodyne receiver.

# The Audio Amplifier

- Just make the audio louder (scale in power)
- All good!

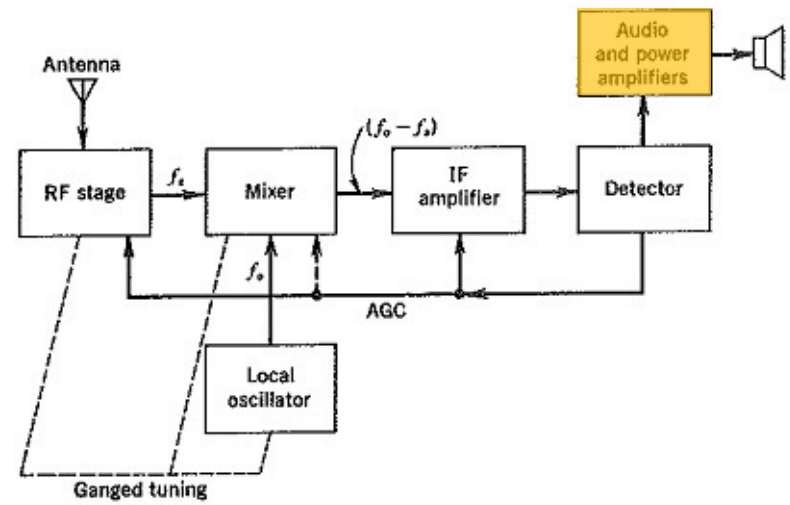


FIGURE 6-2 The superheterodyne receiver.


# The Superheterodyne



- Armstrong wasn't the only inventor of heterodyning, but he did have the dominant US patent and he did get the earliest versions of it working
- Sold that patent to RCA as well..made so much money that he basically set up his own privately funded research lab to keep working on stuff.
- *To this day*, most radio stuff (WiFi, etc...) utilizes some flavor of heterodyning in its signal path. It is a very important signal processing technique.
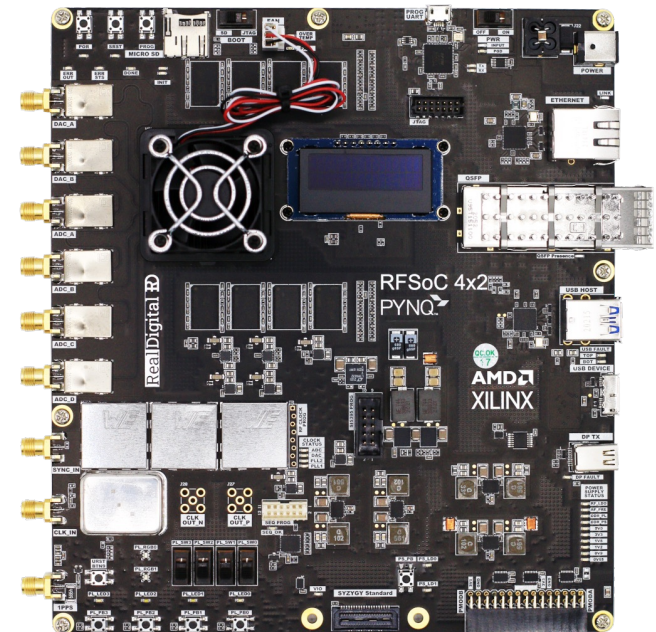
# Even in modern systems...

- Still heterodyne
- The RFSoc we use in 6.S965...
  - Sample at 5Gsp
  - Just do down conversion (heterodyne) digitally rather than in analog



# RCA

- RCA dominated the radio ecosystem in the 1920s and 1930s...they were the Radio Corporation of America after all
- Had the Armstrong superheterodyne patent so RCA radios were very good compared to competitors that were mostly TRFs by this point (which needed a lot more tubes and could not compete with superheterodyne sets in terms of performance)
- RCA built and owned radio stations and networking.
- You listened to RCA content on RCA stations using RCA radio sets. Seems perfectly American.



# FM

- Armstrong got annoyed by the noise that AM radio was prone to so he invented FM (his greatest invention)
- RCA, who Armstrong was close with, did not like this because it endangered their monopoly on AM... So they set up false patents to block/take over FM and had money to litigate and stall Armstrong
- Huge patent fight...drawn out for decades.
- Armstrong lost all his money and jumped off a building in 1954...everyone blamed RCA/Sarnoff
- His wife continued the patent fight and eventually won them 10-20 million in damages





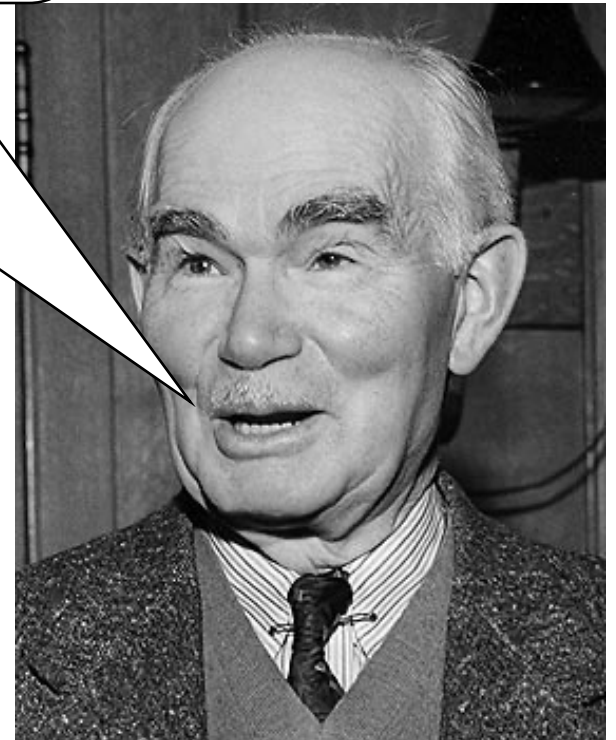
# DeForest...

“I have always taken the keenest delight in having beaten him so thoroughly on the feed-back question... after all, Armstrong has gone and I am alive, well and happy, and hope to live for many years more. What a contrast!”

- This guy sucked
- He died largely penniless in the late 1950s still claiming to have invented everything



# Commodity Radios

- Superheterodyning enabled cheap, good radios.
- Radios proliferated.
- Even in the 1930's/depression, this was how people connected
- Radio was *the internet* of the 1920s-early 1950s before being supplanted by TV.

# 1929 Bosch Model 28

- About \$135 without tubes in 1929...new car was about \$300...that's a lot of money




# 1939 Firestone Air Chief Radio Model No. S7425

- Pre-war *budget set*.
- Made by Firestone (yes the tire company)
- Was a TRF rather than superheterodyne to avoid paying patent royalties to RCA
- Extremely dangerous set
- But...cost **\$19.95** with tubes in 1939


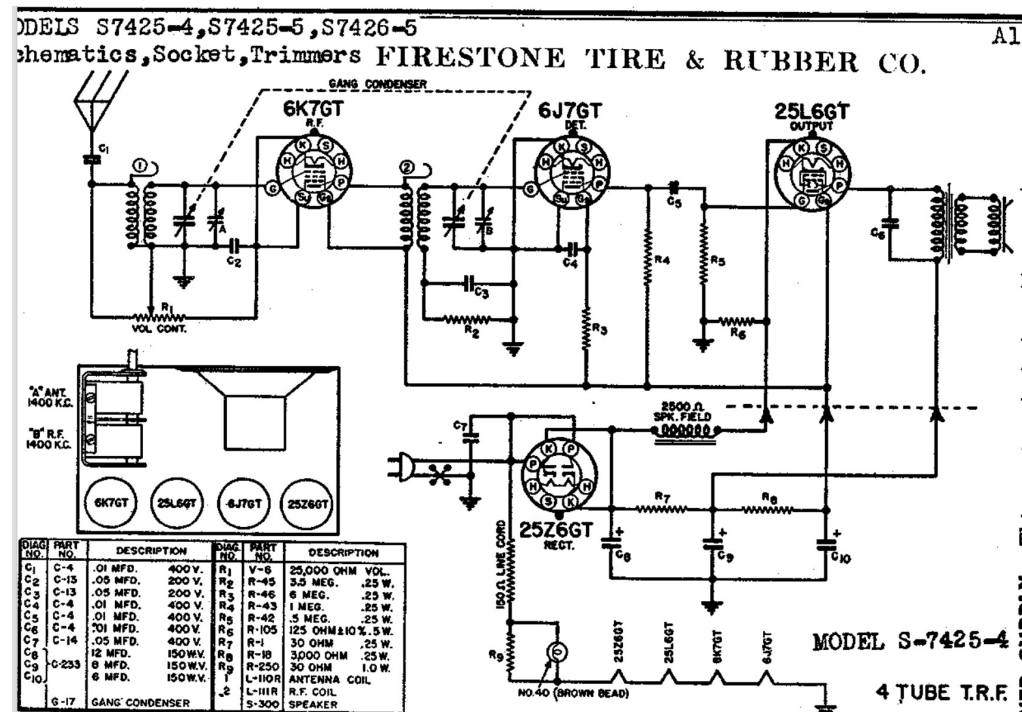
# S7425

- Non-isolated chassis
- Uses curtain-burner cord to drop voltage (about 35W)
- Not amazing reception...
- But it worked...




# S7425

Detector/Demodulate  
Use Pentode grid for nonlinearity

Audio Power Amp


Two stages of RF filtering

Power Supply

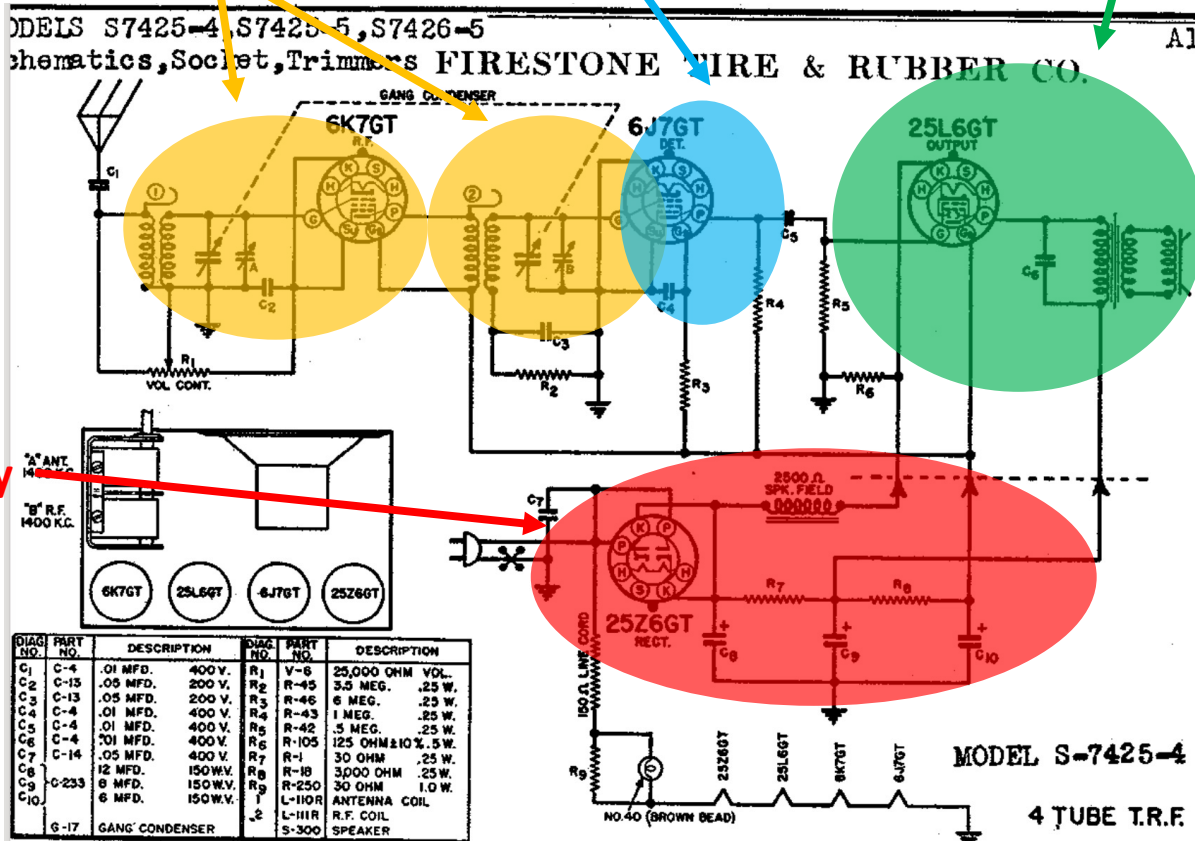
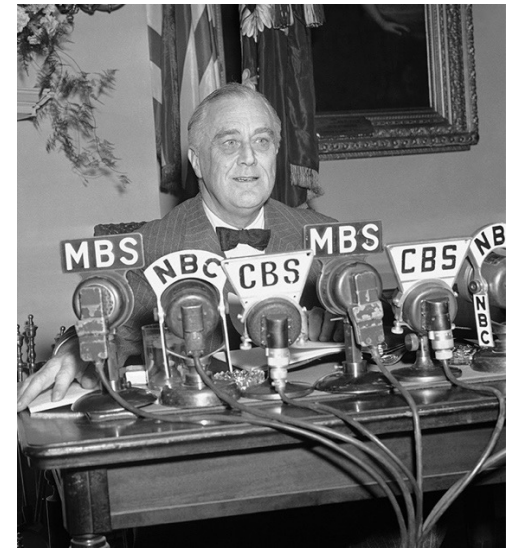
# Radio/Broadcast Audio Everywhere

- By 1930's, cheap, robust sets changed the world. Its impact could not have been understated
- Radio shows were listened to by millions
- Real-time news
- Events became lived
- Society became synchronized at all levels
- People got to hear leaders



*Fireside Chats by FDR*


# German Volksempfänger Radio

- Three tubes!

Audio Power Amp

RF Amp/Detector/First  
Audio

Power Supply

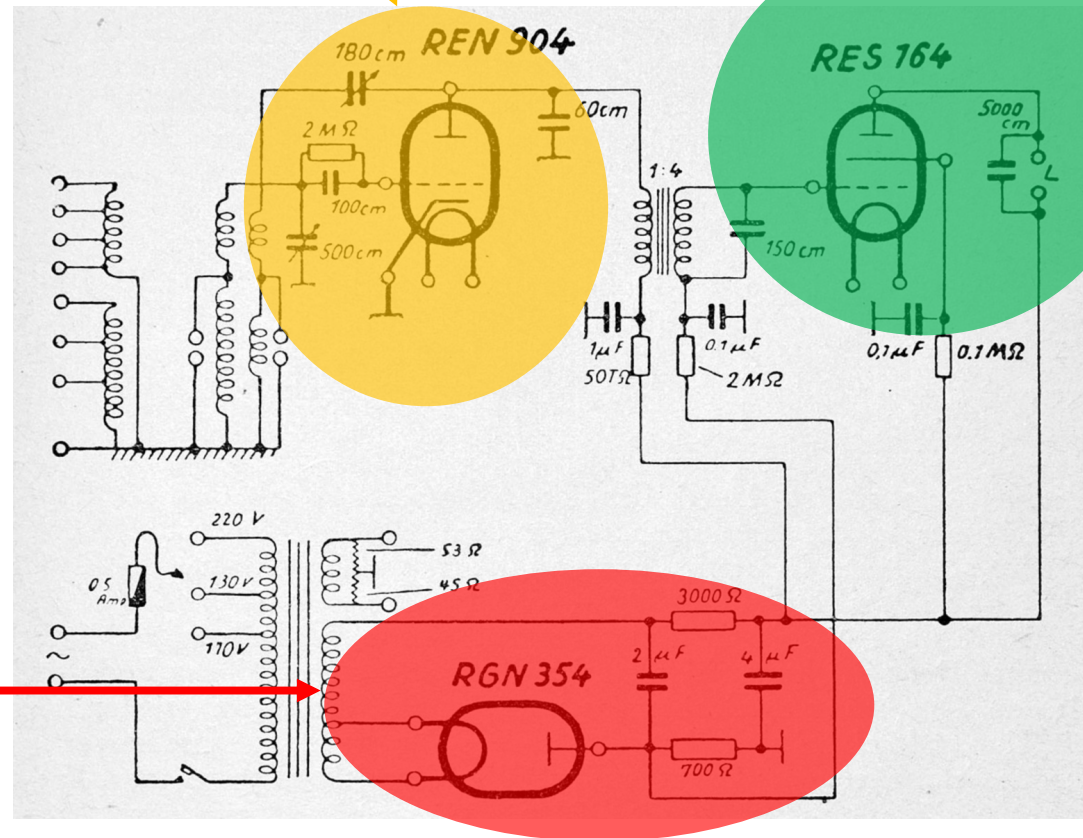



# The People's Radio: Nazi Germany

- Hitler and Goebbels charged engineers with designing an extremely simple and affordable tube radio
- Called *Volksempfänger*
- Millions of these sets sold...enabled propaganda to be blasted into everyone's houses



*Hitler's dictatorship differed in one fundamental point from all its predecessors in history. His was the first dictatorship in the present period of modern technical development, a dictatorship which made the complete use of all technical means for domination of its own country. Through technical devices like the radio and loudspeaker, 80 million people were deprived of independent thought. It was thereby possible to subject them to the will of one man...*

*-Albert Speer  
Nuremberg Trials 1946*

<https://en.wikipedia.org/wiki/Volksempf%C3%A4nger>

1/22/25

6.S917 IAP 2025

<http://oz6gh.byethost33.com/Volksempfänger.html>

A QUICK REMINDER

# What is net neutrality?

All traffic on the internet should be treated equally.


- NO BLOCKING** Your internet access provider (IAP) cannot block you from accessing legal content of your choice.
- NO THROTTLING** Your IAP cannot intentionally throttle legal internet traffic to slower speeds than other traffic.
- NO PAID PRIORITIZATION** Your IAP cannot sell 'fast lane' service to content providers who can pay more than others.

**Sorry, TikTok isn't available right now**

A law banning TikTok has been enacted in the U.S. Unfortunately, that means you can't use TikTok for now.

We are fortunate that President Trump has indicated that he will work with us on a solution to reinstate TikTok once he takes office. Please stay tuned!

[Learn more](#) [Close app](#)



**Welcome back!**

Thanks for your patience and support. As a result of President Trump's efforts, TikTok is back in the U.S.!

You can continue to create, share, and discover all the things you love on TikTok.

[Continue](#)

FORBES > INNOVATION > CONSUMER TECH

**TikTok Users Report Anti-Trump Content Being Hidden Following Platform's Unbanning**

Esat Dedezade Contributor ○  
Esat Dedezade is U.K.-based journalist who covers Big Tech for Forbes

[Follow](#)

Jan 22, 2025, 10:37am EST

TikTok users are reporting difficulties accessing content critical of President Trump on the platform. These reports follow similar recent criticisms raised against Meta over blocked Democrat-related search terms on Instagram, marking the latest developments in a series of content moderation controversies across major social media platforms this week.

**Karl Max** @KarlMaxxed · [Follow](#)

TikTok is now region locking Americans from looking

WORLD WIDE WEB FOUNDATION

BBC

Home News Sport Business Innovation Culture Ar

Instagram hides search results for 'Democrats'

1 day ago

Tom Gerken Technology reporter



# History Reminder

- The world was at war from 1937-1945. This was really the first techno-centric war. Vacuum tubes and radio were at the heart of it
- Much of our modern understanding of RF analog electronics was accelerated in pursuit of fighting each other during this time
- MIT really, really, really expanded during WW2 in terms of research

# Radio in WW2

- Direction Finding
- RADAR
- SONAR
- Electronic Warfare
- Countermeasures
- Early computer development...

[https://en.wikipedia.org/wiki/List\\_of\\_World\\_War\\_II\\_electronic\\_warfare\\_equipment](https://en.wikipedia.org/wiki/List_of_World_War_II_electronic_warfare_equipment)

# Radio Propaganda

- During the Occupation of France by Nazi Germany, England right across the channel would broadcast messages meant to coordinate the Resistance and other things.
- Battle of propaganda:
  - Germany broadcast to England
  - England to Germany/France
  - US to Japan
  - Japan to US



*Lord Haw Haw*

# WW2 Jamming

- Radios in occupied Europe would either be collected/confiscated or have their tuning capacitors fixed in place...varying them could lead to imprisonment/death...just listening to another station could be punished.


# “Wound my Heart with a Monotonous Langour”

- The Allied powers would routinely broadcast radio over Europe even while the Germans occupied countries.
- They’d intersperse messages for the resistance in it.
- Verlaine’s *Chanson d'automne* (“Autumn Song”) was used to indicate the Allied invasion of France was about to begin to soon so the resistance could prepare...
  - *Les sanglots longs des violons de l'automne* meant the invasion was coming within two weeks
  - *Blessent mon cœur d'une langueur monotone* meant the invasion was happening within 48 hours (broadcast on June 5, 1944)


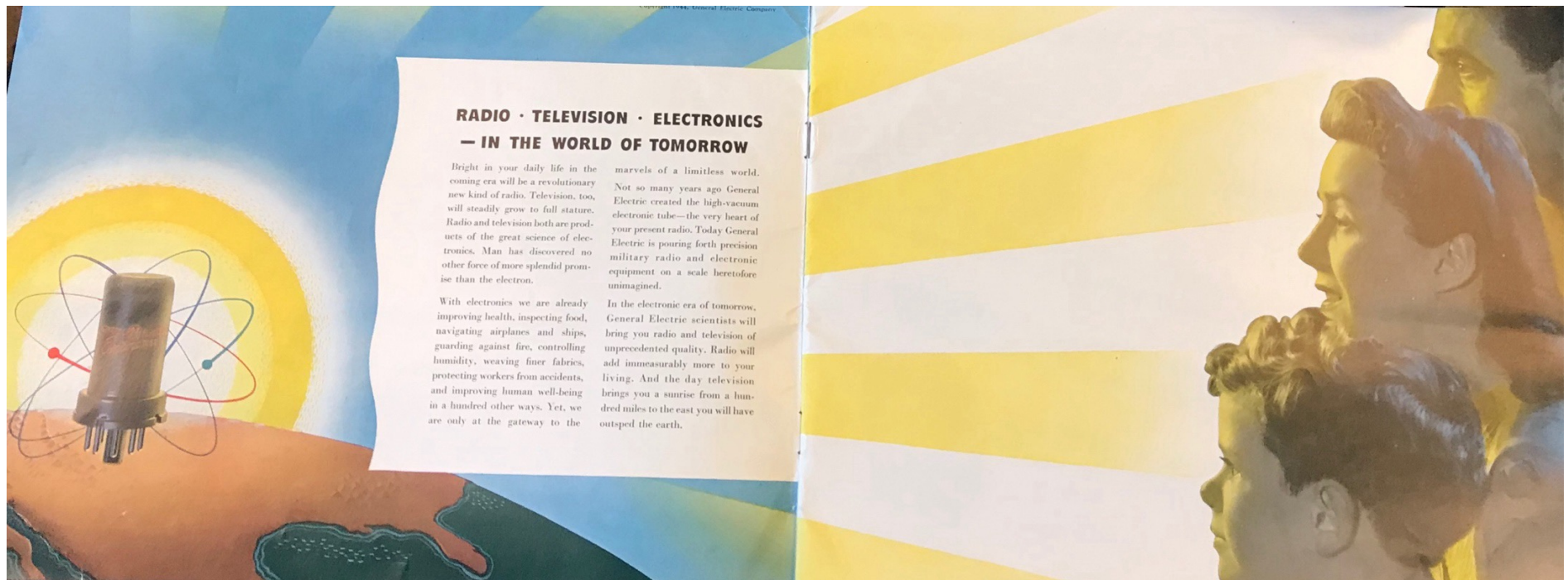
# Obsession, Hope?

- US stopped production of most consumer electronics (mostly radios) ~1941...became item of longing/black marketing in US



*1944 GE advertisement...they couldn't sell sets but they sent out teasers*




# 1953 Zenith L518

- Things went crazy after WW2 ended in 1945
- Postwar radio set, but still uses tubes in a superheterodyne configuration
- Not that different from prewar commodity sets
- An example of an “All American Five” set




# Zenith L518

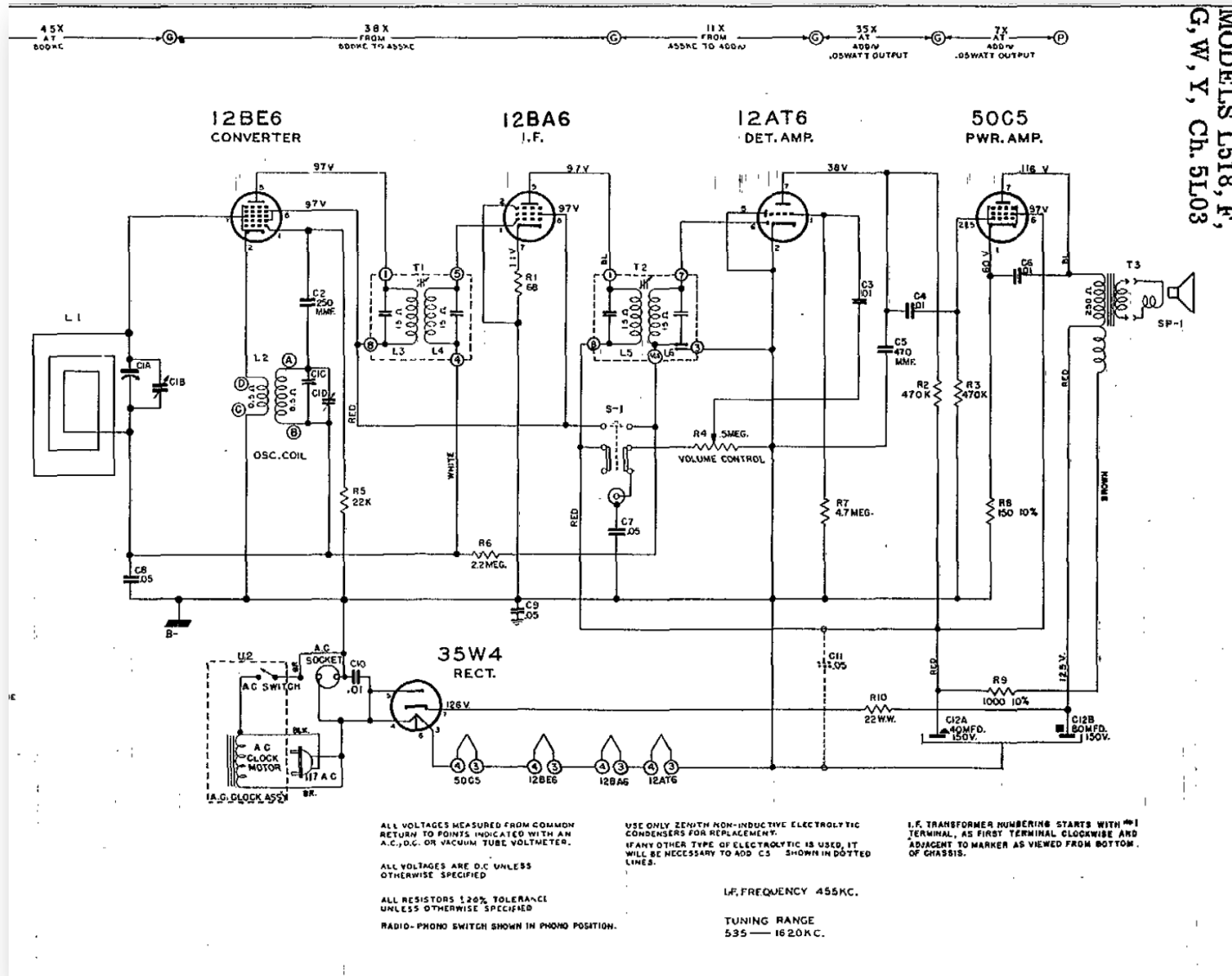



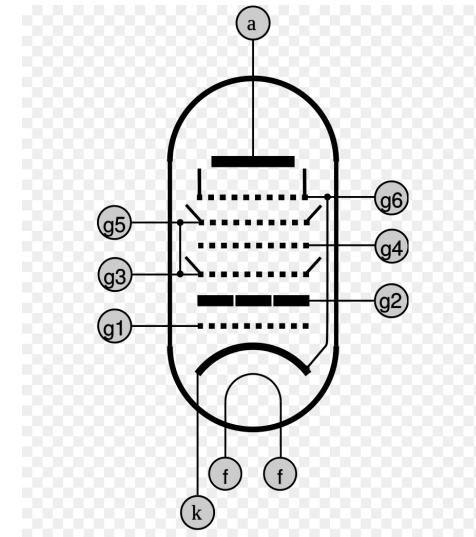
# The Pentagrid Converter

- A heptode tube (seven electrodes) or a octode tube that was used to do the following all in one package:
  - RF Amplification
  - Manage the Local Oscillator
  - Mix the two signals and output on IF
- Still a tube, but a tube that had a lot more functionality built in.
- You could think of this an early form of integrated circuit maybe



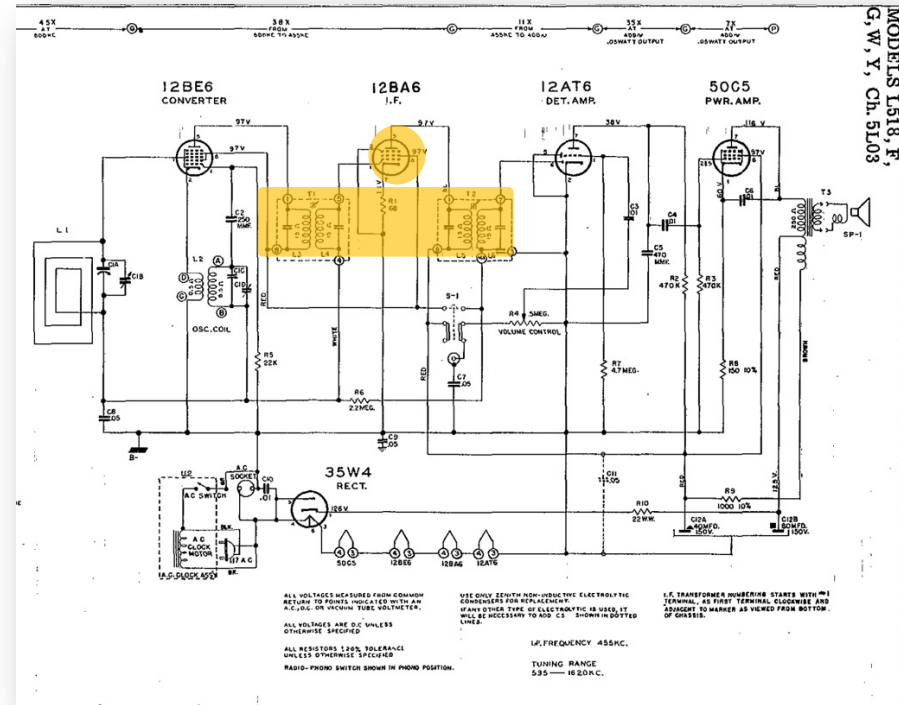
# IF Amp

- A 12BA6 pentode was used to amplify and filter at the IF of 455 kHz



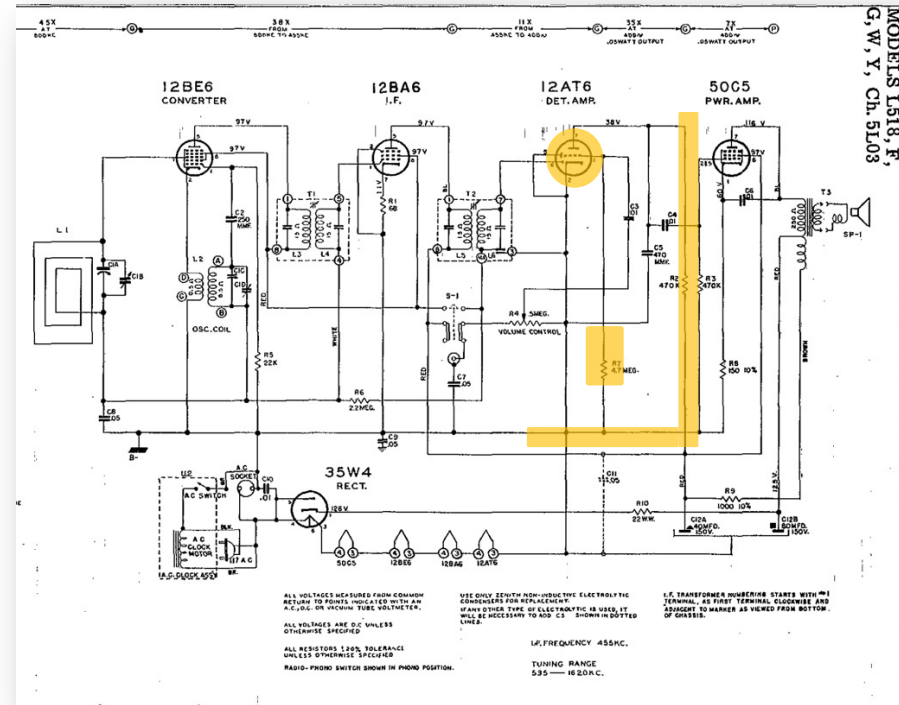
# Detector

- A 12AT6 Double-diode triode was used for detection, audio amplification, and automatic gain control
- Triode used for low noise



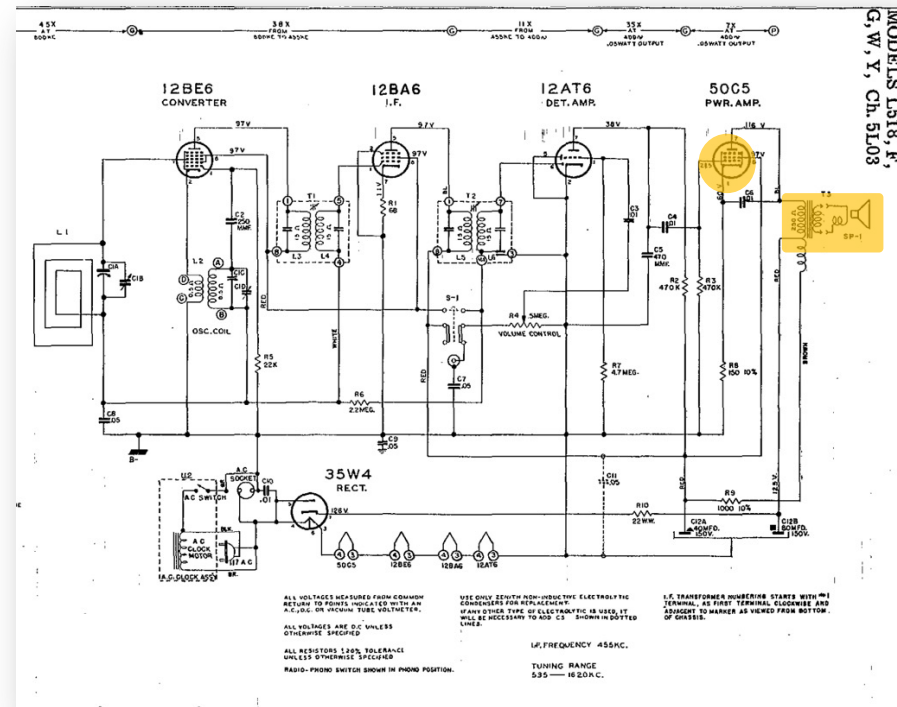
# Audio Amp

- Big Beefy 50C5 Pentode used as power amplifier
- Speaker driven through coil for load matching


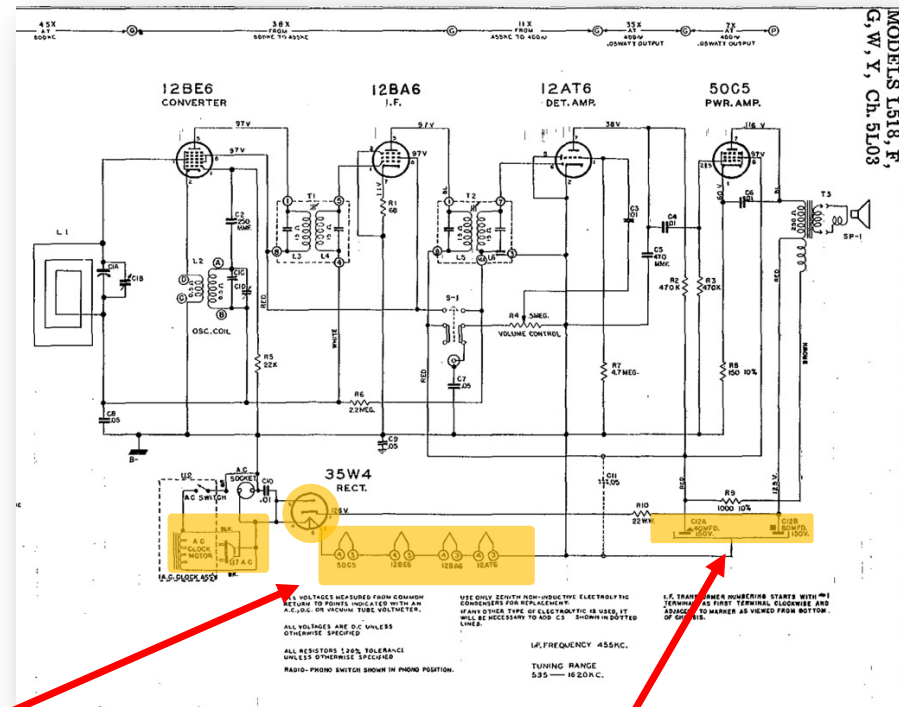
# Power Supply

- 35W4 used for converting 120 VAC into about 150 VDC
- *No transformer.* This set was a hot-chassis (could get electrocuted opening touching the back side)
- Notice how the filaments are all strung in series. Their filament voltages are:
  - $35+50+12+12+12 = 121V$   
... $120V_{RMS}$  ?
  - Coincidence? Nope!



*Big juicy caps to absorb the ripple from AC-DC conversion*



# 1953 Emerson 724


- Another All-American-Five set also from 1953.
- Looks so different!
- So much better!!!



# Emerson 724

MANUAL OF 1953 MOST-OFTEN-NEEDED RADIO DIAGRAMS

## Emerson Radio

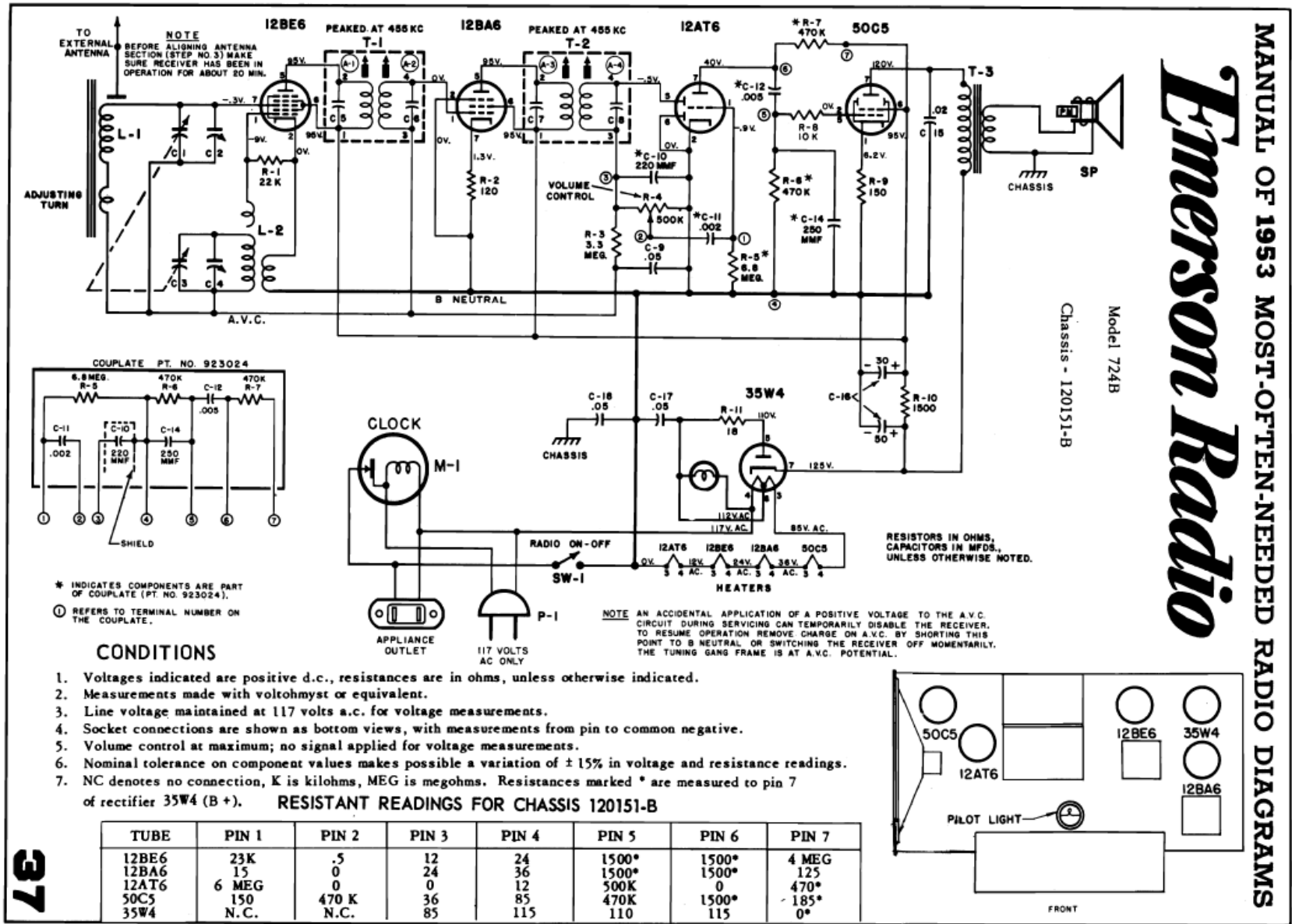

37

# Basically exactly the same as L518

- Both sets use the same set of tubes:
  - 12BE6 Pentagrid converter (oscillation/heterodyning)
  - 12BA6 IF amplifier
  - 12AT6 Detector/first stage AF amp (pre-amp)
  - 50C5 power amp tube driving audio-transformer matched speaker
  - 35W4 for AC-DC conversion
- All the companies had nearly identical models at similar price points...you were mostly buying different cases and brands.

# First of a Common Pattern

- EECS Developments/creations outpaced our ability to anticipate how we as a society would react
  - Lighting
  - TV
  - Computers
  - Cellphones
  - Tiktok
  - ChatGPT
  - Etc...
- All thanks to what this thing started
- A lot to take in.




# But the Days of Tubes were Numbered

- A lot of pressure to make electronics smaller
- Later variants of vacuum tubes did get smaller:
  - Subminiature tubes
  - Compactrons
  - Nuvistors

# Next Time

- Solid-state triodes appear

Step aside, boomer

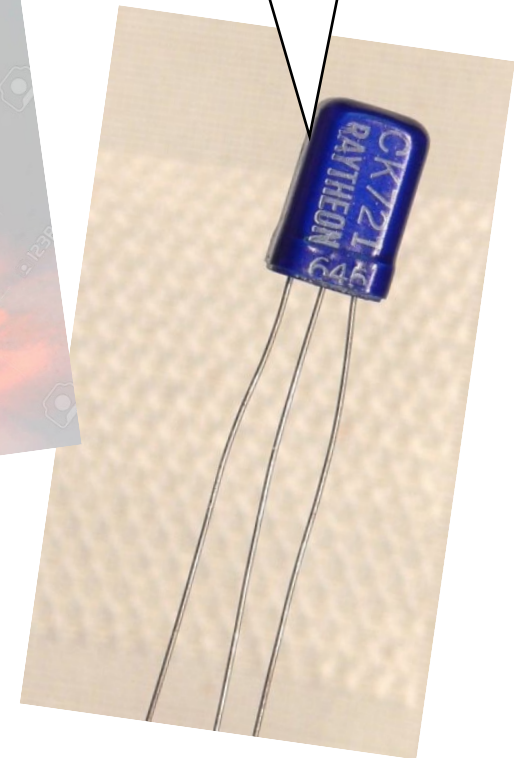

## THE TRANSISTOR - SUCCESSOR TO THE VACUUM TUBE?

By John A. Doremus,  
Chief Engineer, Carrier and Control Engineering Dept.  
Motorola, Inc.